



CPSSC 2019

Next Generation of Data Center Power Architecture

- Opportunities and Challenges


by

Fred C Lee

Virginia Tech

作者授权中国电源学会发布，未经作者同意禁止转载

Beyond Moore's Law

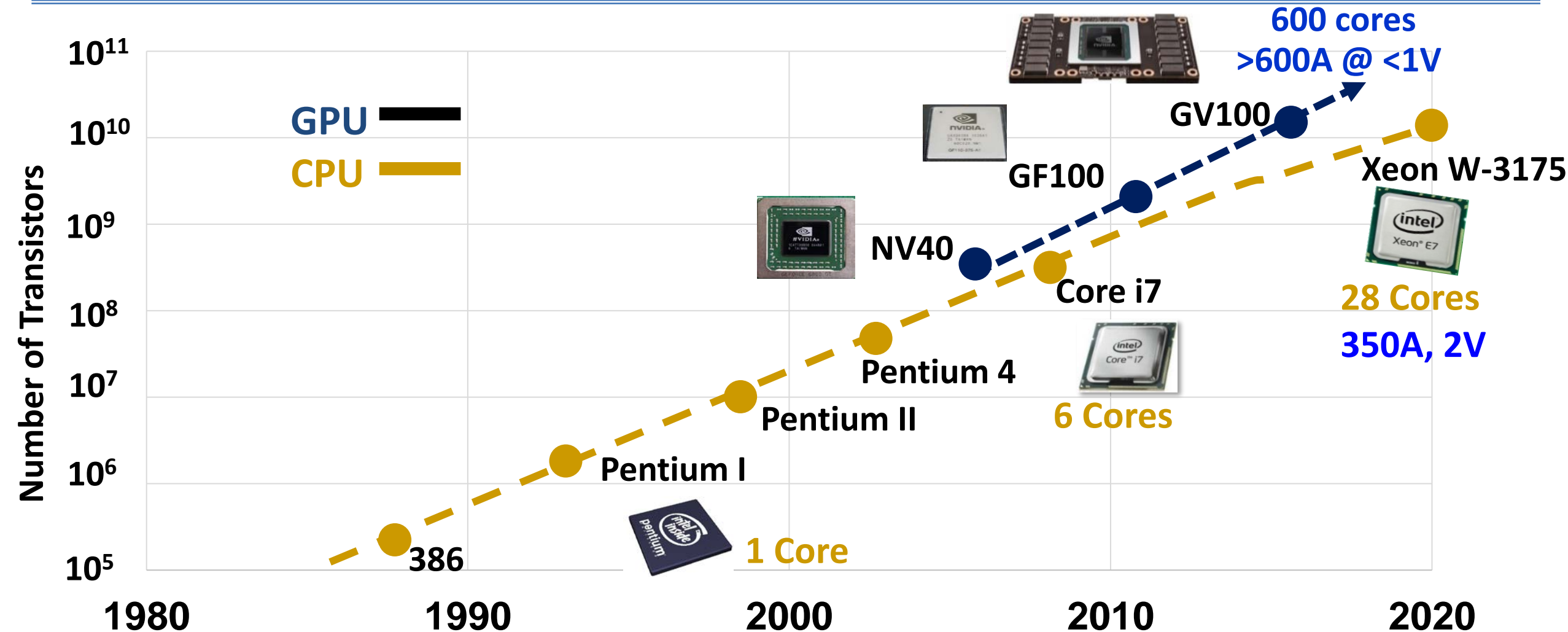

Power Per Server Rack > 25 KW

1V @ 25,000 A

Significant Challenge for VR Design

Generation 1: Data Center Power Architecture



35KV


480V VAC

208VAC, 1 phase




Transformer


Cable
97%

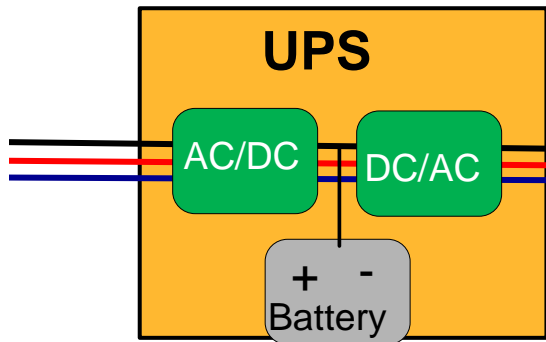

UPS
95%

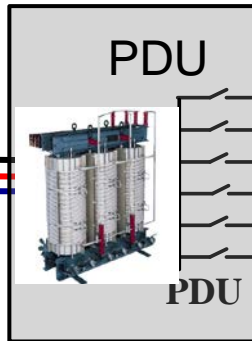

PDU
96%

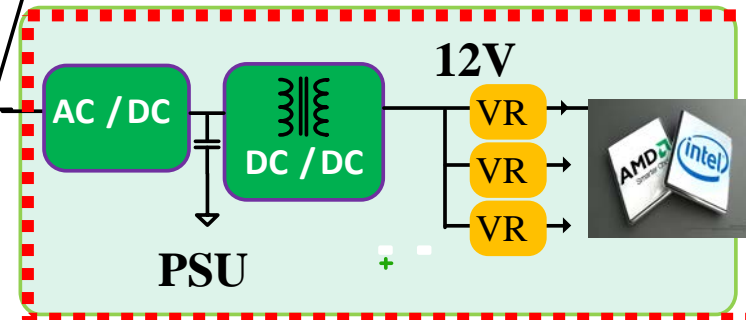

Server rack power supplies

PSU
96%

VRs
90% = 76%




Datacenter will consume 10% of electricity by 2020

1% energy saving → 3 nuclear power plants (each @ 1GW)

Data Center Rack


Voltage Regulators

>25,000A @ 1V

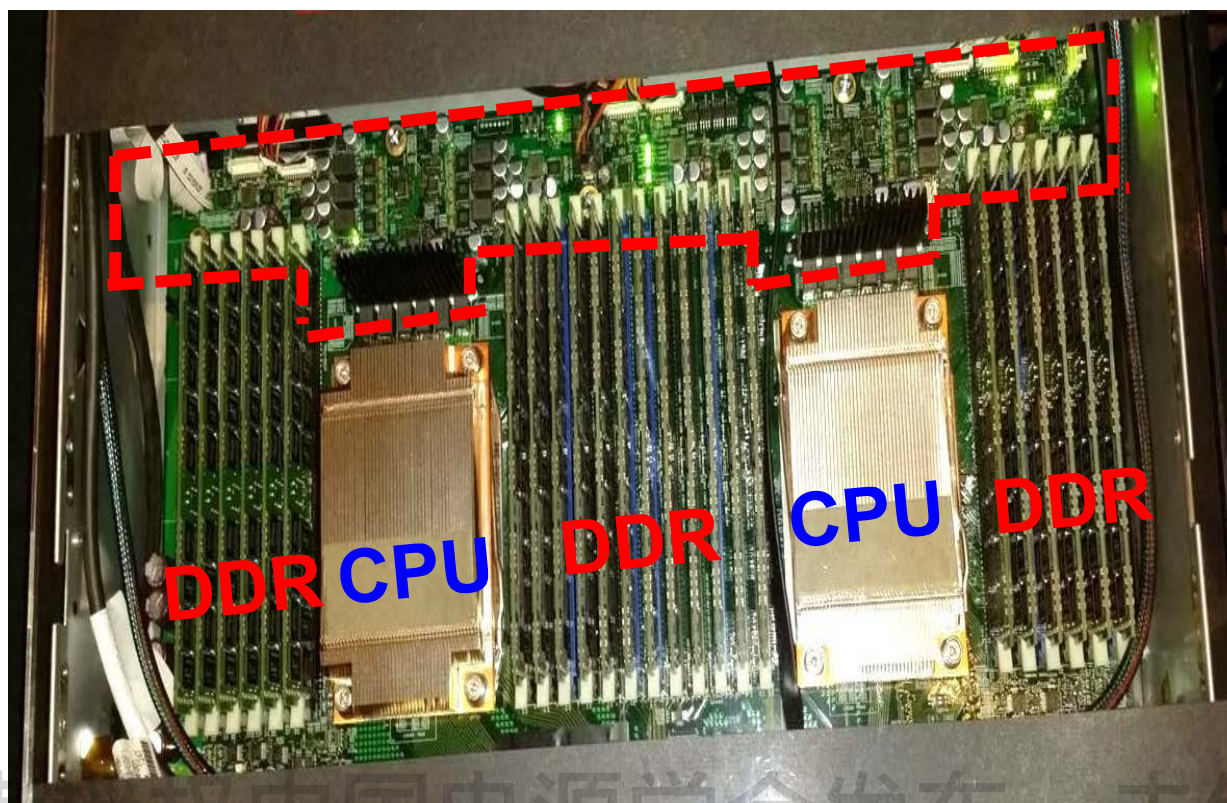


12 V Bus Ba

>2000A

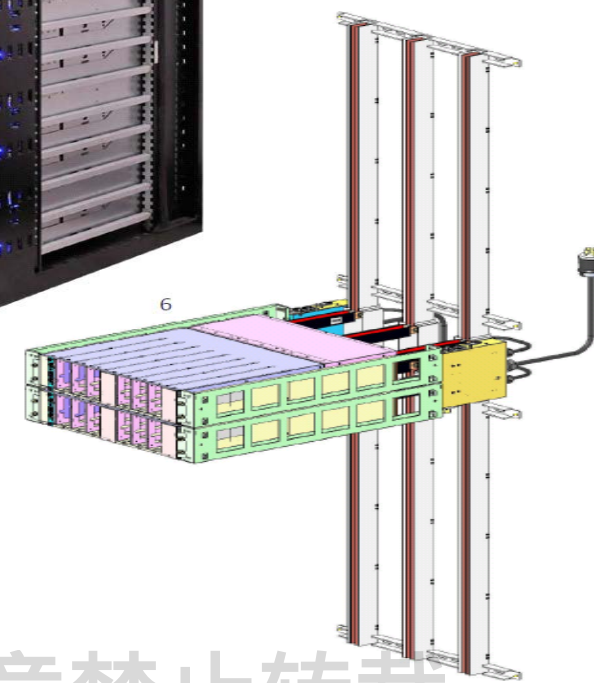


Generation 2: Data Center Power Architecture

Generation 1

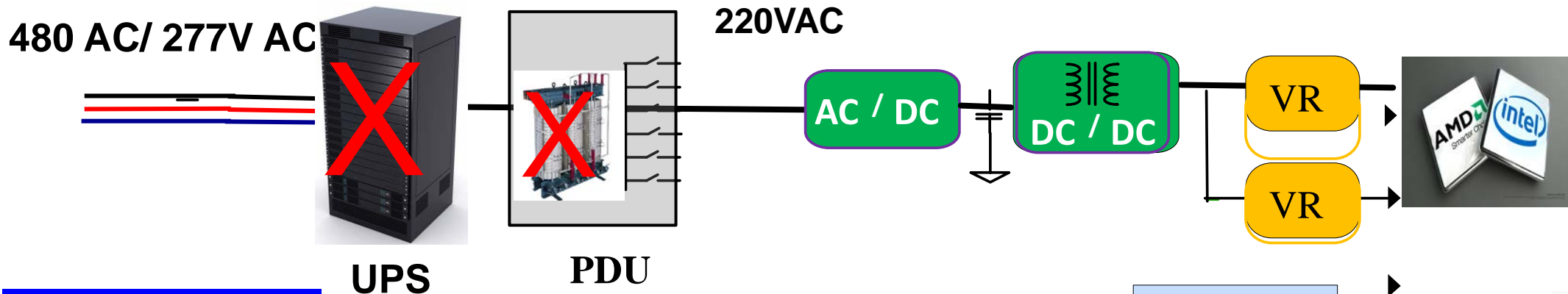

Generation 2

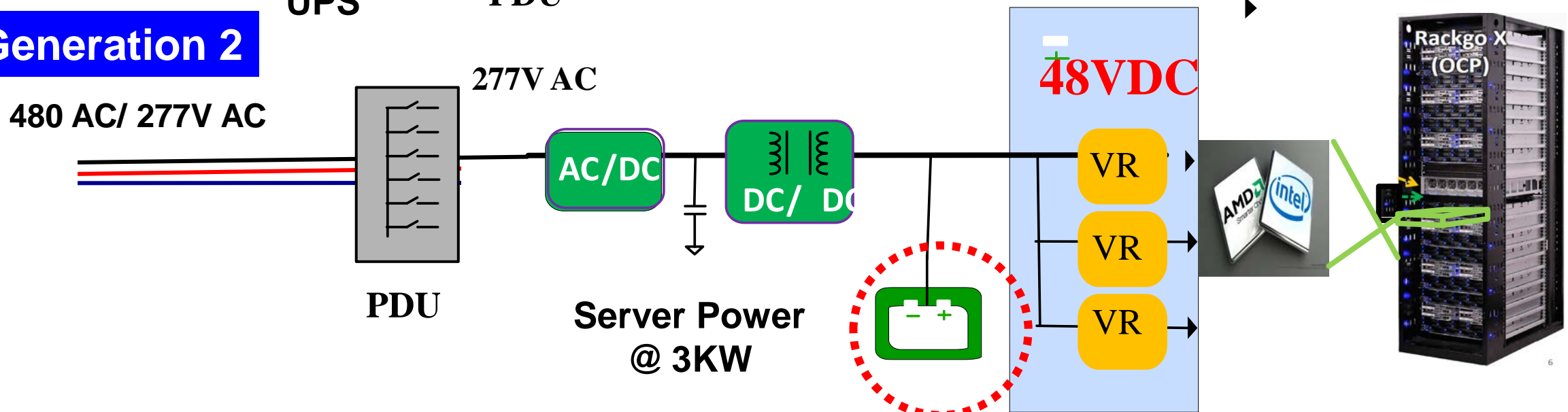

Efficiency 97% 96% 91% 85%

Energy saving equivalent to 27 nuclear power plants (each @ 1GW) = 2.5 三峡

VICOR's Two-Stage (2012)


40-60V

PRM (Regulator)
ZVS Buck/Boost



48V

VTM(Unregulated)
ZVS DC/DC

1.x V

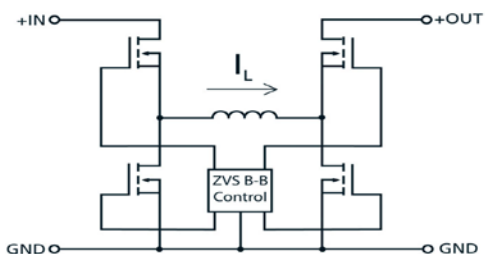


Buck/Boost

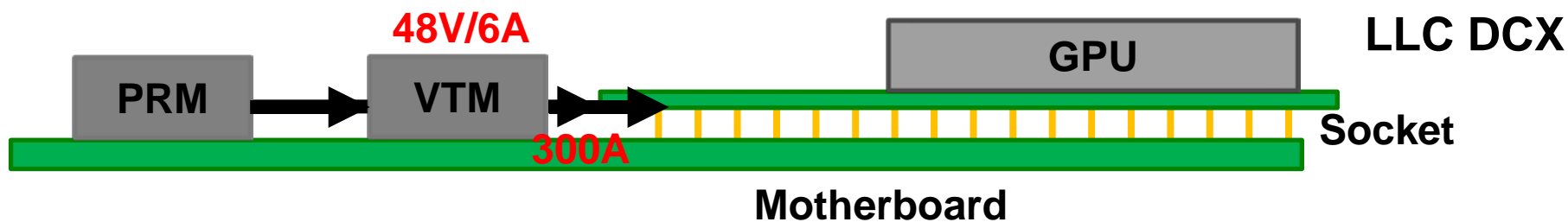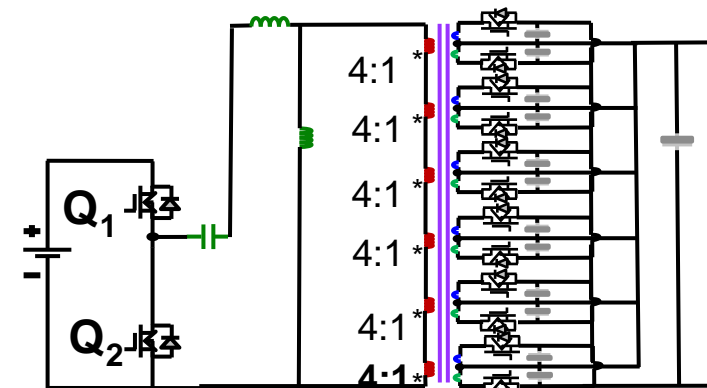

作者投稿中国电源网公开发布, 未经作者同意禁止转载


High-Density, High-Efficiency, Not Easily Scalable

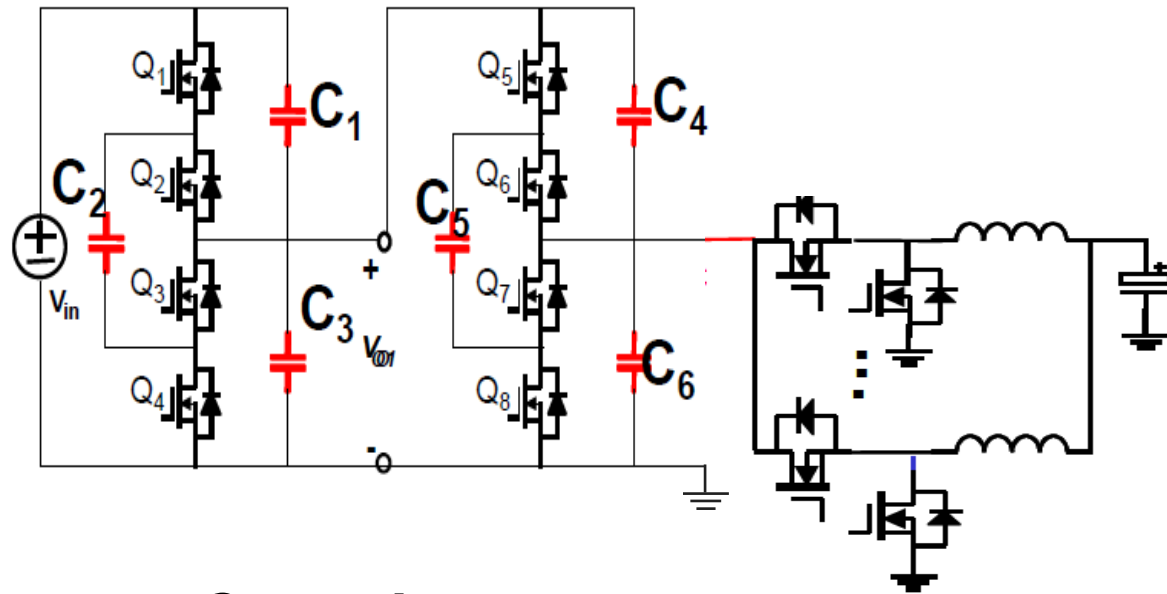CPES Switch Capacitor Voltage Divider (2008)



**4:1 Capacitor
Voltage Divider**

Multi-Phase VR

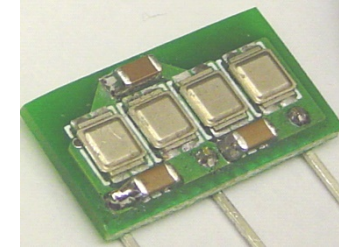


Eff = 98%
PD = 1050 W/in³

First Stage: High Efficiency and Power Density

Second Stage: Scalable, Low Cost and High BW Control

作者授权中国电源学会发布，未经作者同意禁止转载

Google's STC Two-Stage (2016)

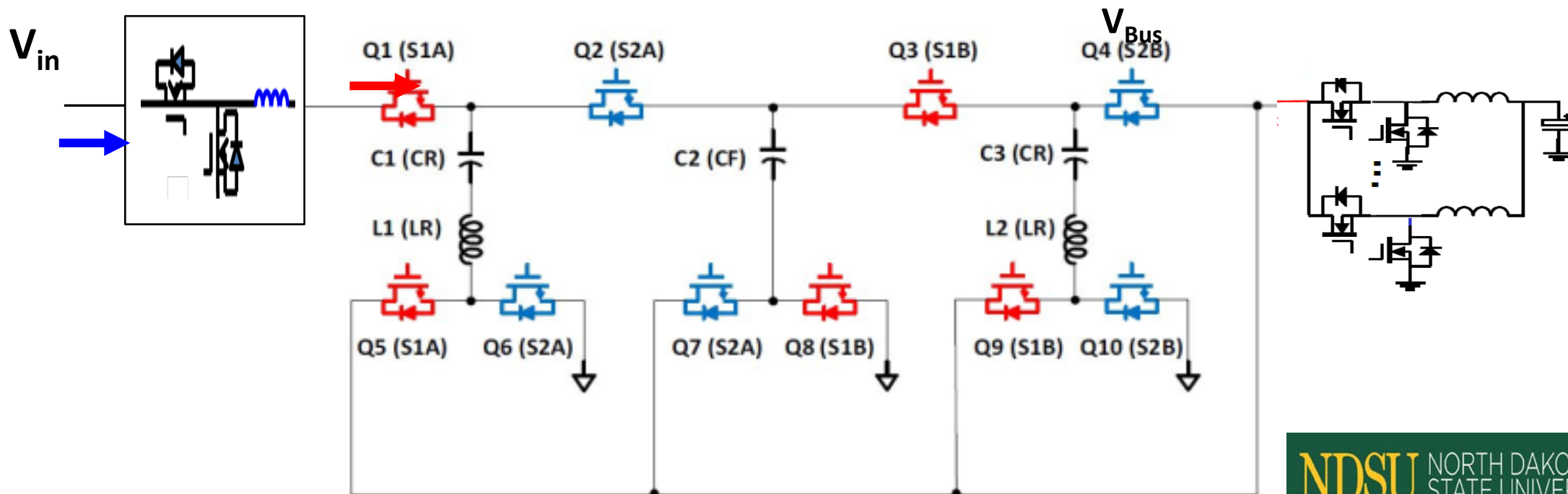


48/12V – 650W

Efficiency = 98.6%

Power Density ≈ 250 W/in²

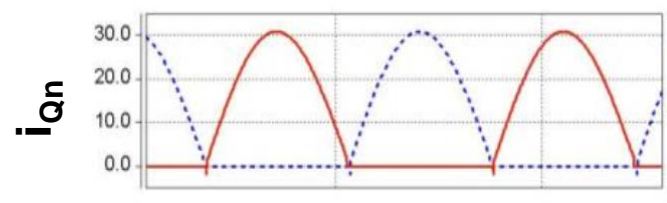
- Zero Current Switching Operati
- Sensitive to component tolerances
- Not easily extendable to lower bus voltage





作者授权中国电源学会发布，未经作者同意禁止转载

Google Proposed 48V Power Architecture

NVidia 48V SXM Card

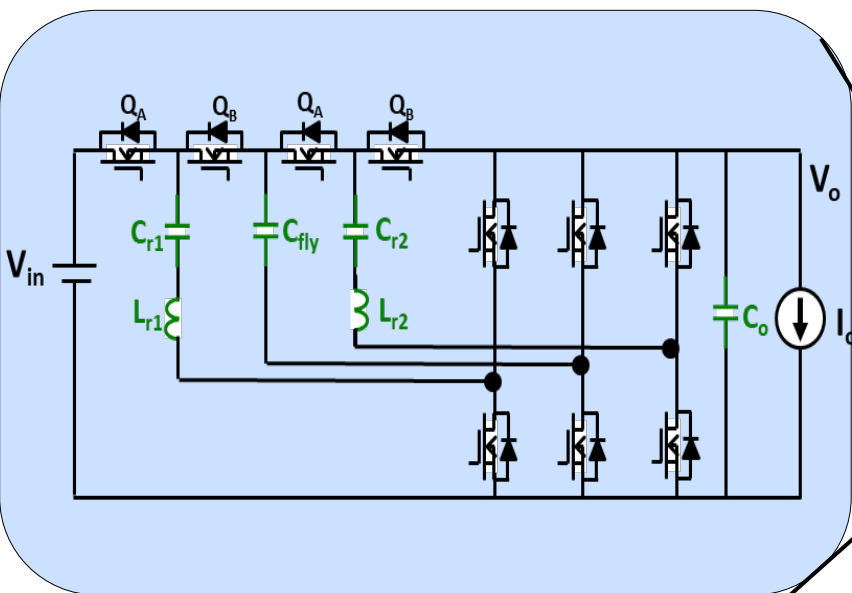



48V/12V
100KHz

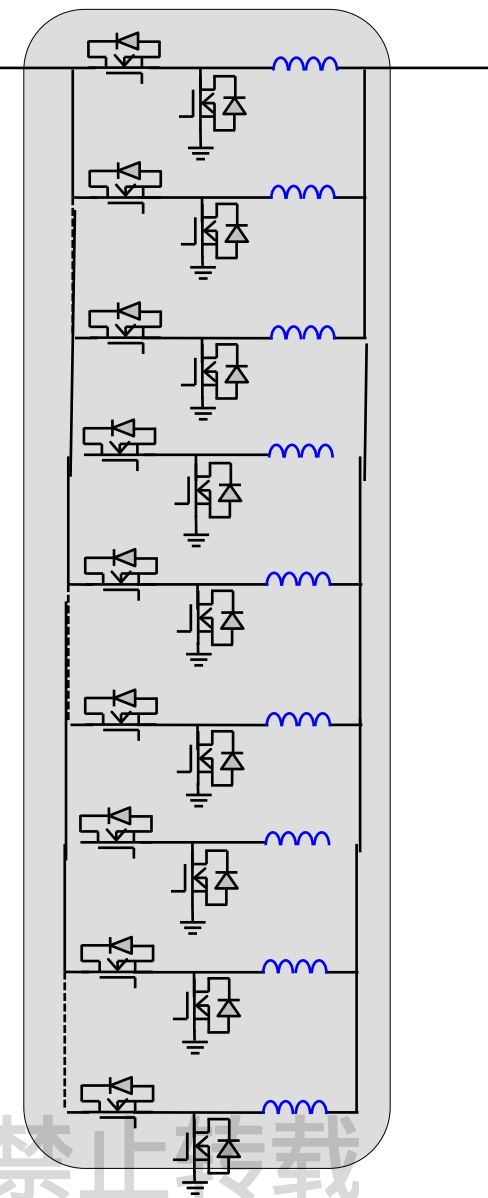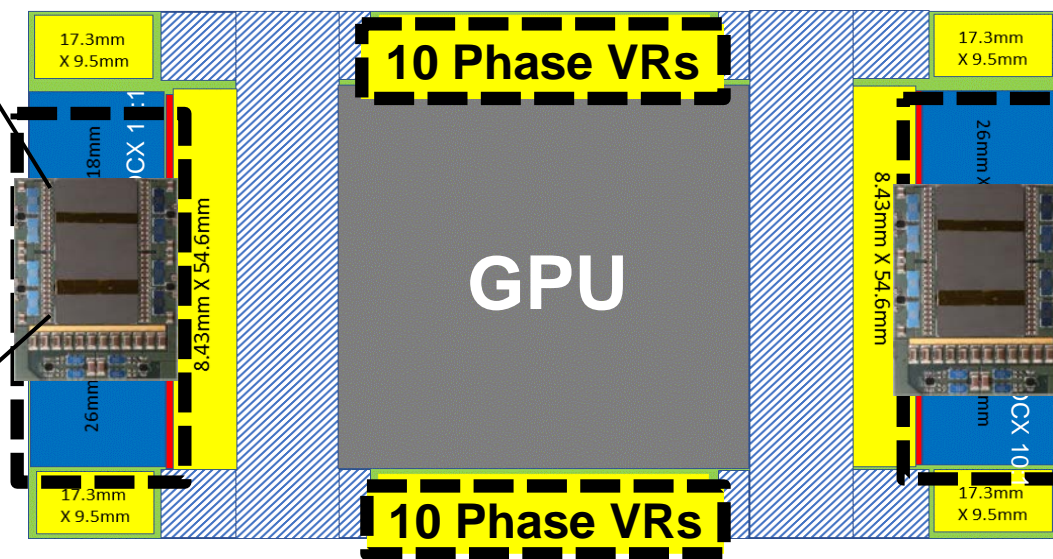



12V/1V
400-600 KHz

CPES Prototypes for 48V VRs

48V/12V - 900W

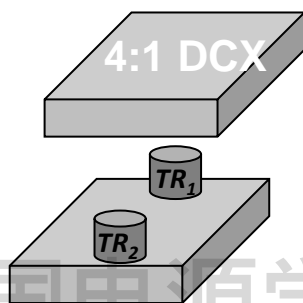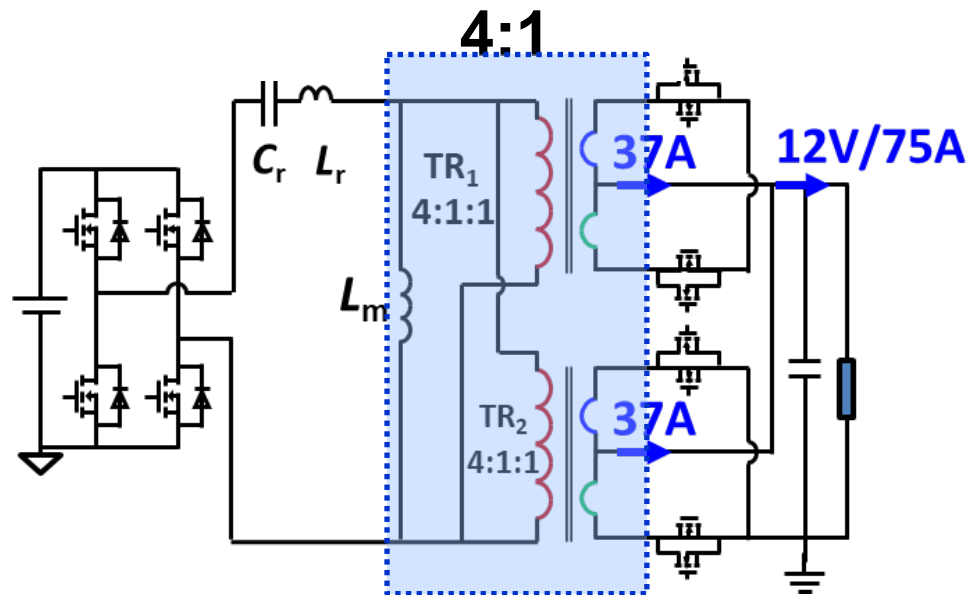


48V/6V - 900W

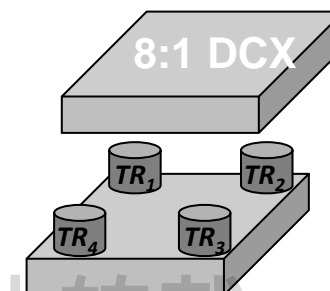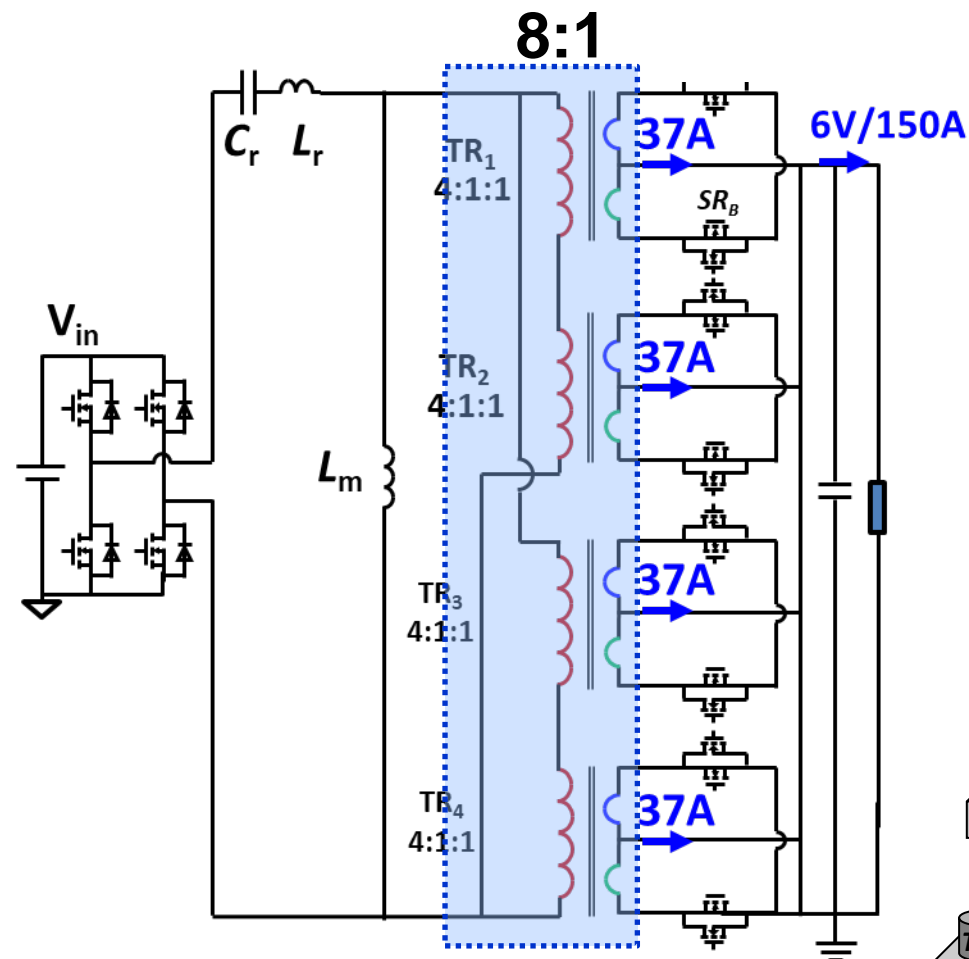


Comparison of 48V/12V Converter

CPES

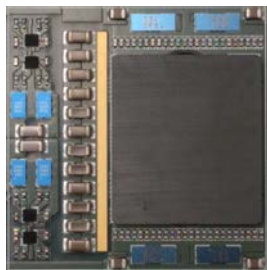


450 W/in²

Google's STC

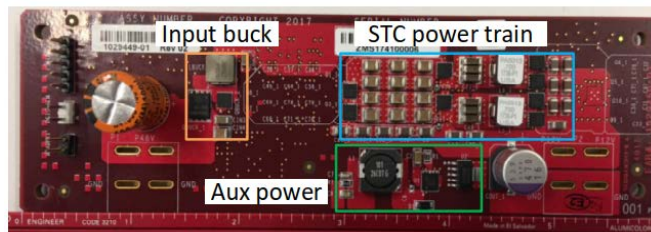


225 W/in²

MPS DCX

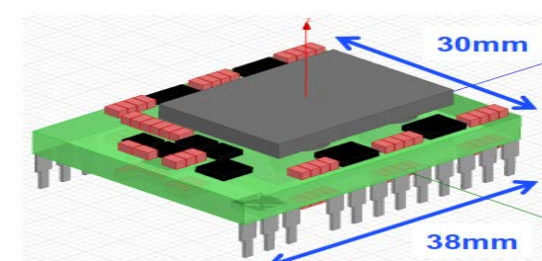


450 W/in²

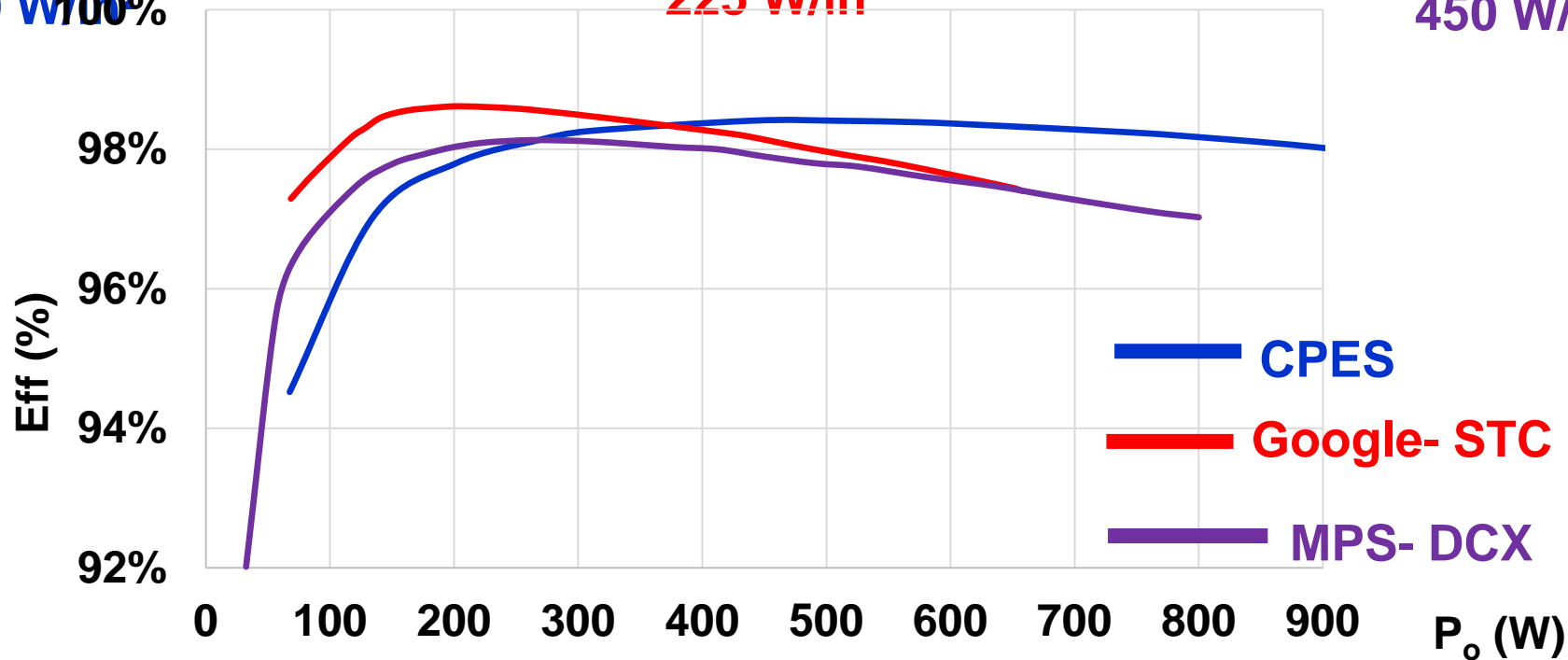


作者撰写的中国电源学会... Higher Efficiency and Power Density Than All Other Solutions

Comparison: 48V/12V v.s. 48V/6V


CPES: 48/12V

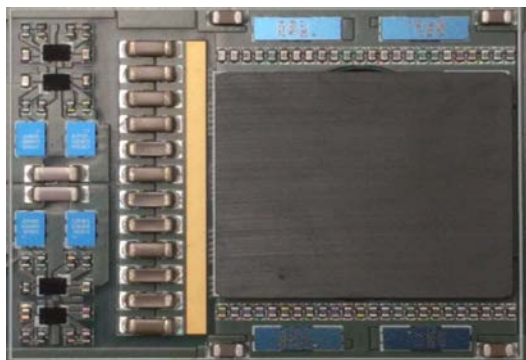


**GaN bases
1MHz
1600 W/in²
98.4%**

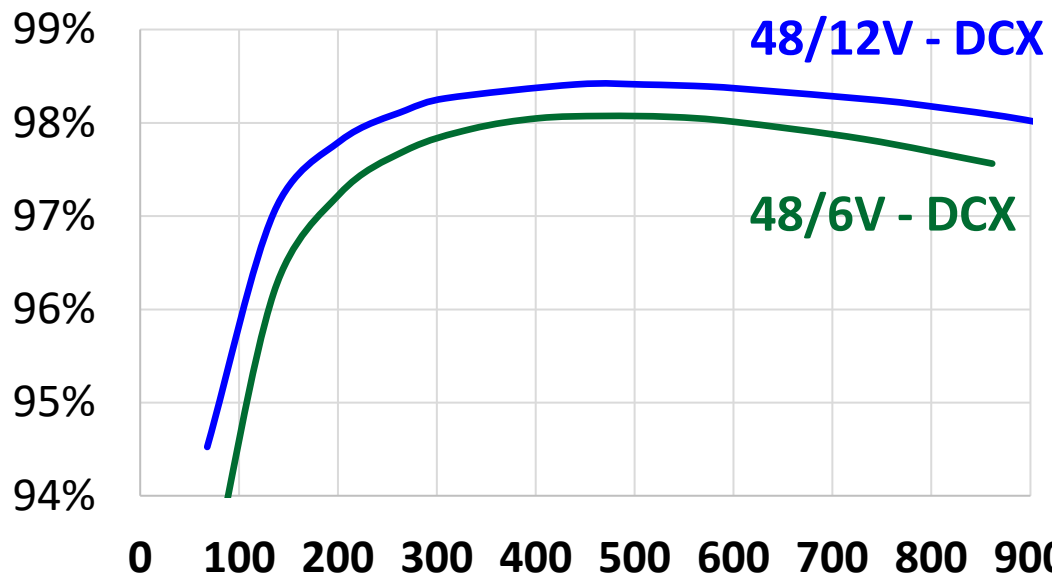

CPES: 48/6V

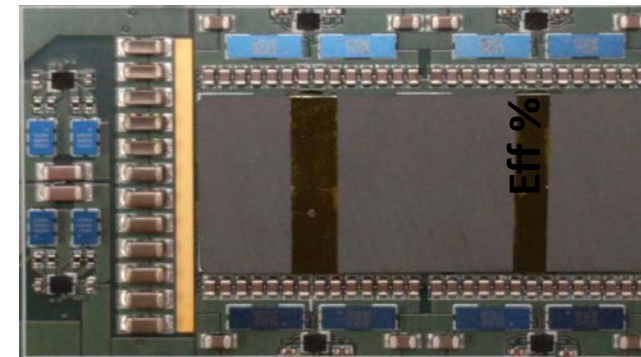

**GaN based
1MHz
1200 W/in²
98%**

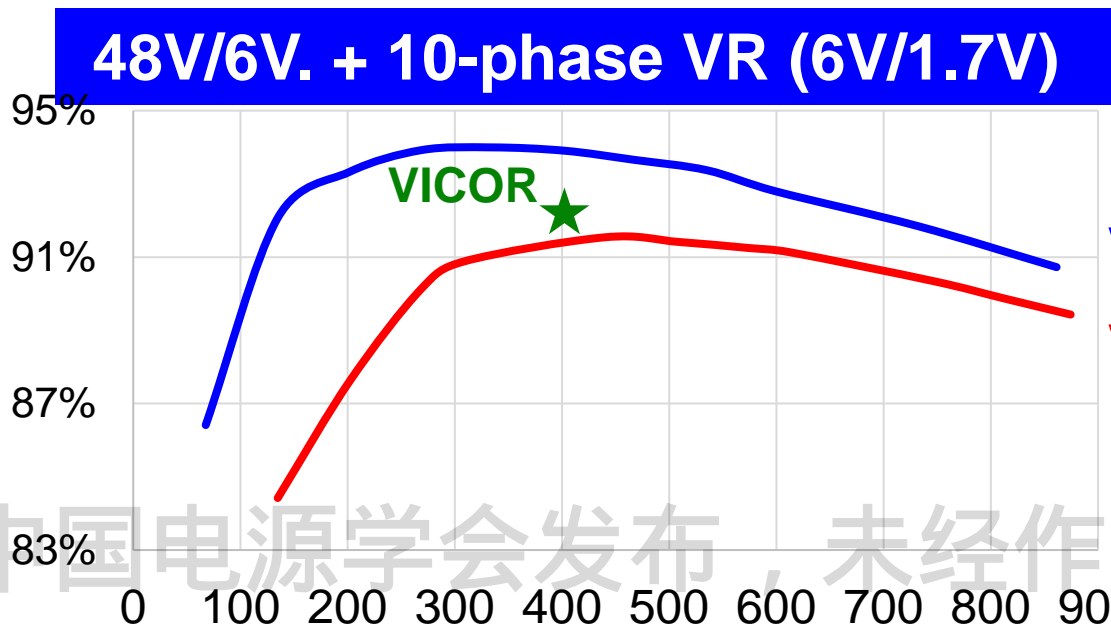

P_o (W)


V_{Bus} = 6V

V_{Bus} = 12V


Best efficiency demonstrated

Switch Capacitor Voltage Divider

48V to 12V

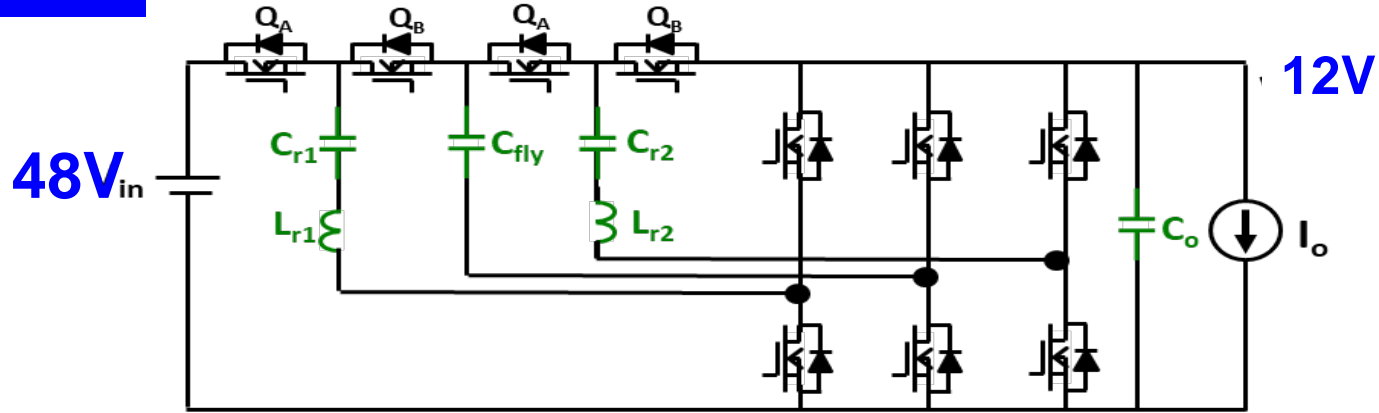

48V to 6V:

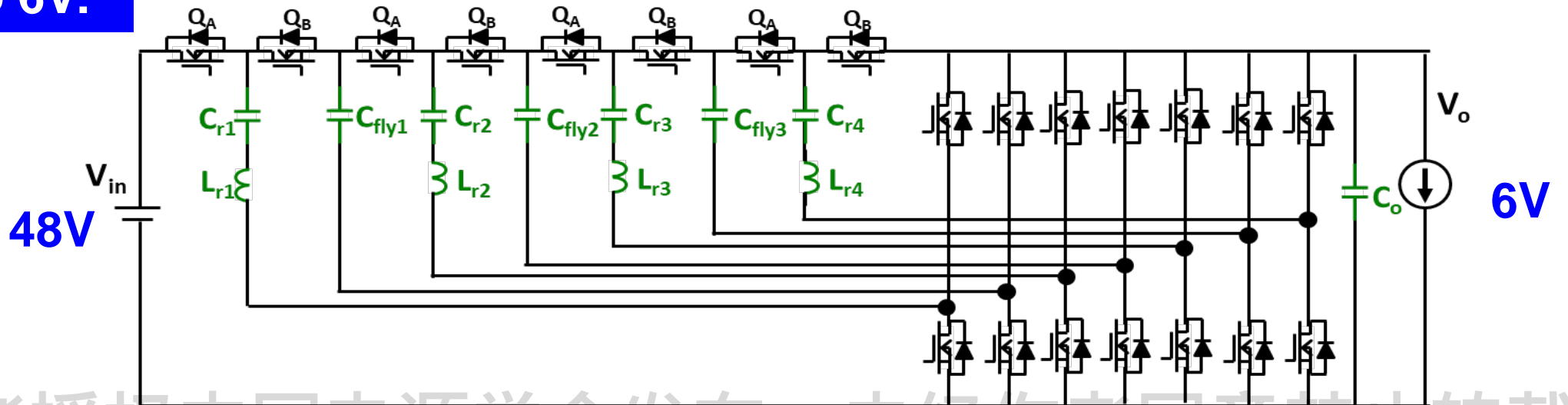


作者授权中国电源学会发布 未经作者同意禁止转载

Too complicate, not practical

Alternative # 2: Sigma Converter

LLC DCX with Programable Gain

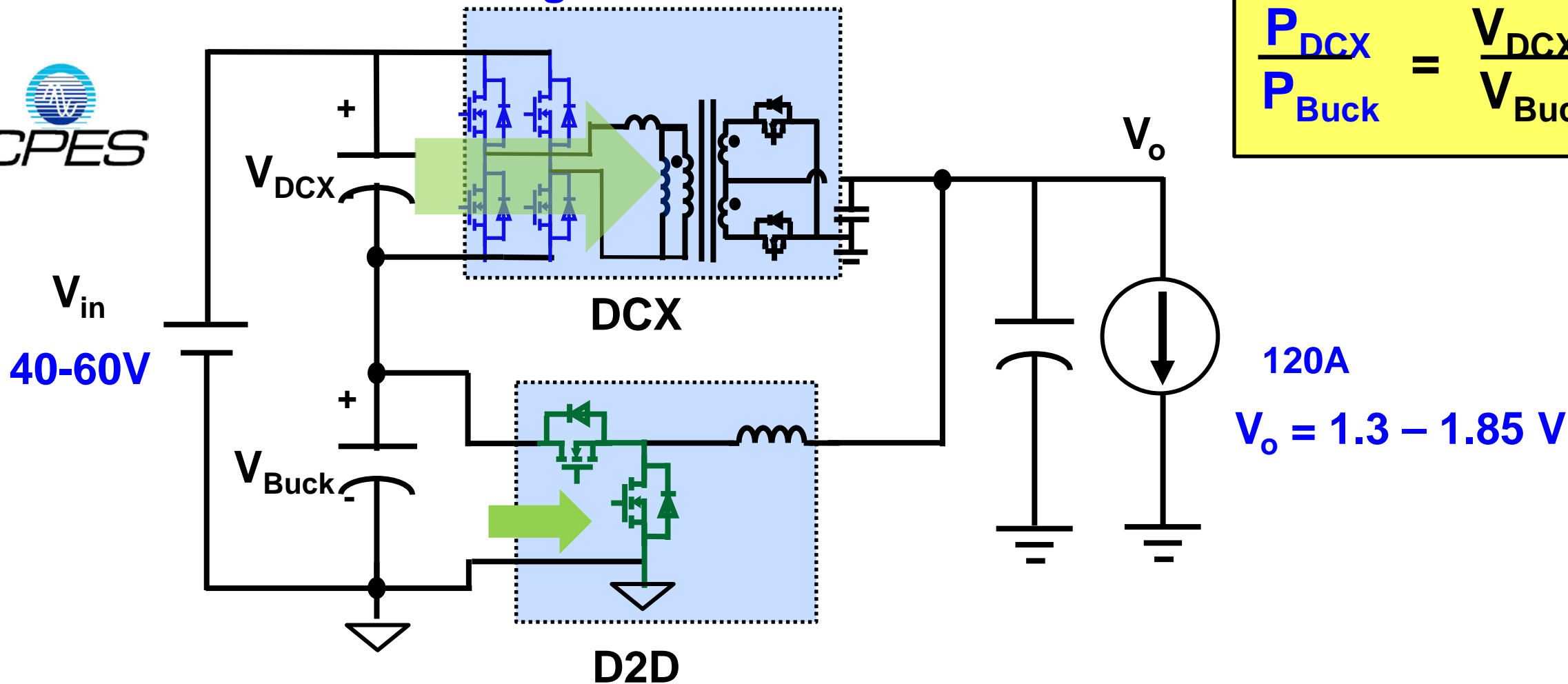


$$\frac{P_{DCX}}{P_{Buck}} = \frac{V_{DCX}}{V_{Buck}}$$


↑ More efficient power conversion comparing to two-stage 載

Operation Regions for Sigma Converter

Operating Regions

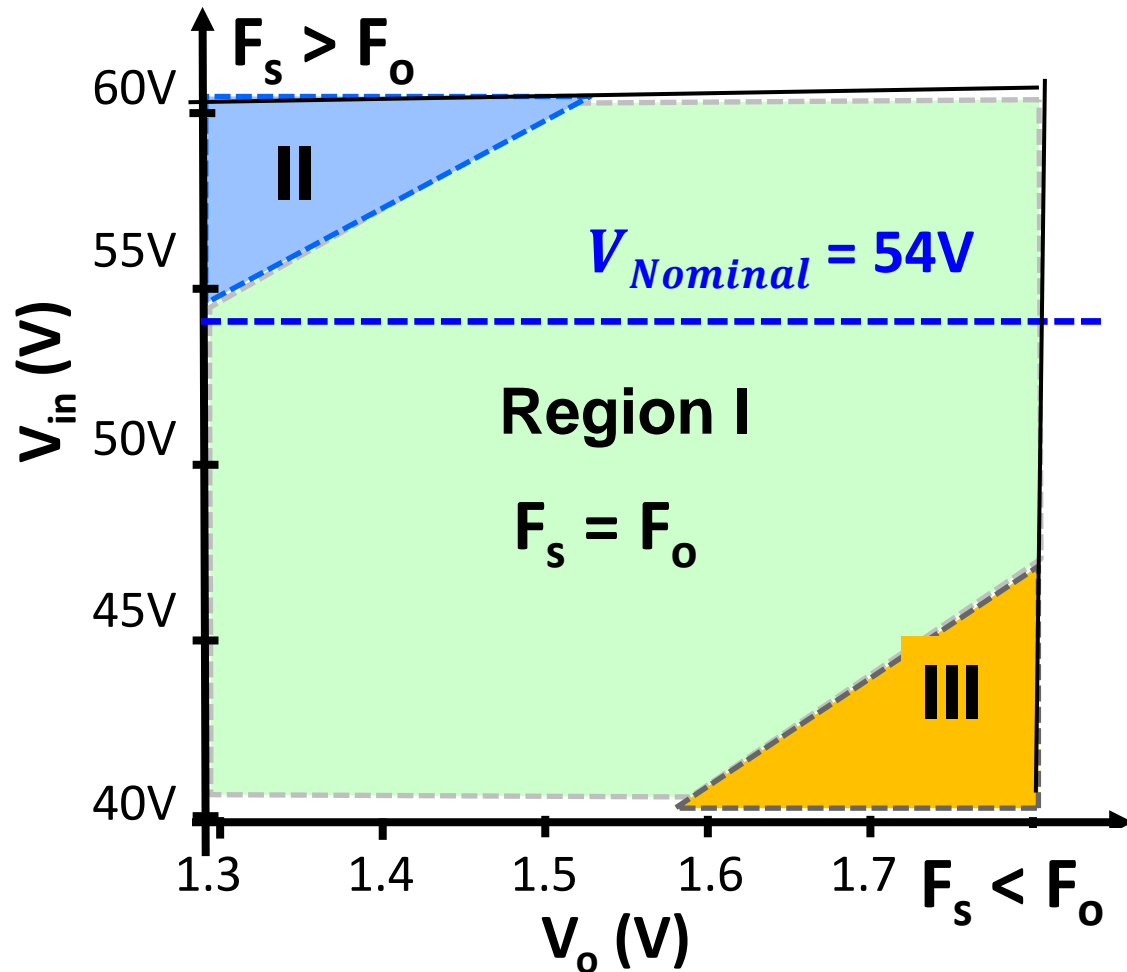


Required LLC Gain

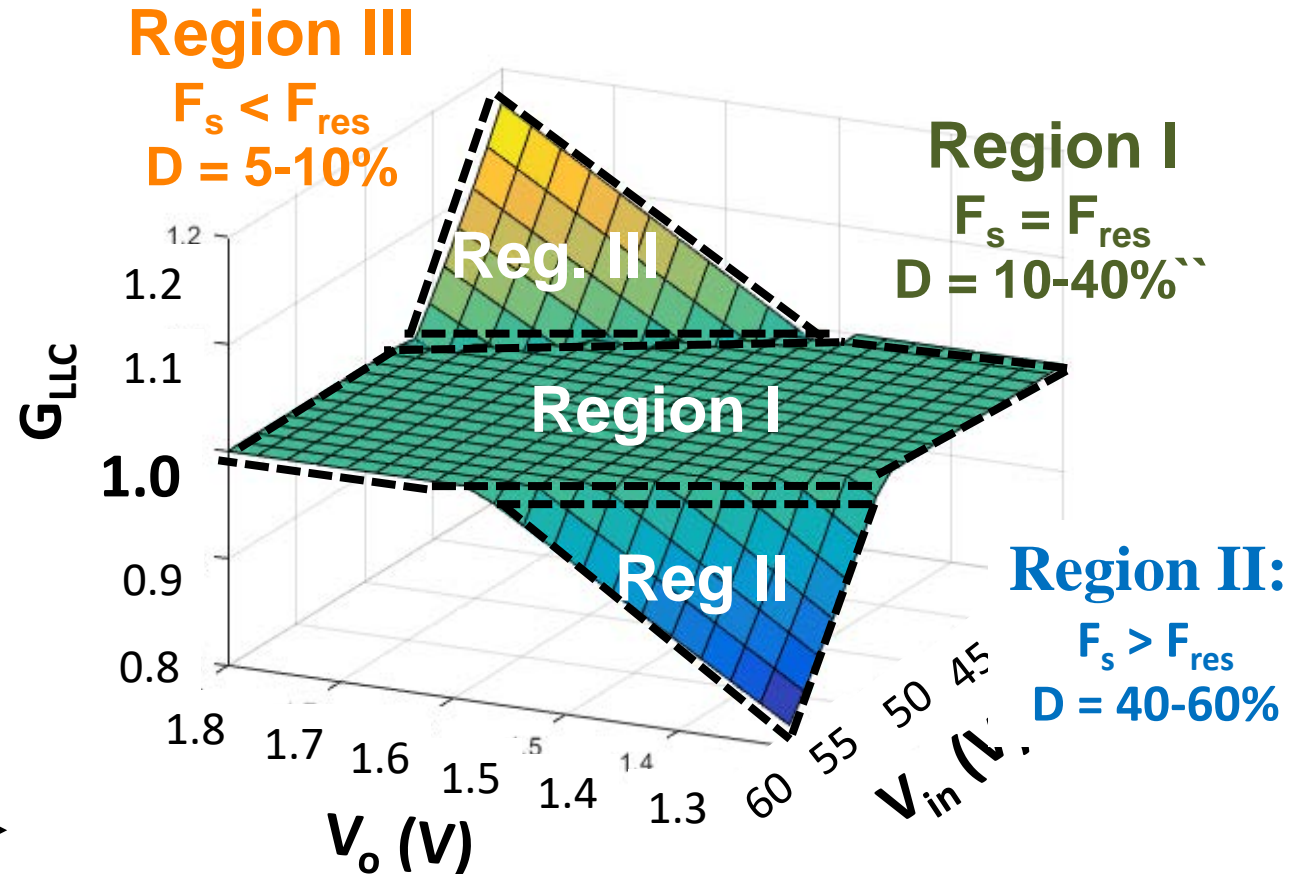

Optimal LLC Operation with $F_s = F_{Res}$ During Nominal Voltage Ranges


LLC Gain Requirements For Wide Range Operation

Operating Regions

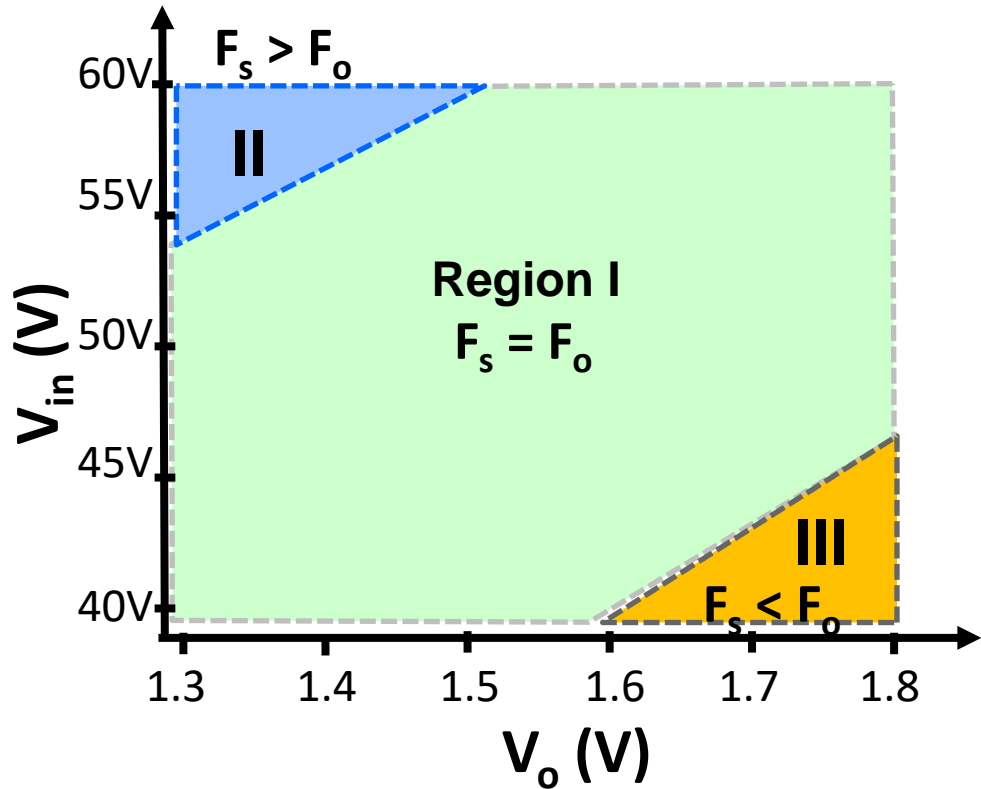


LLC Gain Characteristics

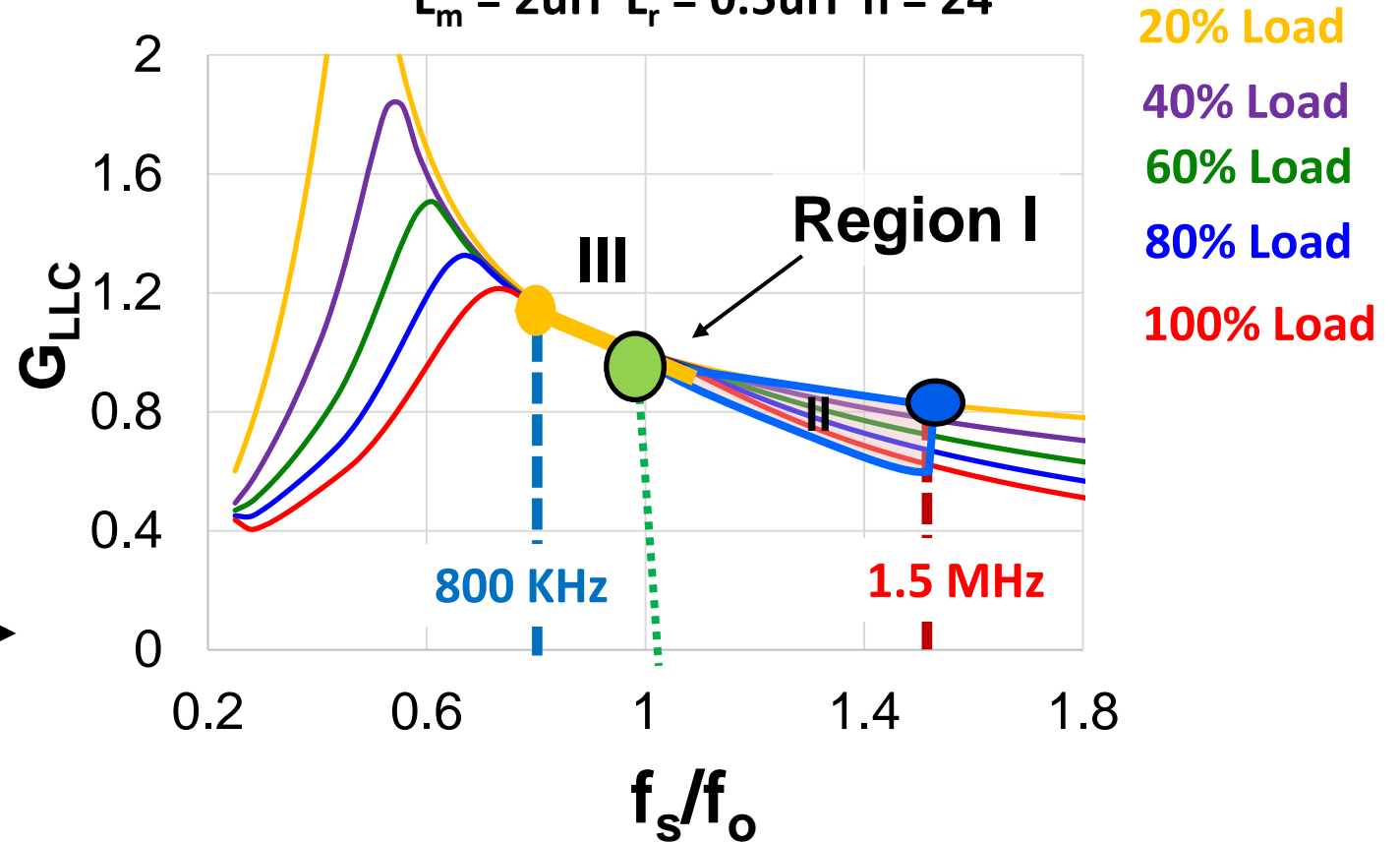$L_m = 2\mu\text{H}$ $L_r = 0.5\mu\text{H}$ $n = 24$




Relatively narrow frequency range for required LLC gain

Sigma VRM Experimental Results

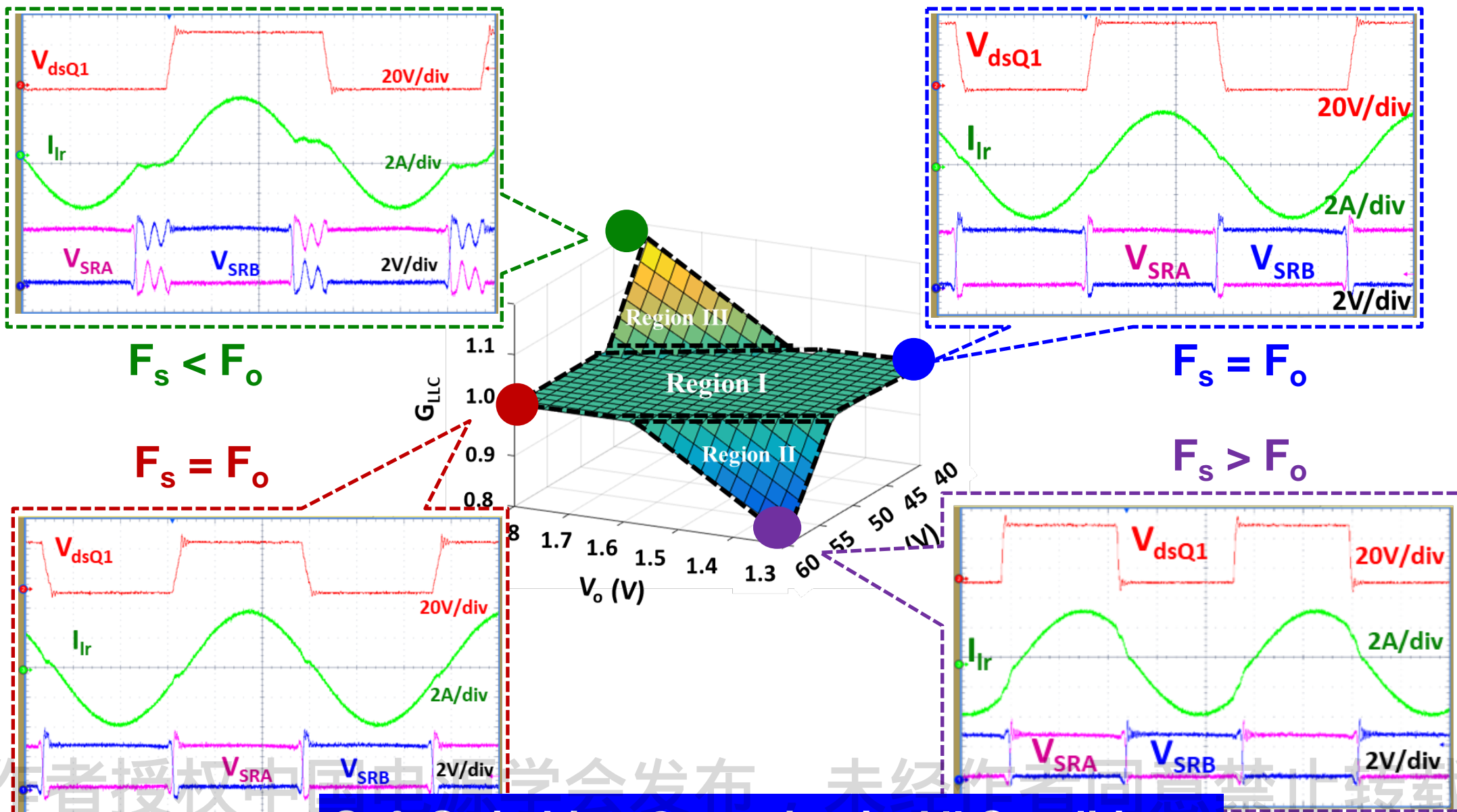


Soft Switching Operation in All Conditions


Integrated Inductors and Transformers

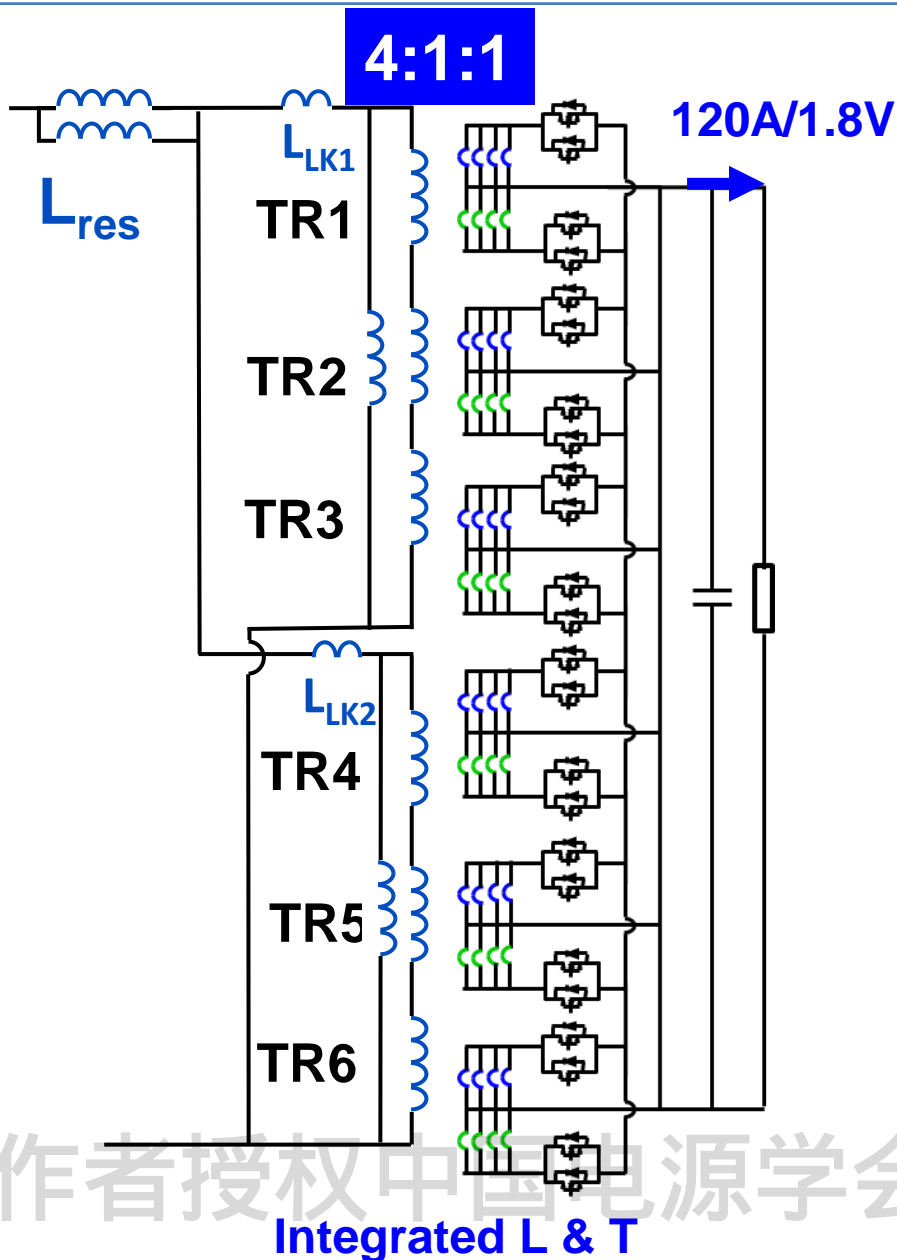

Secondary Windings

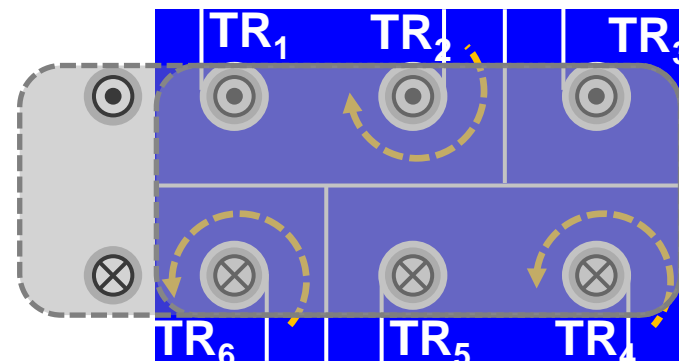


Primary Windings


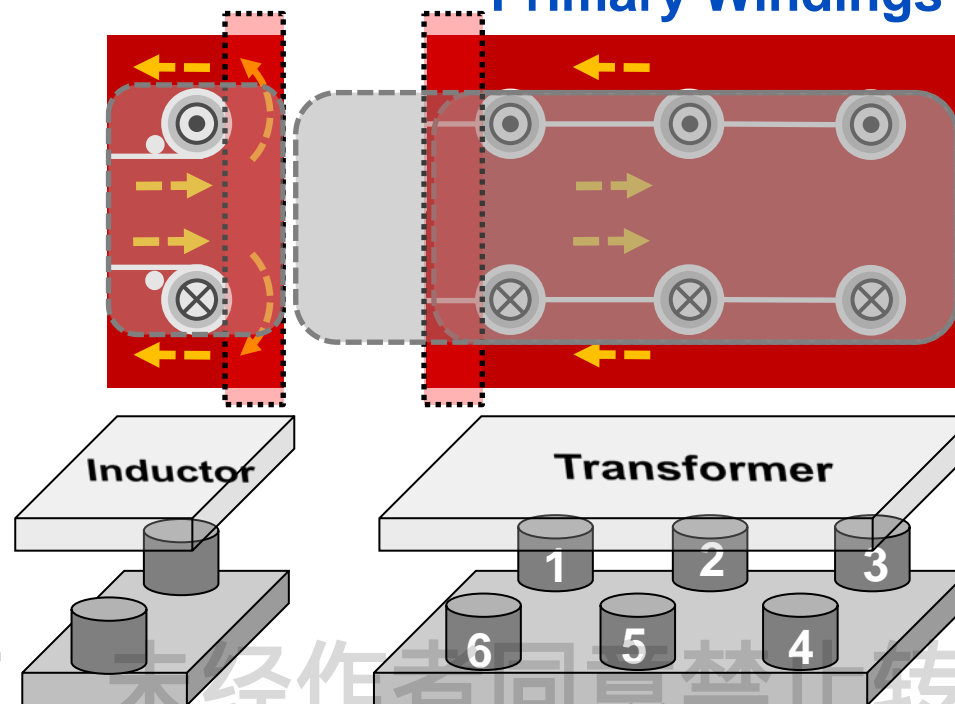


Sigma Converter Hardware Prototype

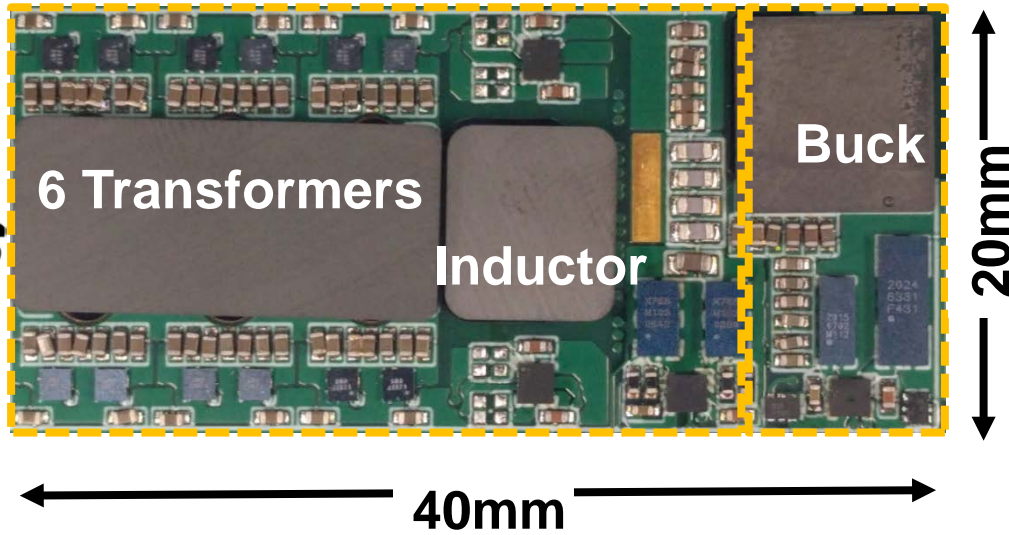$V_{in} = 40 - 60 \text{ V}$ $V_o = 1.3 - 1.85 \text{ V}$ $I_o \approx 120\text{A}$



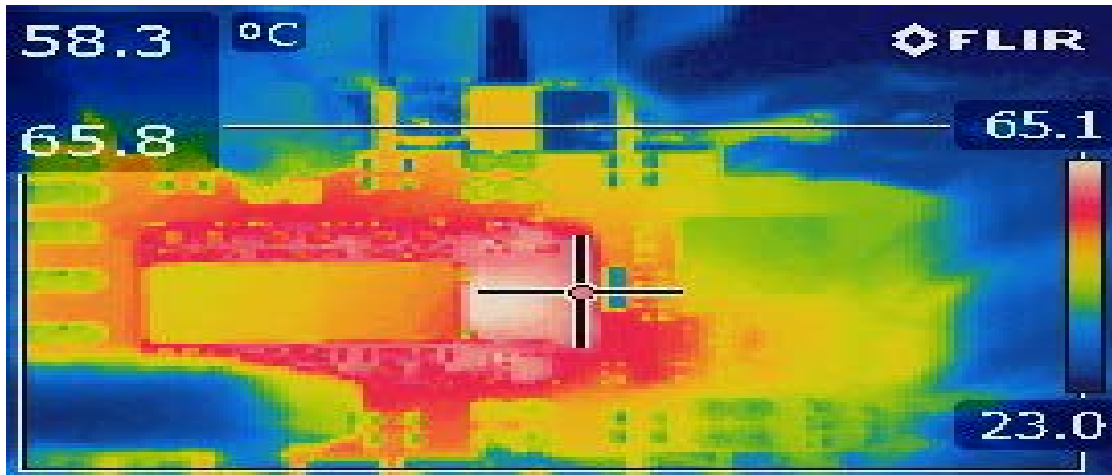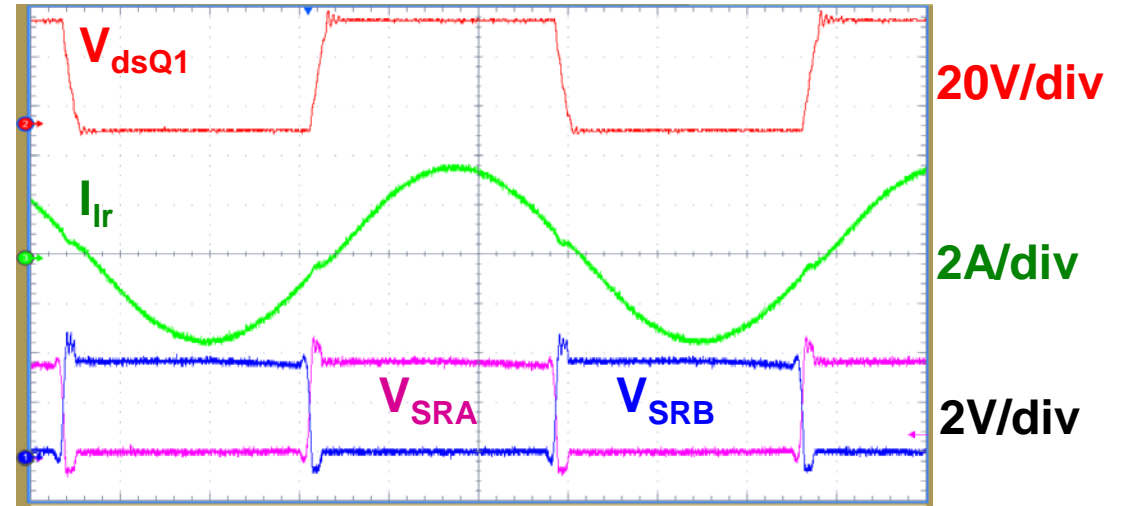$V_{in} = 54\text{V}$, $V_o = 1.8\text{V}$, $F_s = F_o$




- Power Density > 700W/in³
- ZVS Operation
- Excellent Thermal Performance

Wide Range 48V VRM Design Example


$V_{in} = 40 - 60 \text{ V}$

$V_o = 1.3 - 1.85 \text{ V}$

$I_o \approx 120\text{A}$

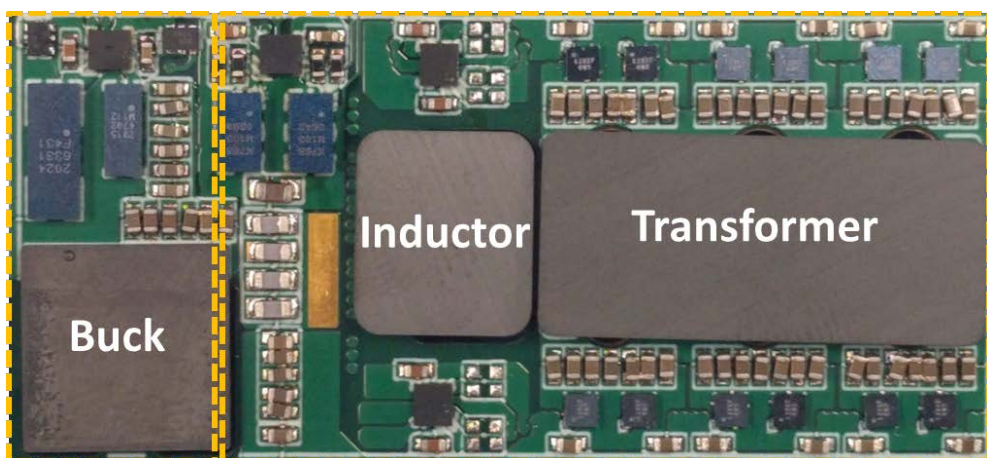

700W/in³

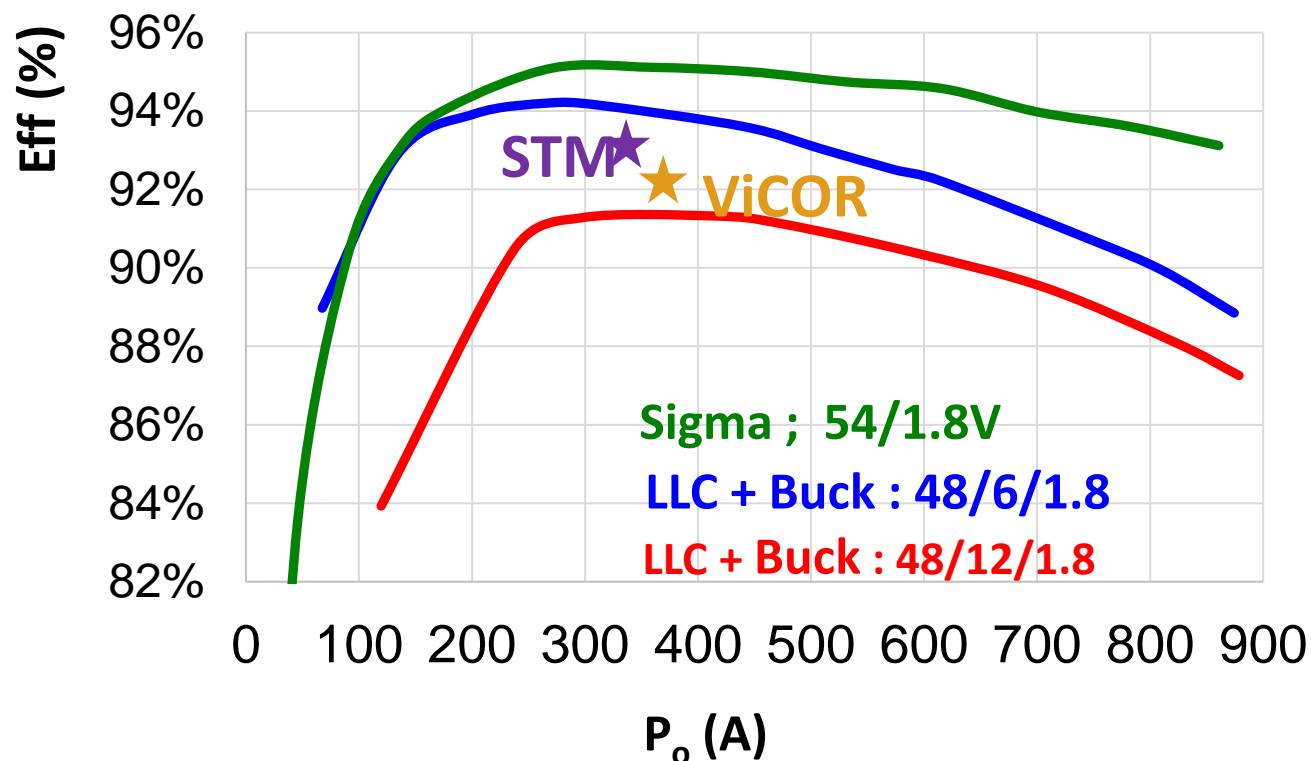


LLC converter serves as a variable gain DCX

Buck converter for regulating output voltage

作者授权

禁止转载

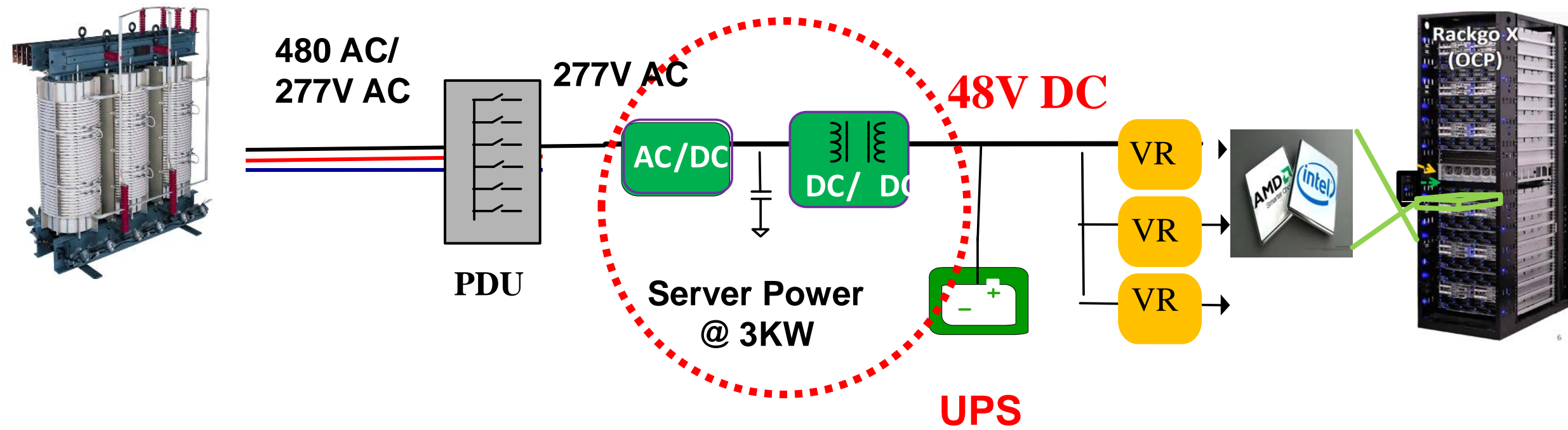Generation 2: Data Center Power Architecture




Efficiency 97% 96 % 91% = 85 %

作者授权中国电源学会发布，未经作者同意禁止转载




Integrated Magnetics (3L & 3T)

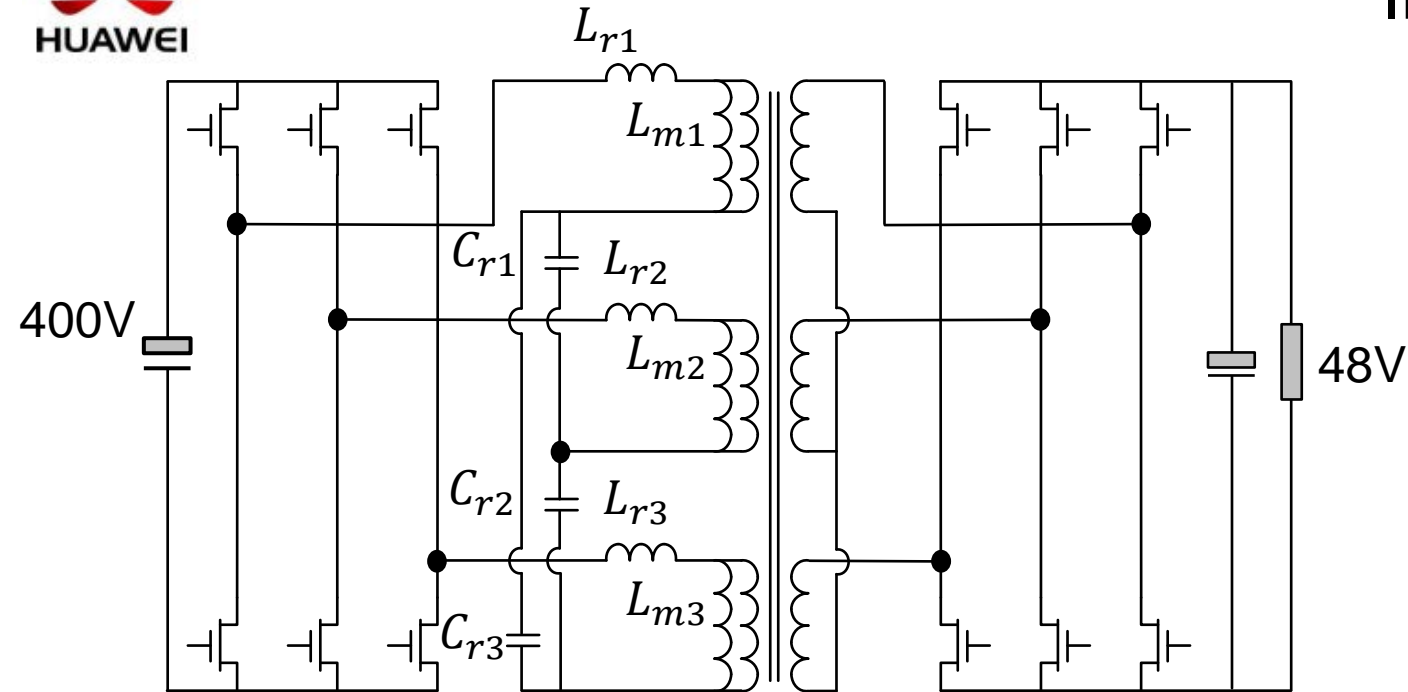

Primary: Y
(Δ -connection for Cr)


Secondary: Y

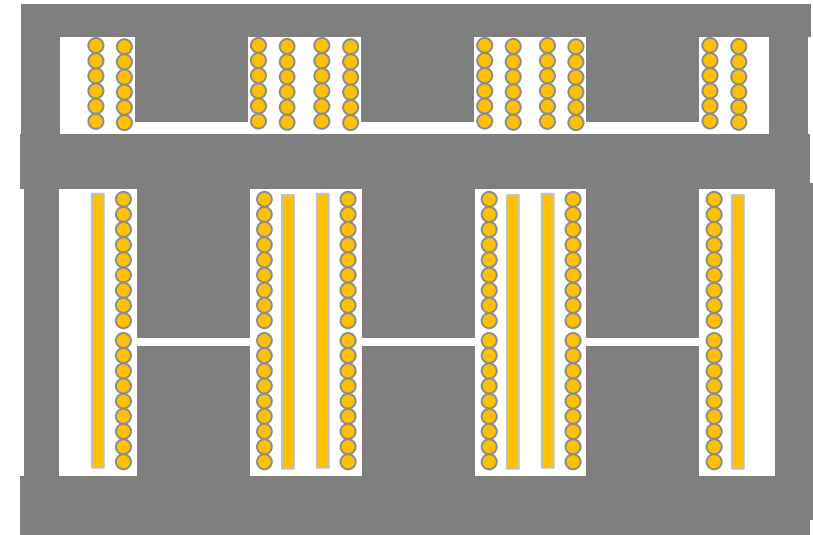

- **Switching frequency 100 kHz**
- **Power Density 40.8 W/in³**
- **Peak efficiency ~ 99%**



作者授权中国电源学会发布，未经作者同意禁止转载

Primary Y Secondary in Parallel

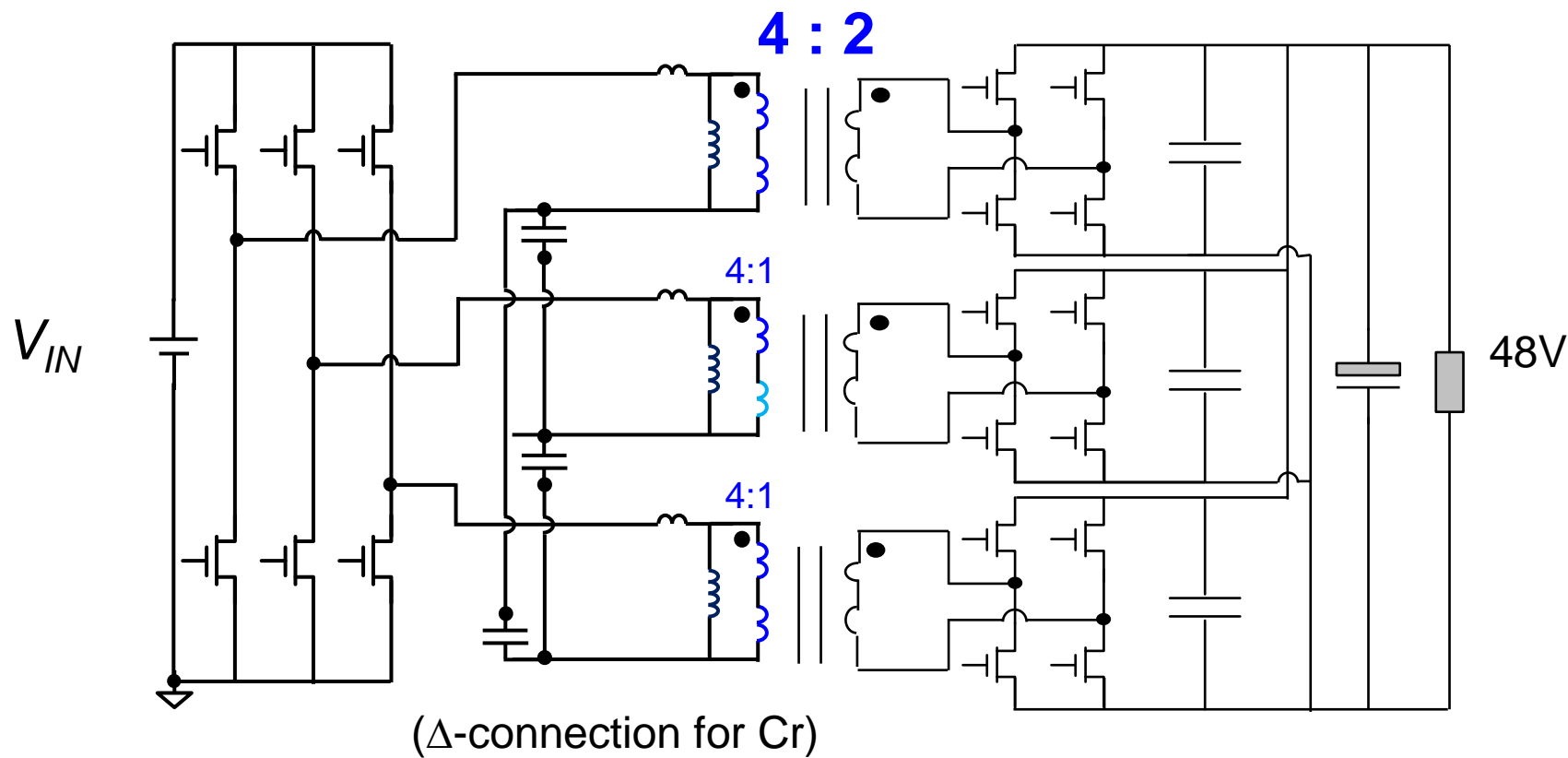



- Switching frequency 1MHz using GaN
- Shielding to reduce the CM noise

Integrated Magnetics (3L & 3T)

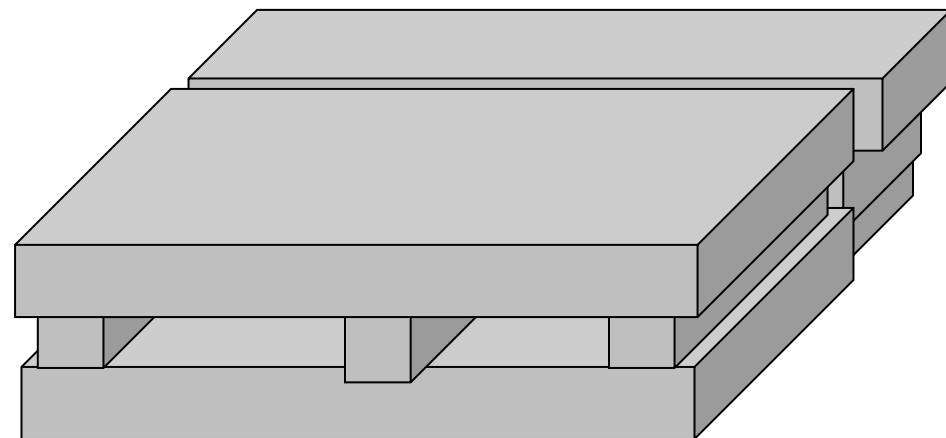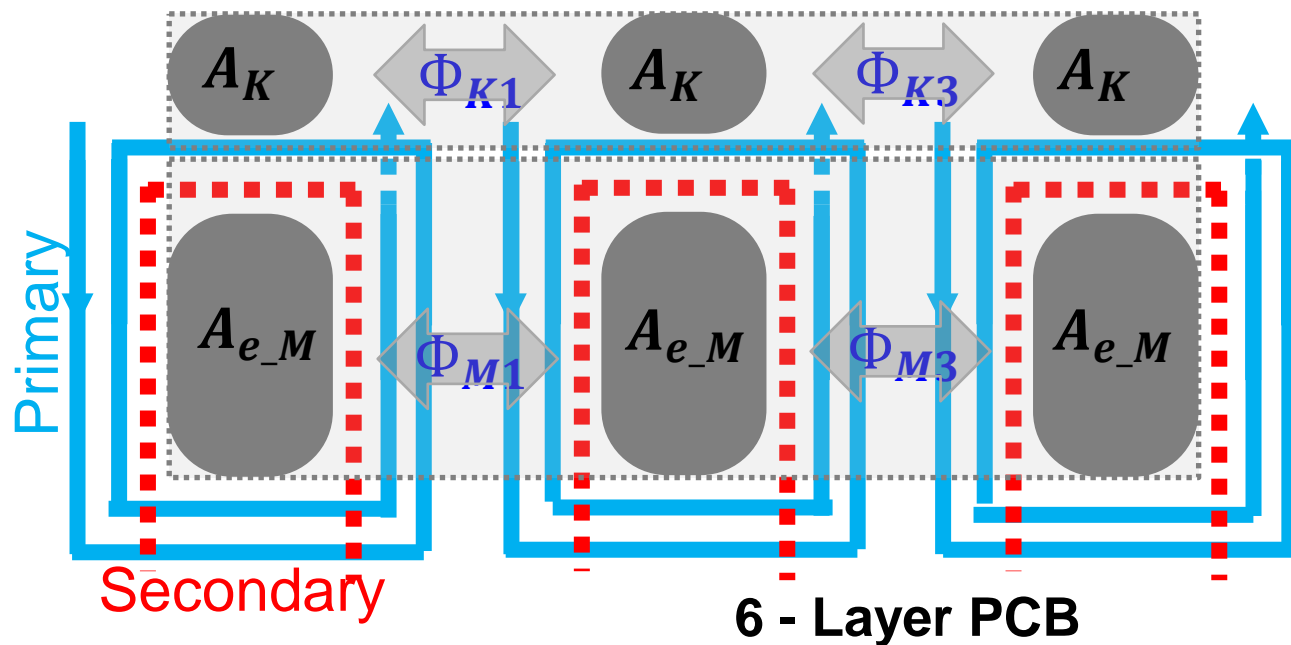

作者授权中国电源学会发布，未经作者同意禁止转载


Shielding for 3-phase LLC

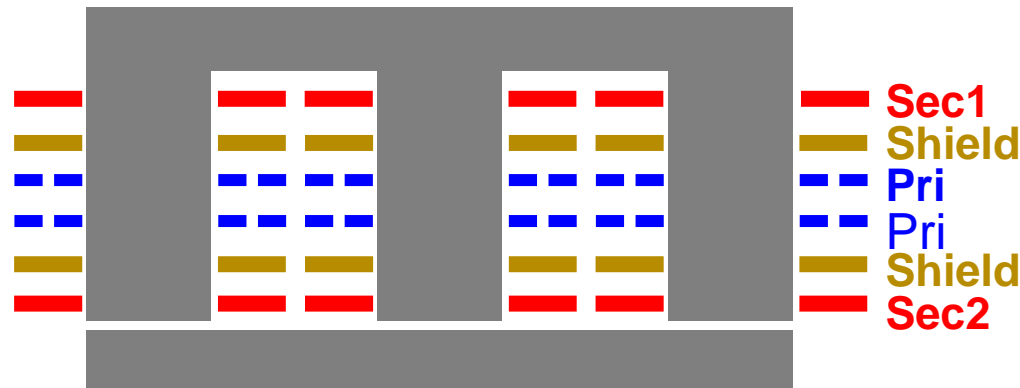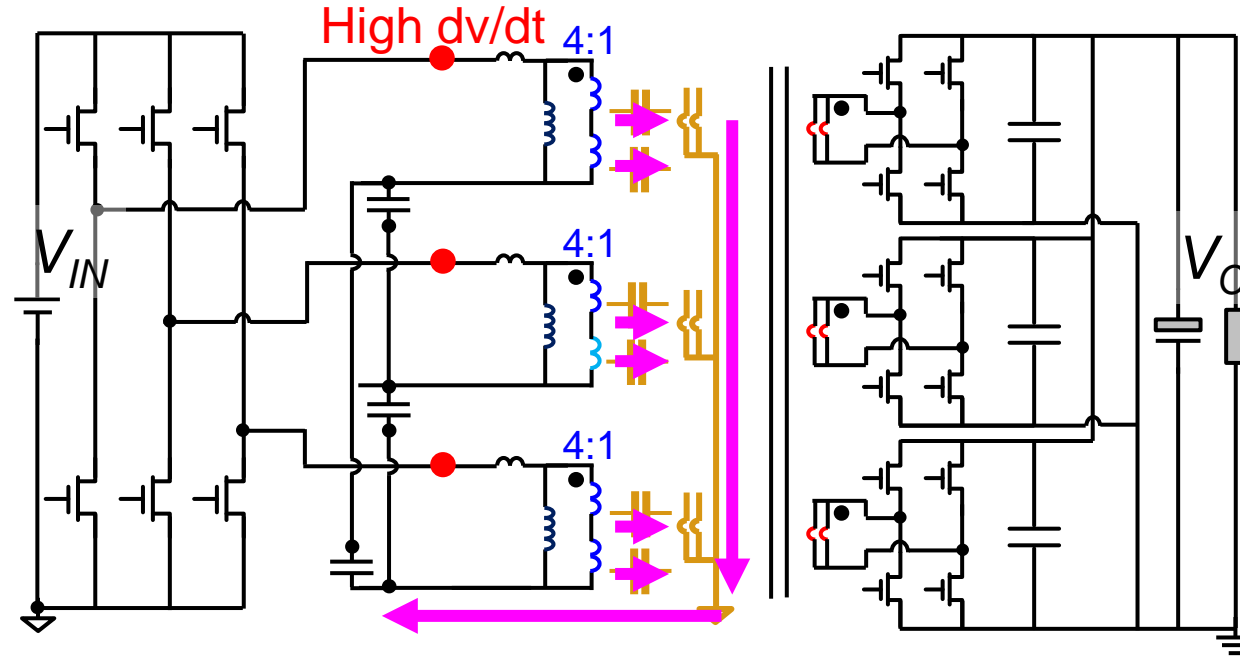


6-layer PCB

CM current flows to shielding and comes back to primary


Primary Y Secondary in Parallel

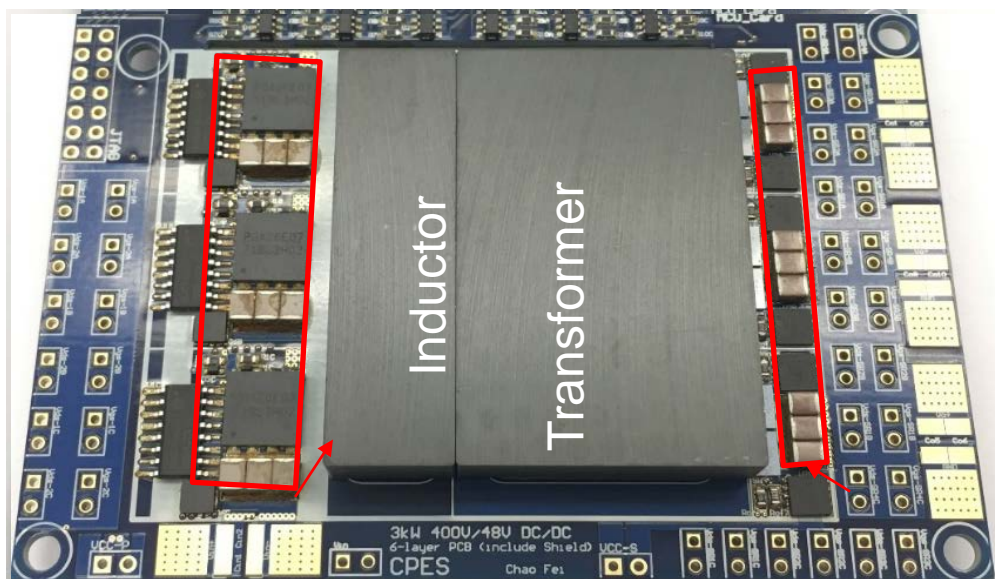

Power Density 600 W/in³

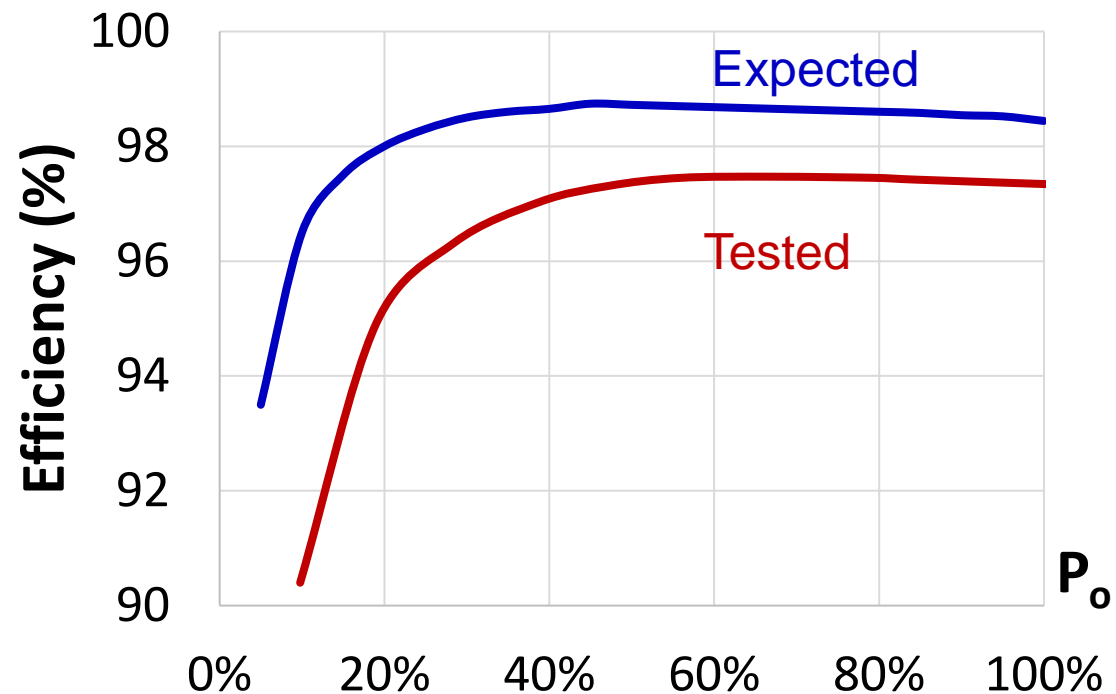

Improved Topologies


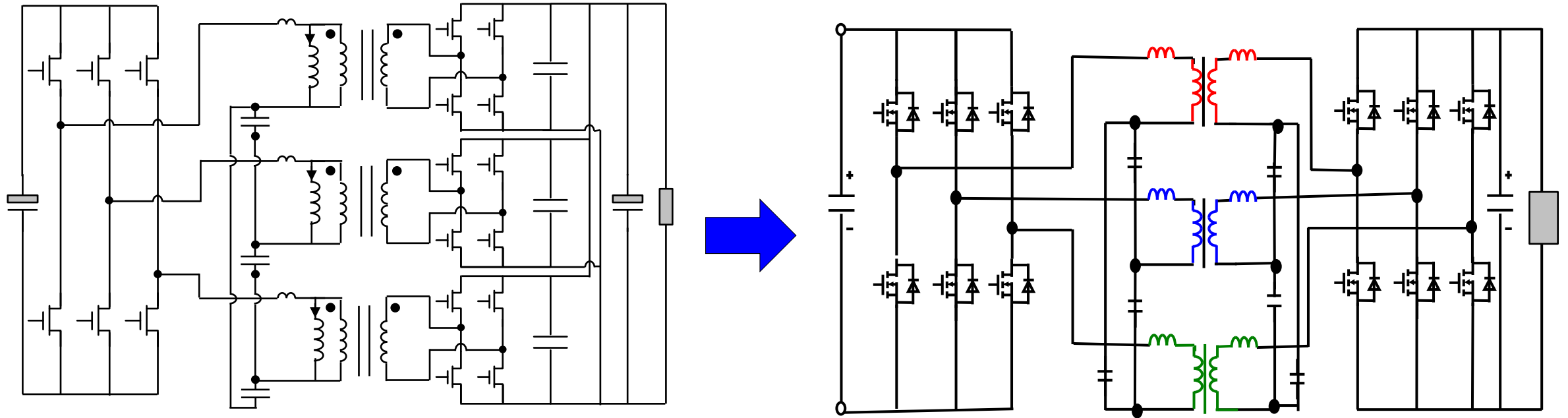


(Δ -connection for Cr)


Integration of 3 Transformers & 3 Inductors

作者授权中国电源学会发布，未经作者同意禁止转载


Single-Phase LLC Resonant Converter

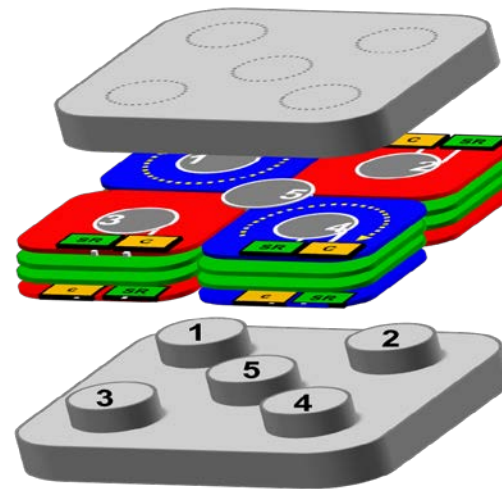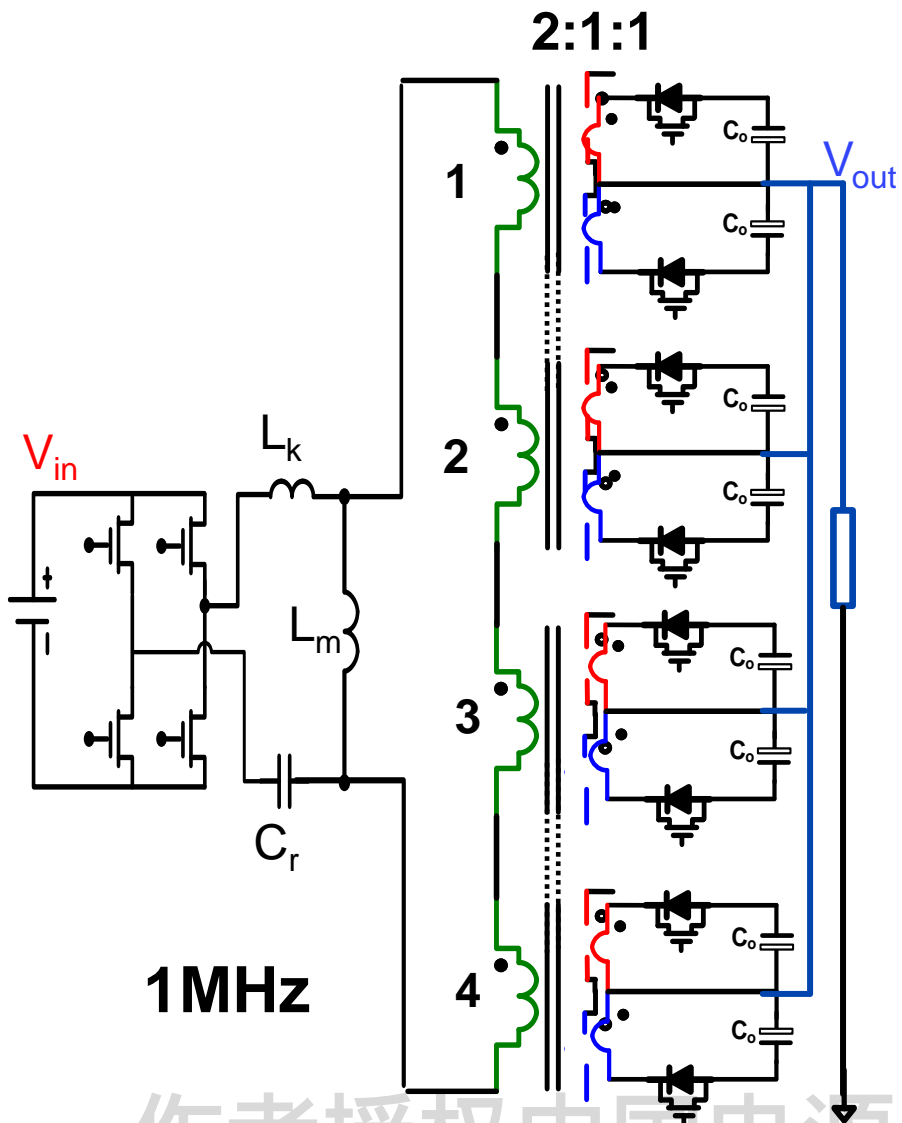


4 - Layer PCB

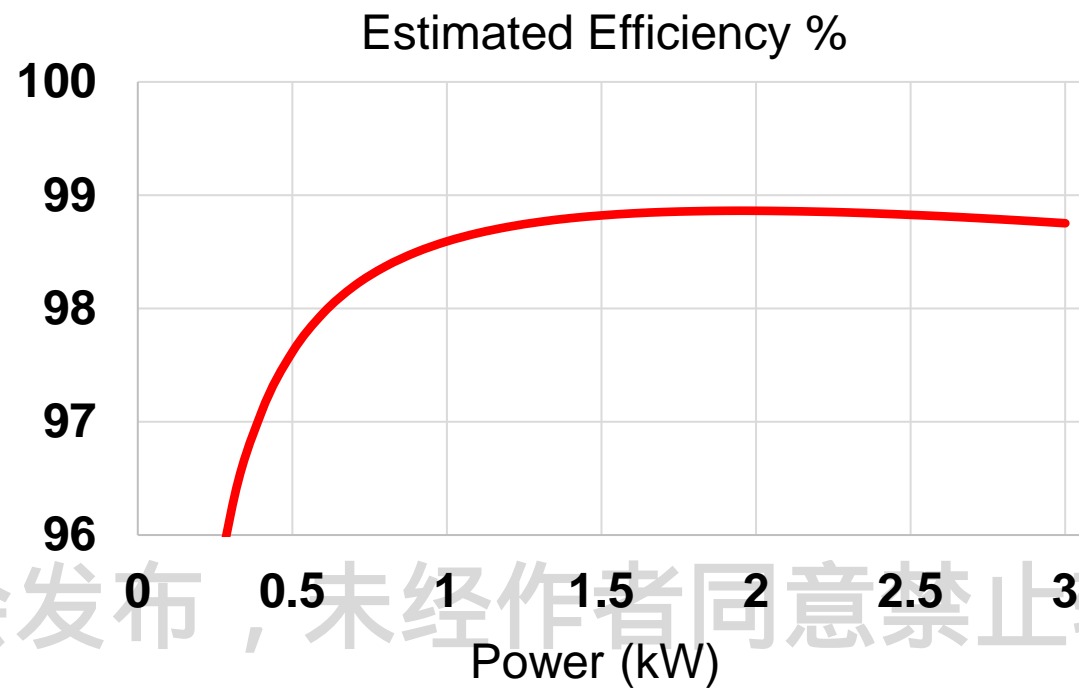


Next Generation Data Center

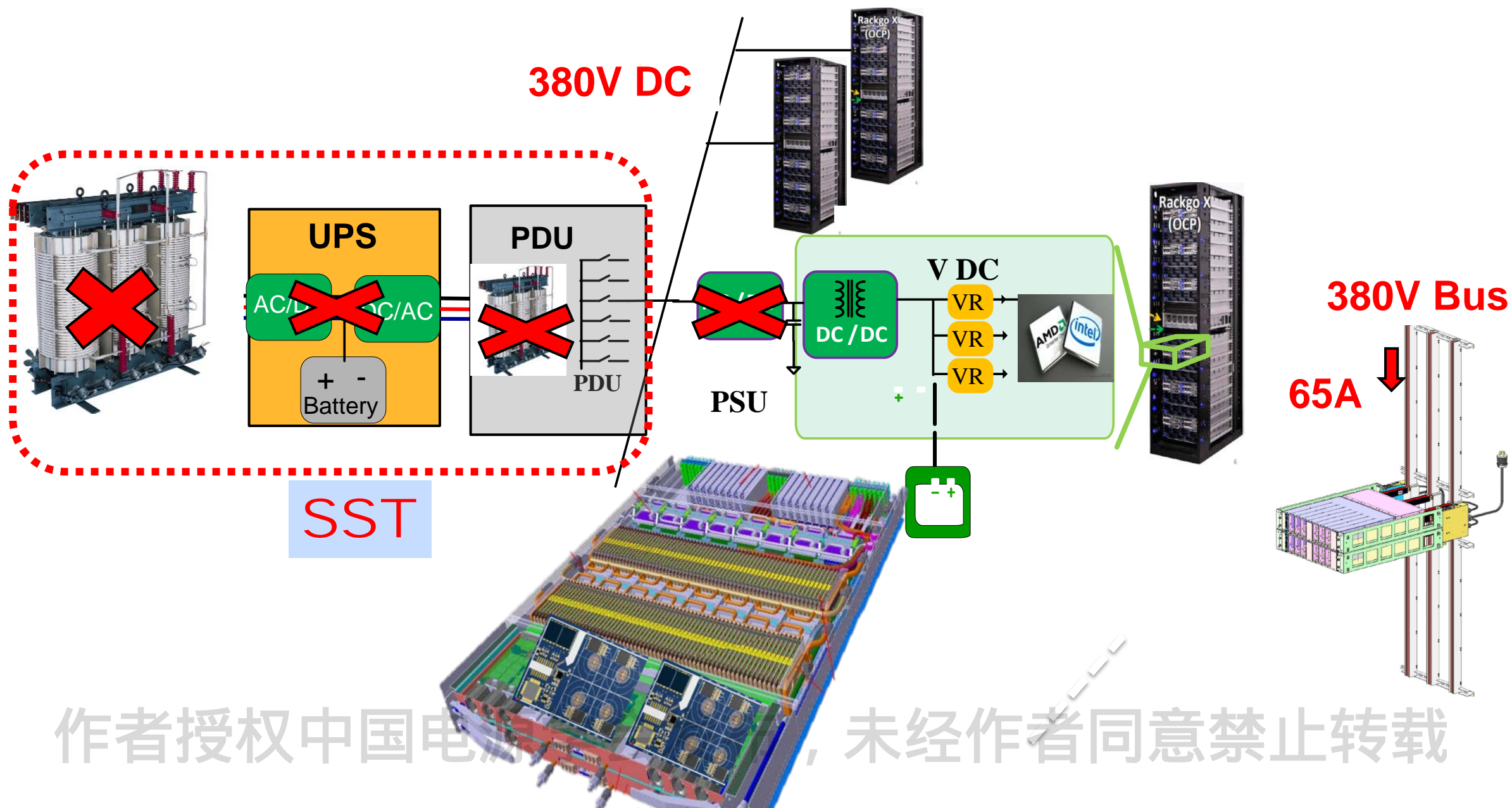


GaN Based Server Power Supplies

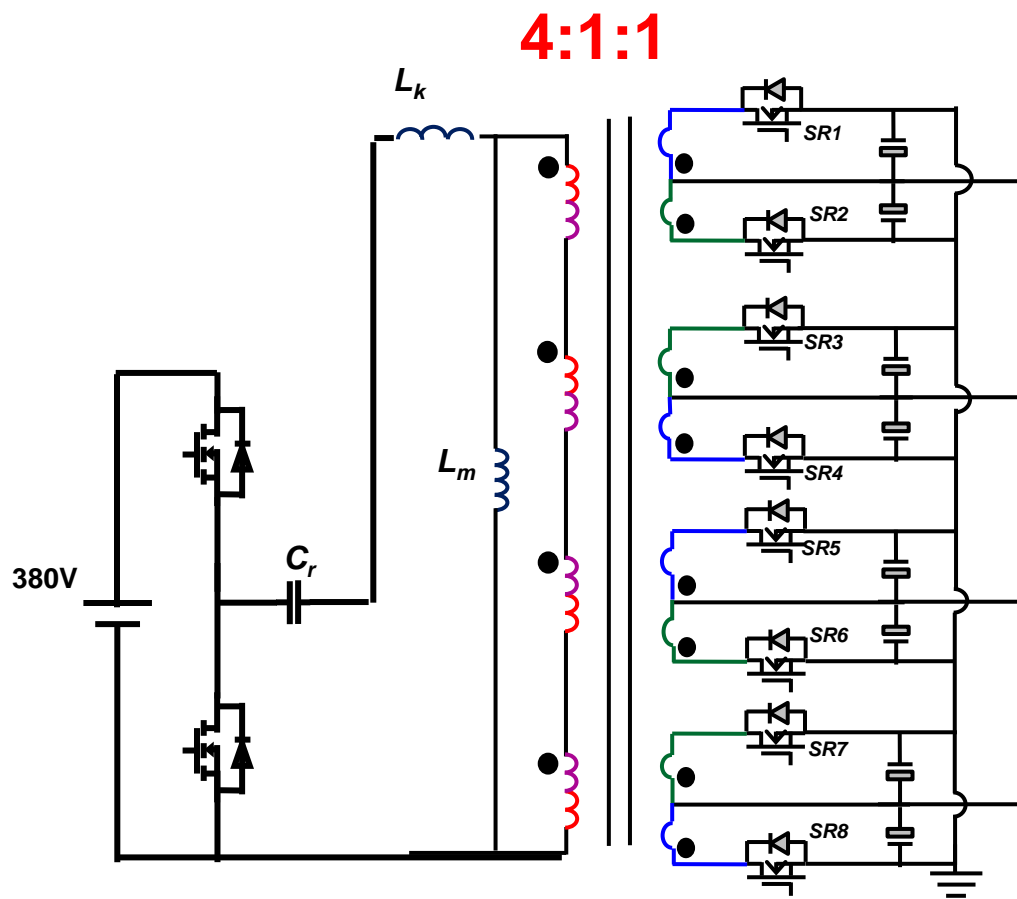

Primary windings

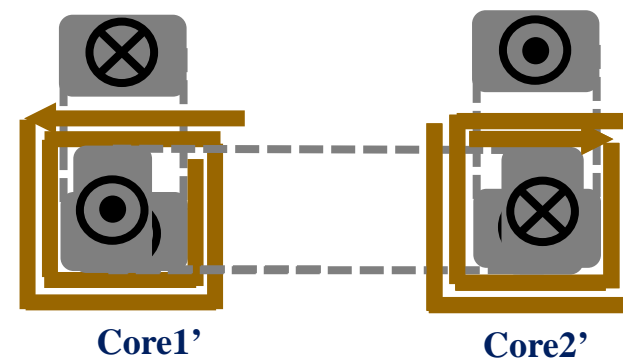



4:1:1

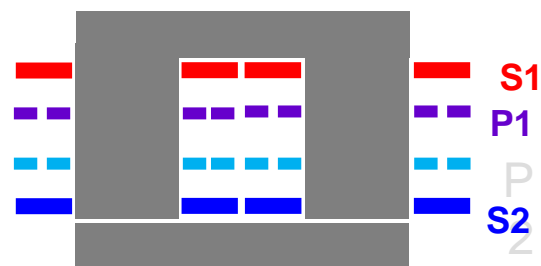



4 layers PCB

作者授权中国电源学会发布，未经作者同意禁止转载

Matrix Transformer

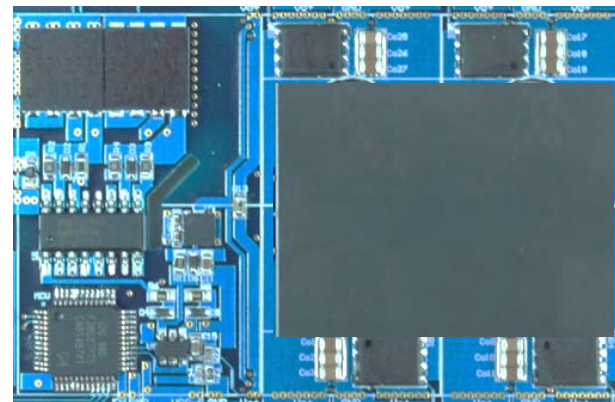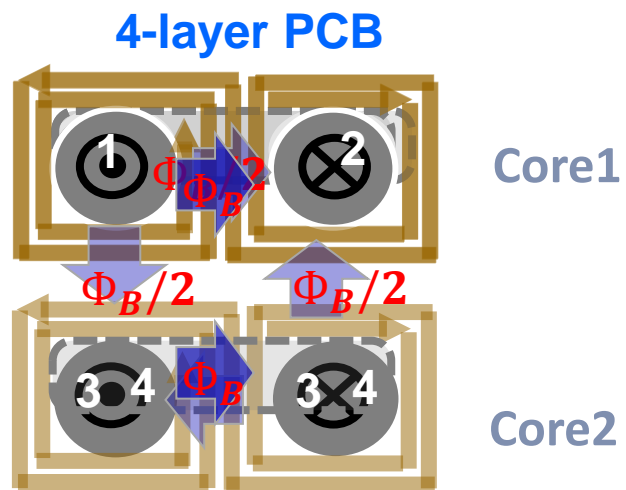

900W/in³

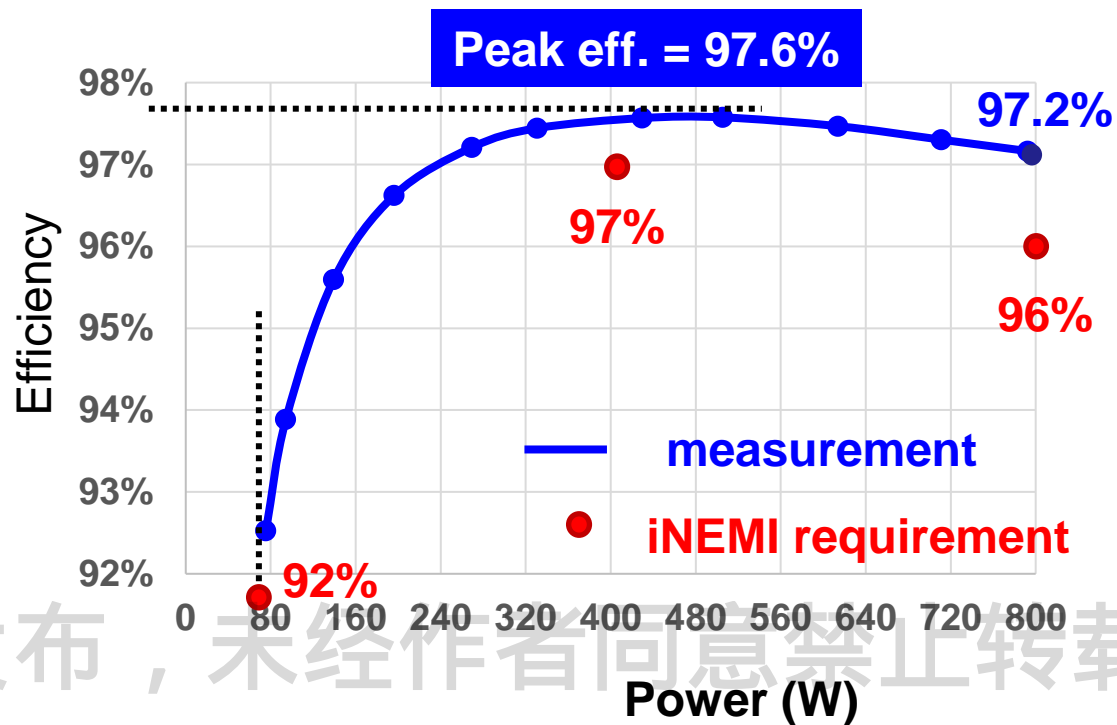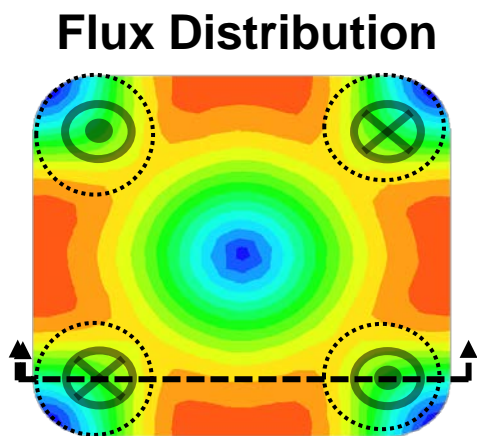

Generation 3 Data Center




13.8KV utility Service


Utility Service



13.8KV
3-Phase

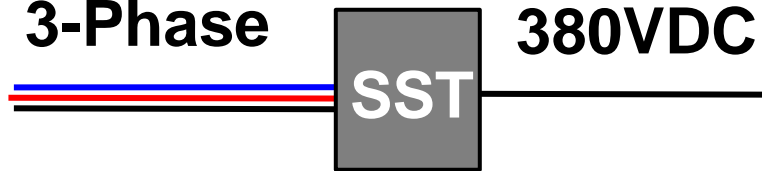

98%

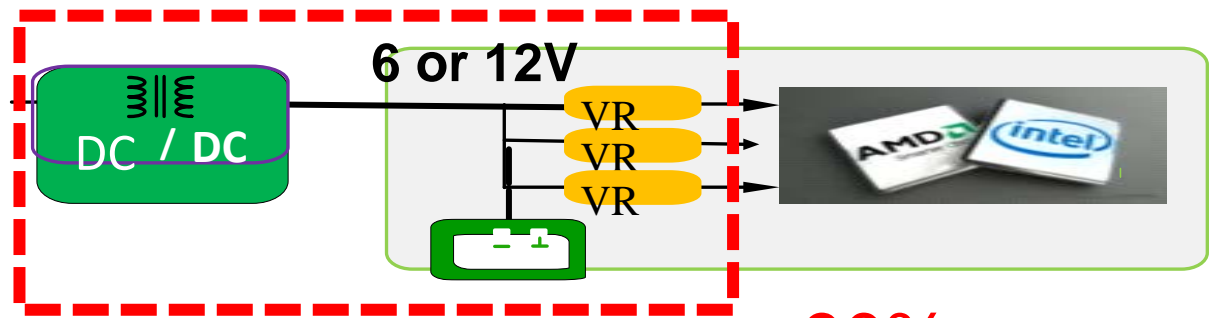

92%

90%


作者授权中国电源网发布 未经许可不得转载

Truly Modular and Scalable Data Center

Solid-State Transformer


13.8KVAC

380VDC

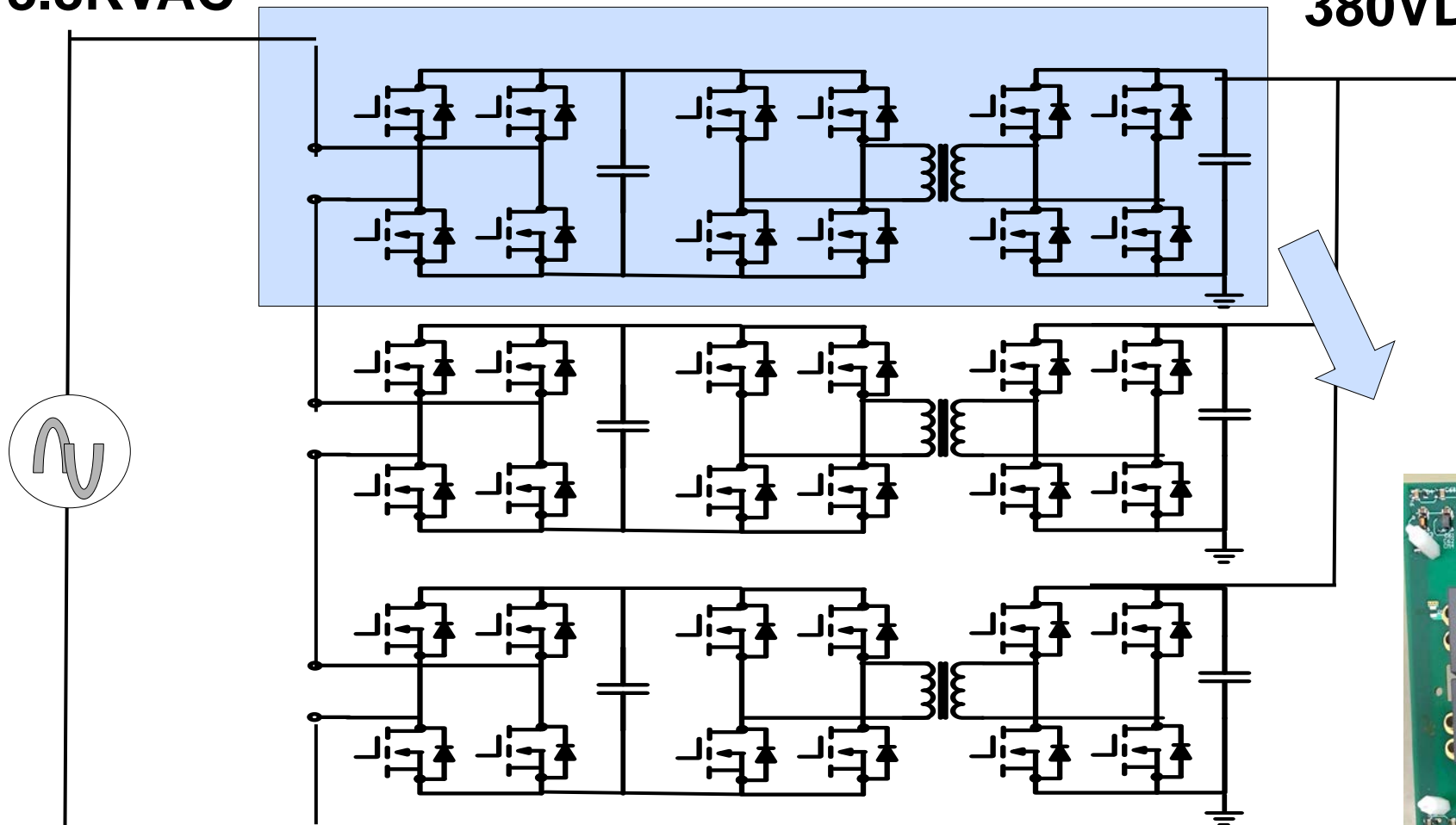

SST

200 KHz @ 98.5%

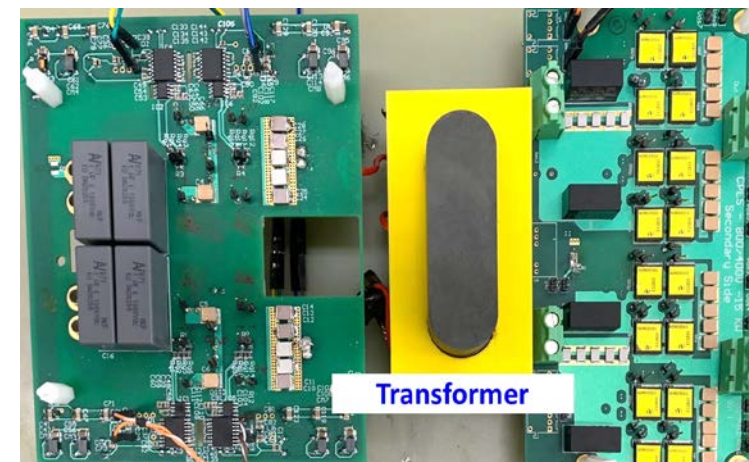

作者授权中国电源学会发布，未经作者同意禁止转载

Acknowledgement

CPES Research Collaborators

Professor Qiang Li
Dr. Xiucheng Huang
Dr Zhengyang Liu
Dr Yuchen Yang
Dr. Fei Chao
Dr Bin Li
Zhengrong Huang
Rimon Gadelrab
Ahmed Nabih

Thank You

作者授权中国电源学会发布，未经作者同意禁止转载