


High frequency ac-dc converter

Opportunities, Progress and Challenges in Piezoelectric-Based Power Electronics


Power Electronics and Applications Conference

Xiamen, China


6 November 2022

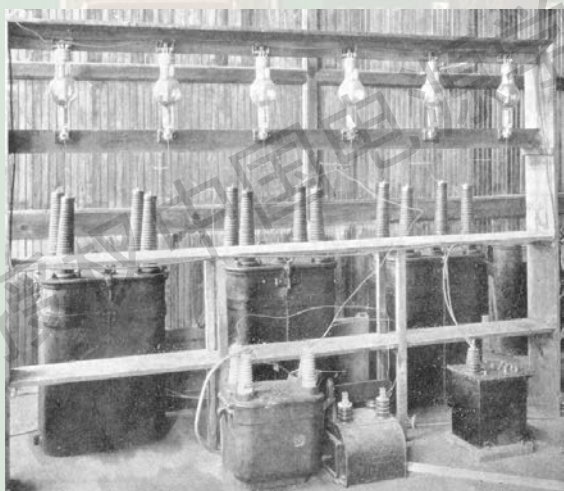

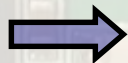20 kW Kenotron Rectifier, Circa 1926
(From Principles of Rectifier Circuits,
Prince and Vogdes, McGraw Hill 1927)



1 kW, 1 MHz, 380-12 V
Server Power Supply, Circa 2021
(Mike Ranjram, MIT)

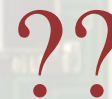


Circa 2030

■ Power electronics are an enabler for all kinds of systems



Efficient Lighting
(LED driver)

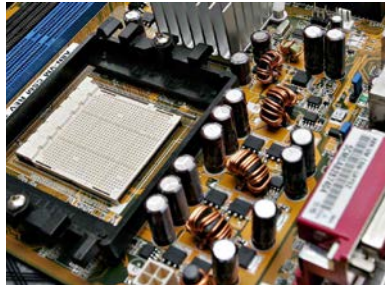

Computers
(Power Supply)



Transportation
(Inverter for Prius)




Renewable Energy
(Microinverter)

■ They can also be a bottleneck

■ Needs

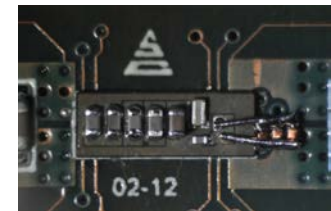- Miniaturization (smaller, lighter)
- Higher efficiency (converters *and* systems)
- Higher performance (better systems)



Mobile Devices
(Power management)

Continued advances in power electronics are important to our future



Passive Components Dominate



- **Passive components dominate size, weight and loss**
 - **Magnetics especially challenging**




- **Scaling laws work *against* miniaturization of power magnetics**
 - Simplified case: power handling (VA) of a fixed-frequency inductor
 - Flux density B_0 limited by core loss
 - Current density J_0 limited by winding loss
- **If we scale dimensions by factor α**
 - Areas scale as α^2
 - Volumes scale as α^3
 - Power handling as α^4 , *faster* than volume
- **Power *density* scales as α**
 - Gets worse at smaller size!

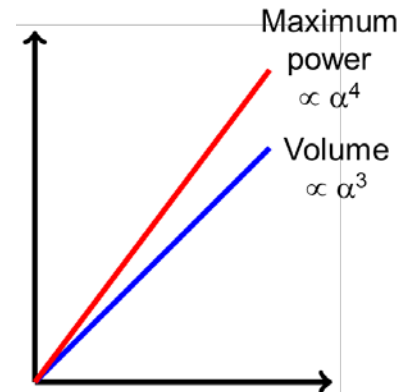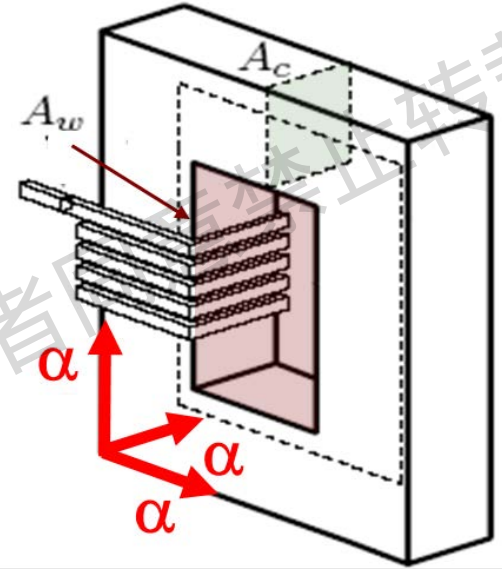


$$VA = V \cdot I \propto (NfB_0A_C) \cdot \left(\frac{J_0A_W}{N} \right) = f \cdot B_0 \cdot J_0 \cdot (A_C A_W)$$

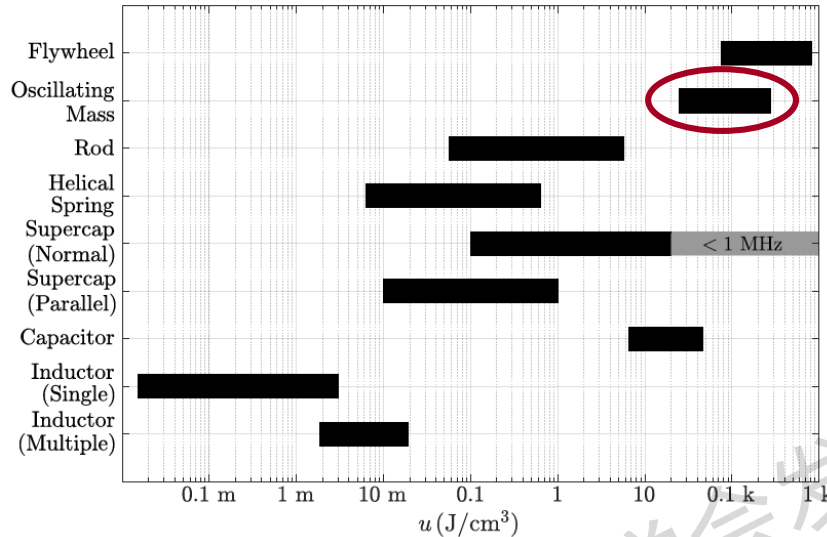Theoretical energy density @ 1 cm³ and 10 MHz



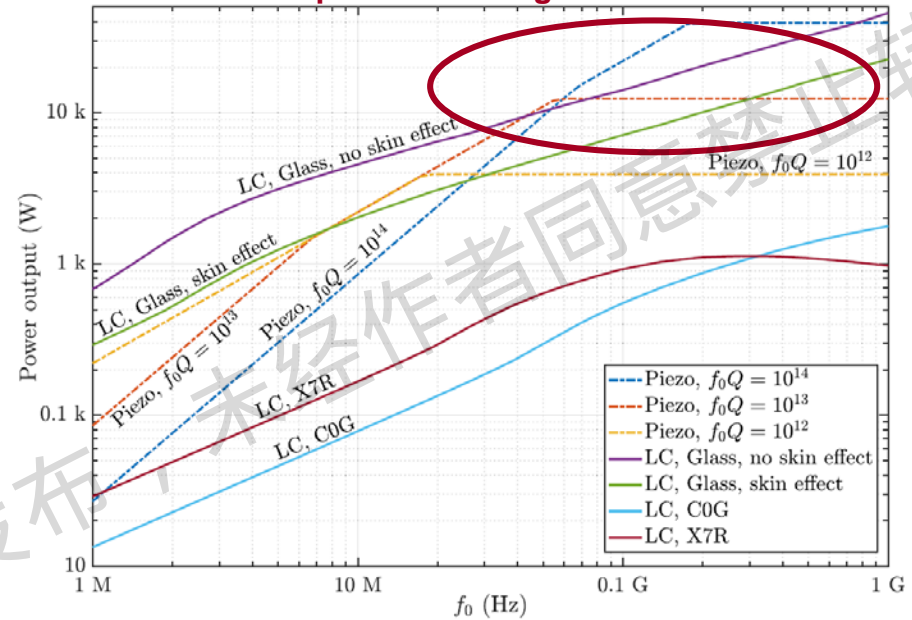Theoretical power handling @ 1 mm³ and 300 V



- Mechanical energy storage offers extremely high densities
- This can in principal be well leveraged through piezoelectric electromechanical systems


Piezoelectric & Inverse Piezoelectric Effects

Electric field and charge





Mechanical strain and stress

Butterworth-Van Dyke Model of PR

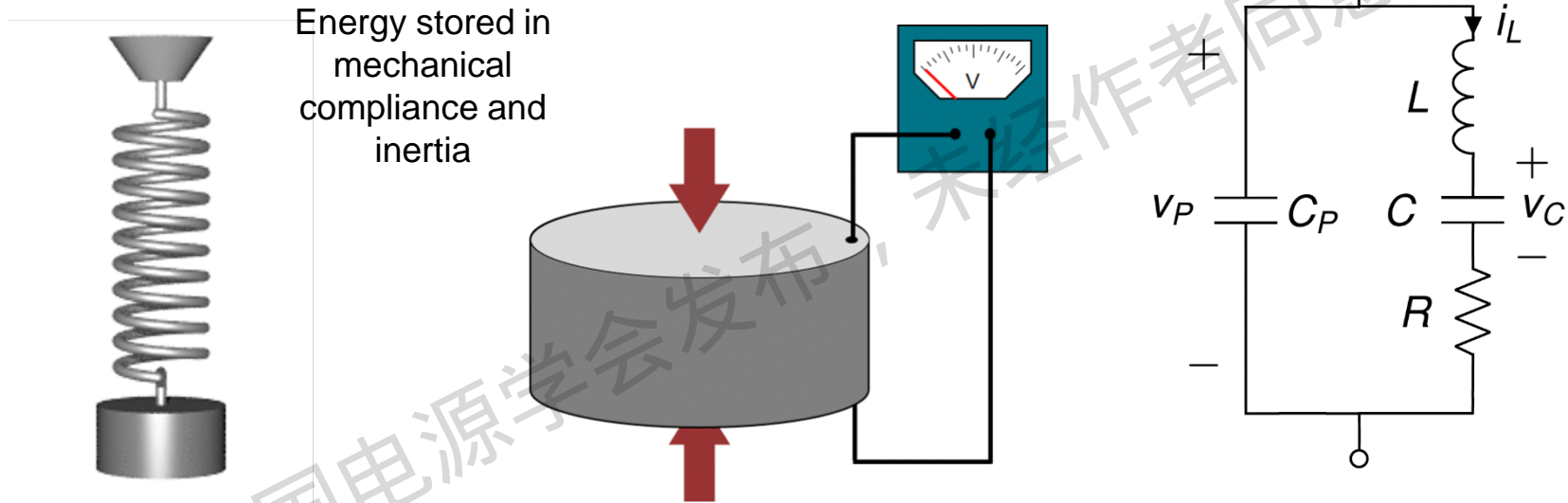

- Leverage *piezoelectrics*: transduce and store energy mechanically rather than magnetically
 - Can obtain (narrowband) inductive impedance characteristics
 - Potential for very high power density, better scaling to small size, improved fabrication

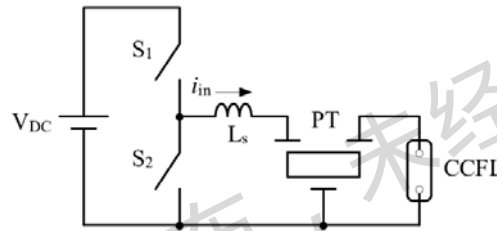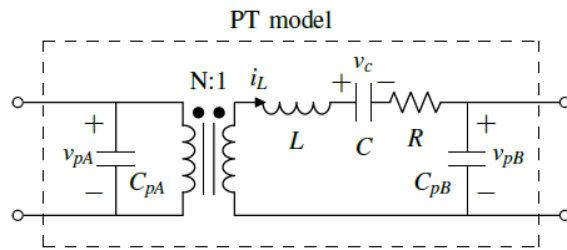- Piezoelectric transformers were historically used in CCFL drivers at high production volume
 - Designs still typically utilized magnetics



- Didn't transition to high-density, high-performance power electronics
 - Little understanding of suitable magnetics-free topologies, operating modes or control methods
 - Little understanding of material performance or selection criteria
 - Little understanding of resonator / transformer design and construction for high density

Recent research has started to address these limitations

■ What would we want in a converter based on a piezoelectric resonator?

■ No magnetic components


■ High-efficiency behaviors:

- Soft charging of the piezo
- Soft switching (ZVS) of all switches
- Minimum piezo energy storage

■ Practical characteristics:

- Wide voltage gain range
- Simple switch implementations

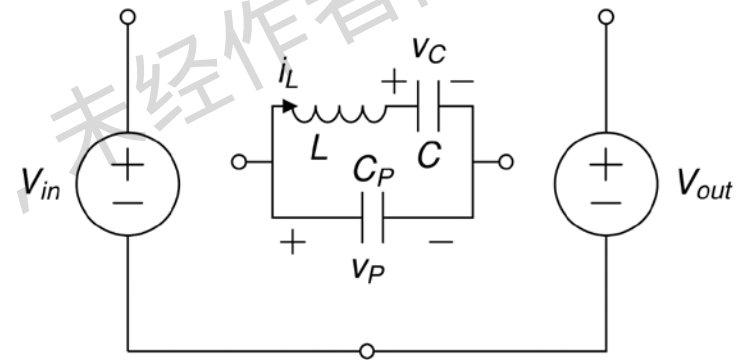
■ Choose operating sequence to achieve this



A High-Efficiency Sequence




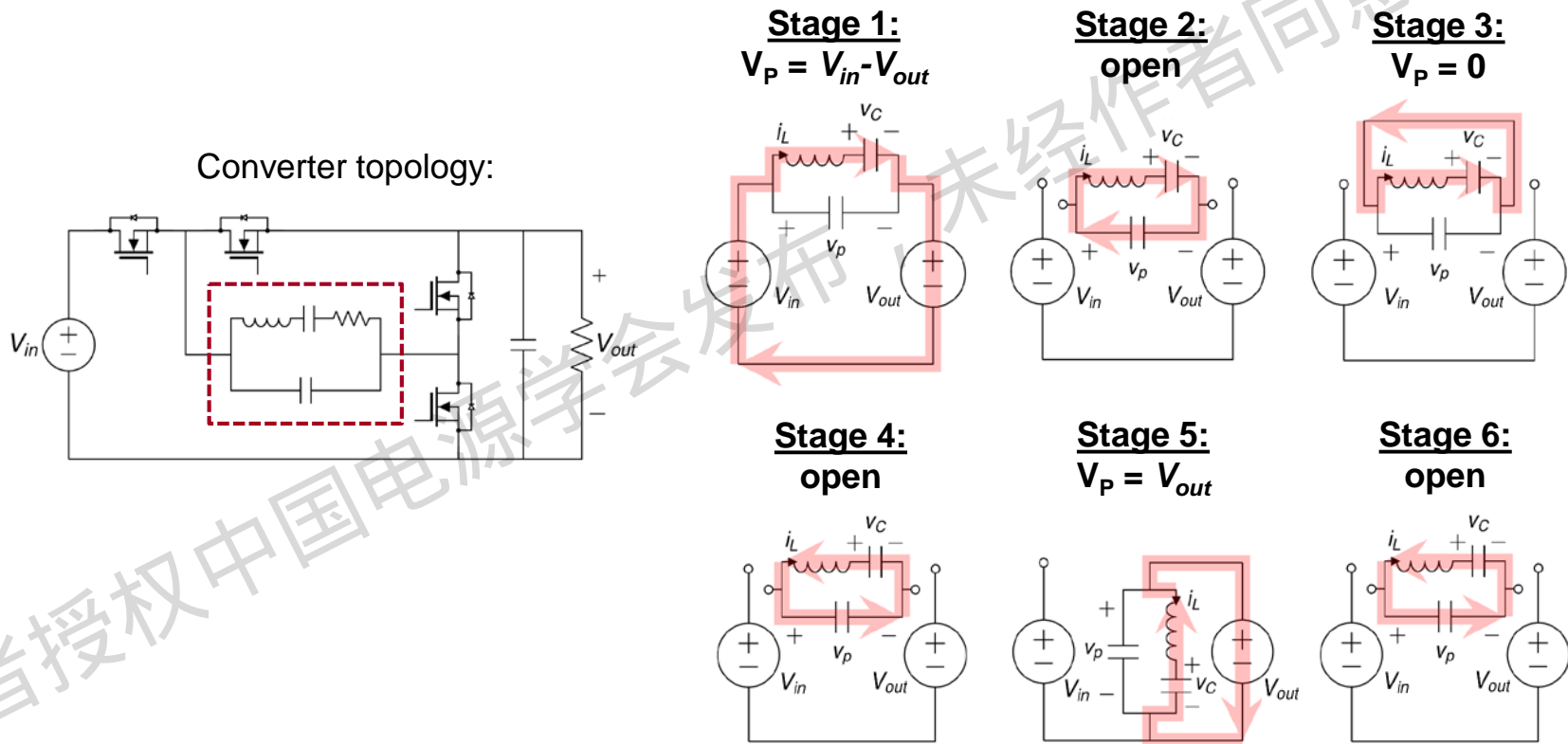- Consider the following 6-stage switching sequence and associated topology (“ $V_{in}-V_{out}$, Zero, V_{out} ”)
 - Alternate connected stages with open stages to soft-charge C_p




- We can achieve the desired high-efficiency behaviors!

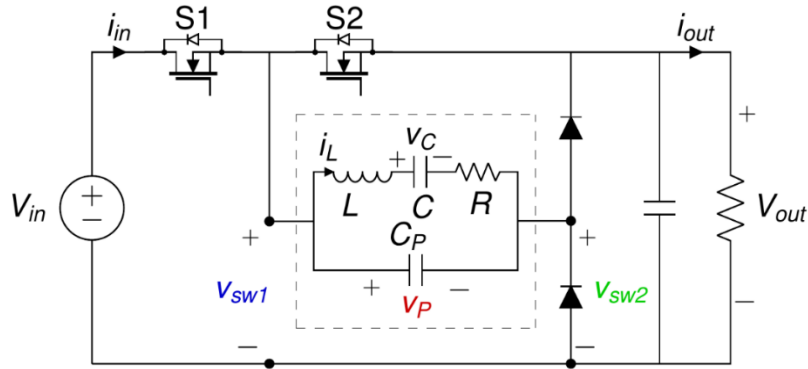
■ Experimental results validate predicted performance



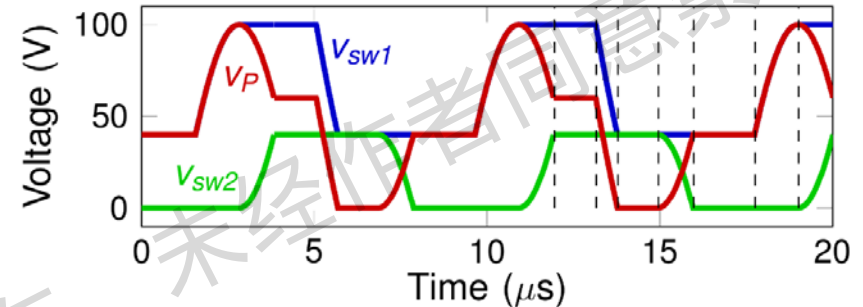
Simulation for $V_{in} = 100\text{ V}$, $V_{out} = 40\text{ V}$, $P_{out} = 6\text{ W}$



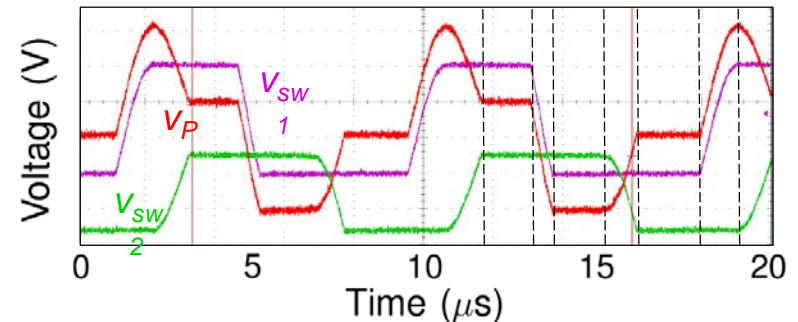
Experiment for $V_{in} = 100\text{ V}$, $V_{out} = 40\text{ V}$,
 $P_{out} = 6\text{ W}$, $\eta = 97.1\%$



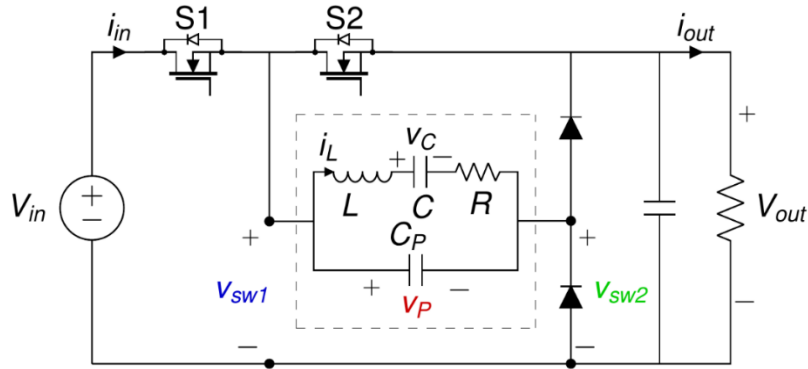
■ Can achieve high experimental efficiency





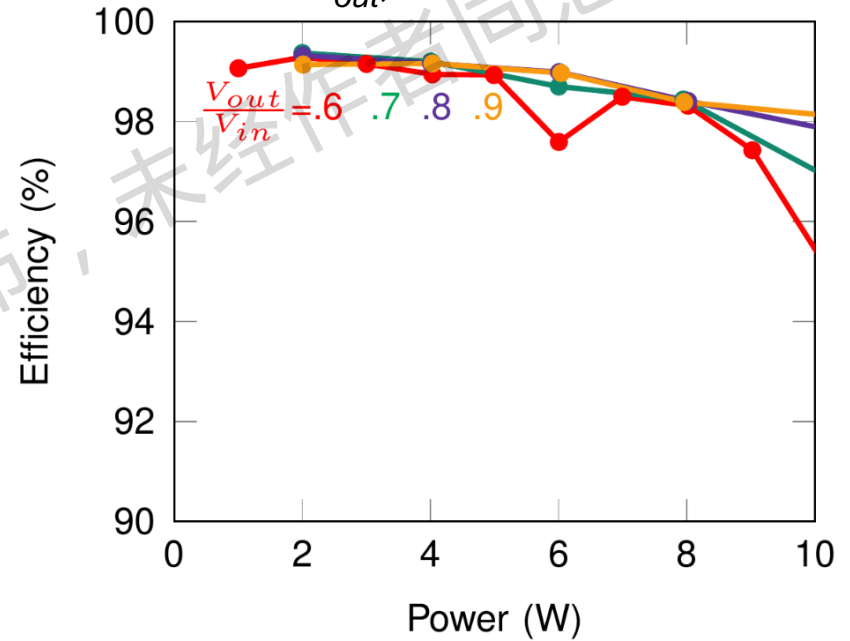
Experiment @ $V_{in} = 100$ V, varying V_{out} , ~ 114 kHz



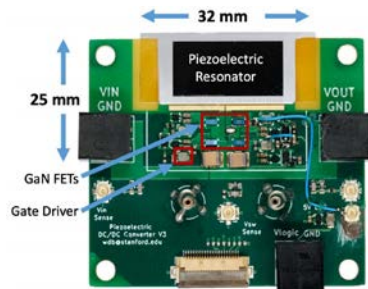- Other teams have also seen promising results with this sequence
 - Including operation at > 6 MHz



Active area

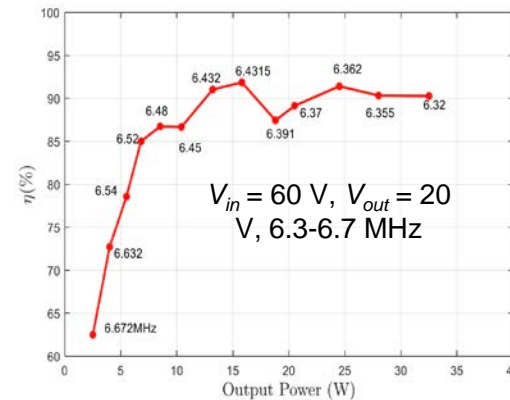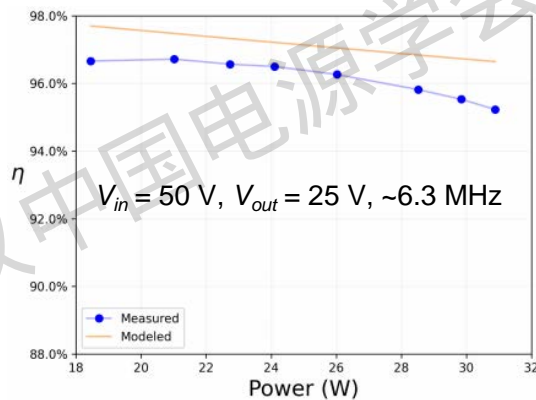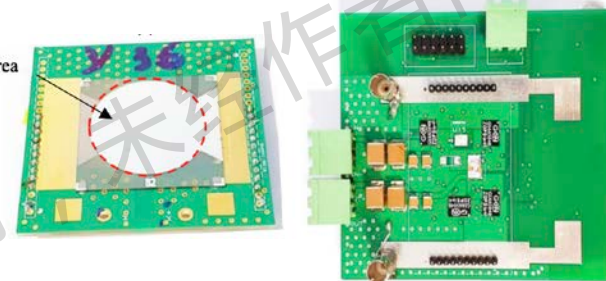

W. Braun et al., "Optimized resonators for piezoelectric power conversion," OJPE, 2021

M. Touhami et al., "Piezoelectric materials for the dc-dc converters based on piezoelectric resonators," COMPEL, Nov. 2021.

■ Identify high-efficiency switching sequences

□ Develop models that predict performance (e.g., efficiency)

Step-down:

Sequence	Range
$V_{in}, V_{in}-V_{out}, V_{out}$	$\frac{1}{2} < V_{out}/V_{in} < 1$
$V_{in}, \text{Zero}, V_{out}$	$0 < V_{out}/V_{in} < 1$
$V_{in}-V_{out}, \text{Zero}, V_{out}$	$0 < V_{out}/V_{in} < 1$
$V_{in}-V_{out}, -V_{out}, \text{Zero}$	$0 < V_{out}/V_{in} < 1$
$V_{in}, -V_{out}, \text{Zero}$	$0 < V_{out}/V_{in} < 1$


Step-up:

Sequence	Range
$V_{in}, V_{out}-V_{in}, V_{out}$	$1 < V_{out}/V_{in} < 2$
$V_{in}, \text{Zero}, V_{out}$	$1 < V_{out}/V_{in} < \infty$
$V_{in}, \text{Zero}, V_{out}-V_{in}$	$1 < V_{out}/V_{in} < \infty$
$V_{in}, V_{in}-V_{out}, \text{Zero}$	$1 < V_{out}/V_{in} < \infty$
$V_{in}, -V_{out}, \text{Zero}$	$1 < V_{out}/V_{in} < \infty$


$$\eta \approx \frac{P_{out}}{P_{out} + \frac{1}{2} I_L^2 R} \times 100\%$$

$$I_L = \frac{\pi}{2} f Q_{total} = \pi \left(\frac{P_{out}}{2KV_{out}} + f C_p \underline{V_{pp}} \right)$$

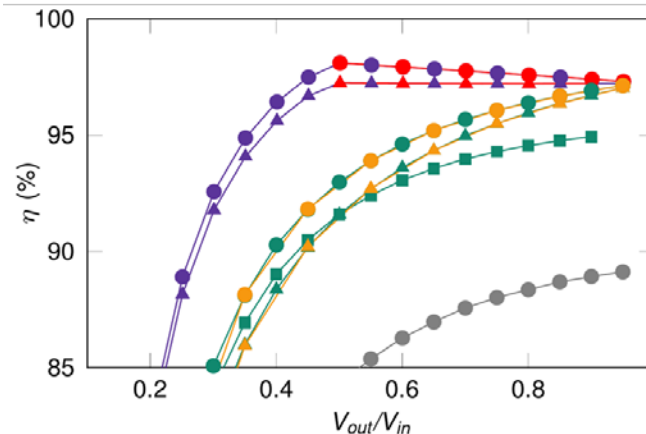
Expected piezo efficiency for $V_{in} = 100 \text{ V}$, $P_{out} = 10.0 \text{ W}$



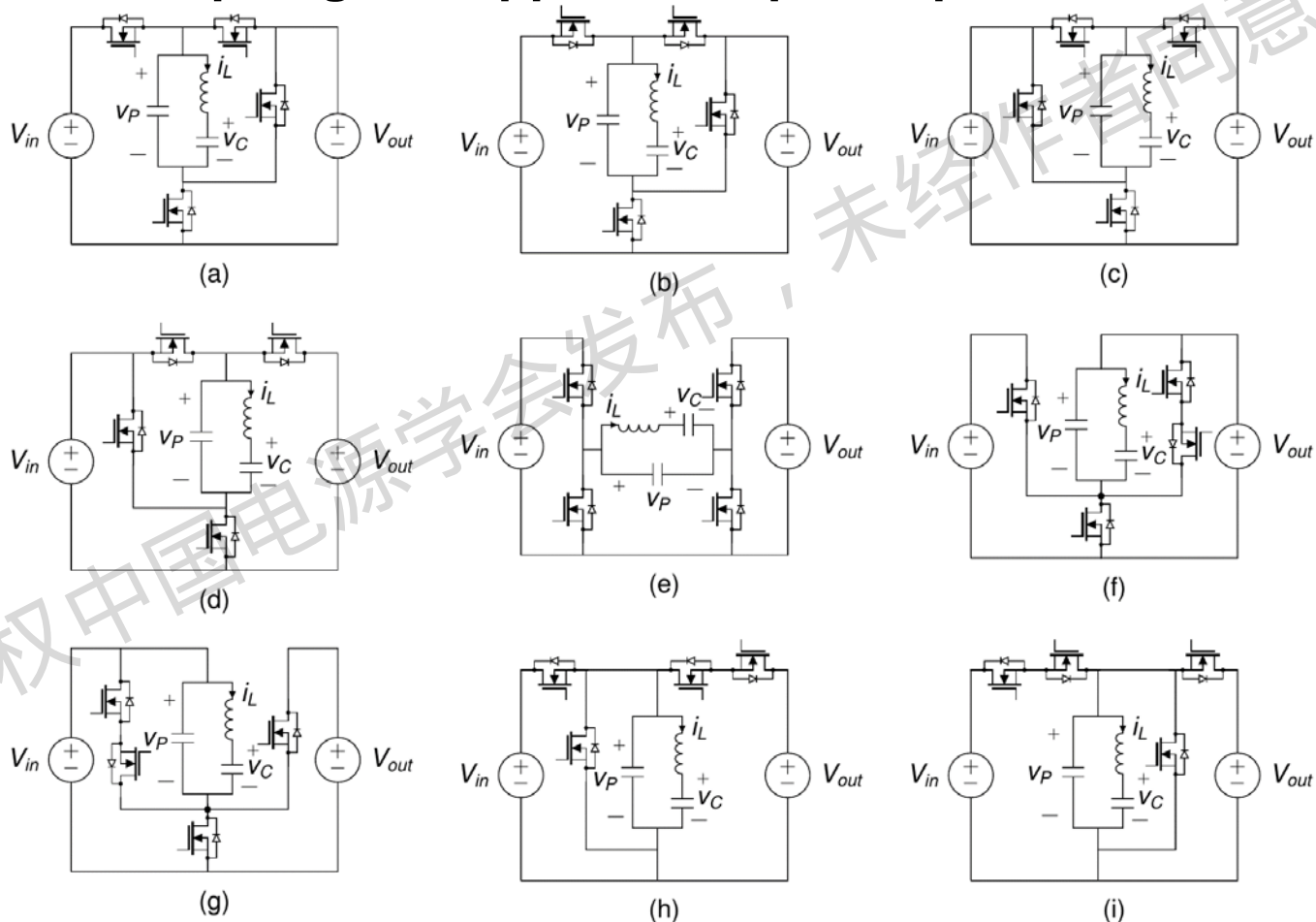
- Identify the *full set* of minimum-switch topologies with piezoelectric resonators for energy transfer
- Some topologies support multiple sequences



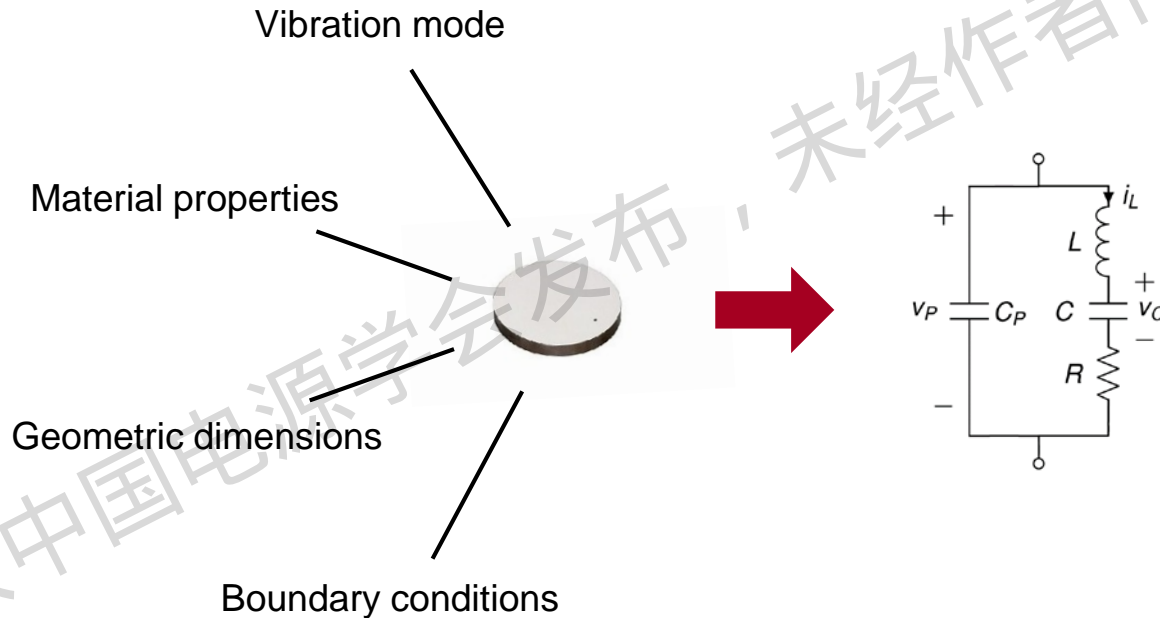
- How to best design piezoelectric components for power conversion is not straightforward



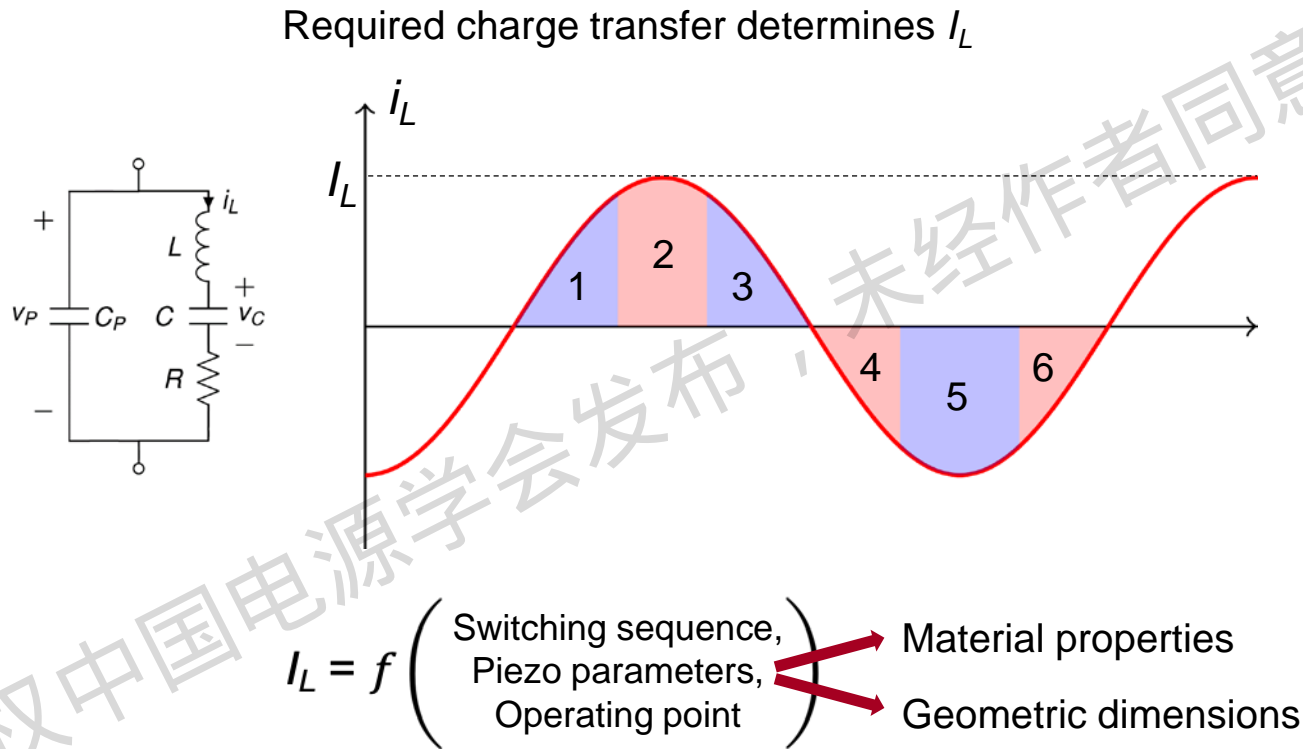■ We model PR behavior with “amplitude of resonance”



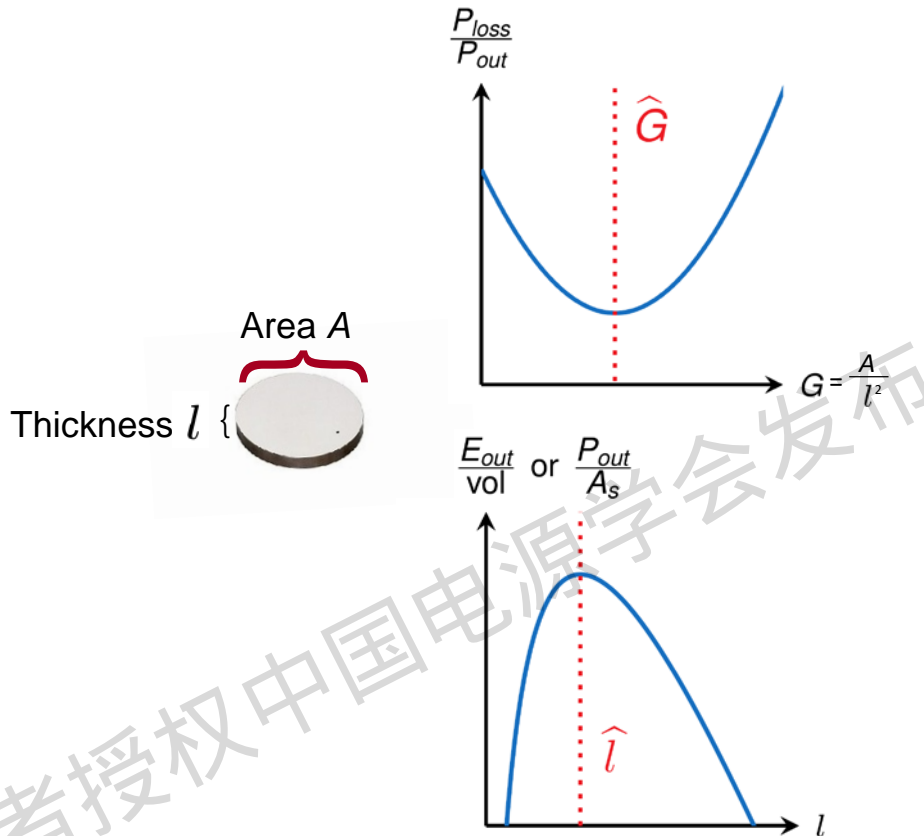■ Optimizing wrt geometry gives material FOMs



Minimum loss ratio:

$$\left(\frac{P_{loss}}{P_{out}}\right)_{min} = FOM_{Efficiency} = f(\text{material properties})$$


Maximum volumetric energy handling density:

$$\left(\frac{E_{out}}{vol}\right)_{max} = FOM_{Vol} = f(\text{material properties})$$

Maximum areal power density:

$$\left(\frac{P_{out}}{A_s}\right)_{max} = FOM_{Area} = f(\text{material properties})$$

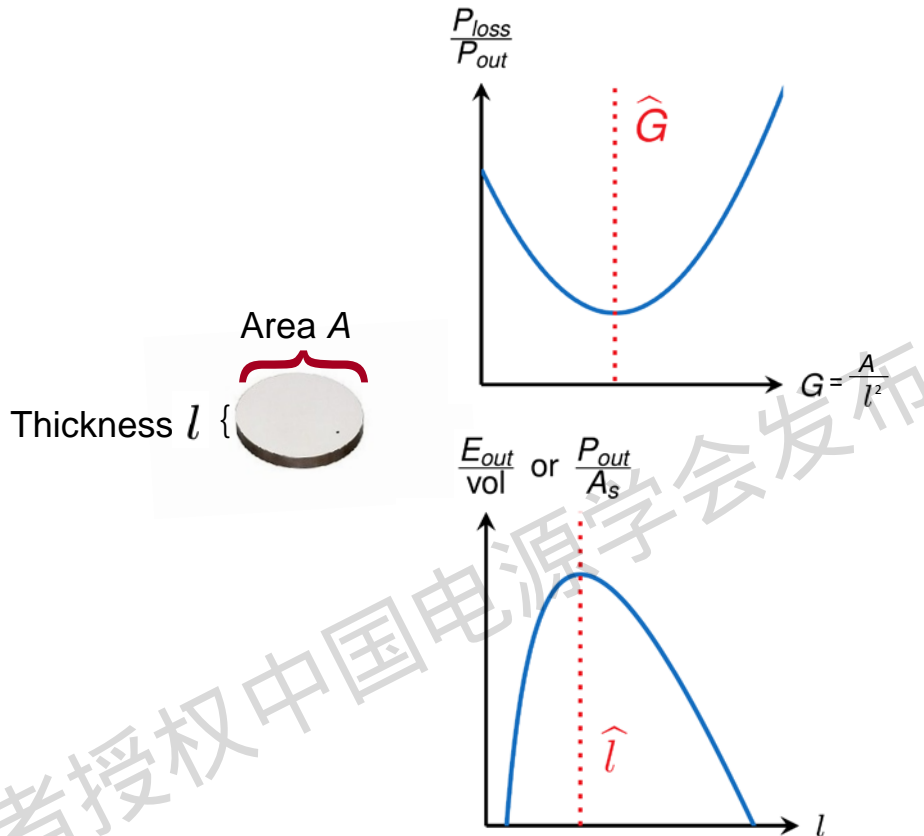■ Optimizing wrt geometry gives material FOMs



For thickness extensional mode:


$$FOM_M = \left(\frac{P_{loss}}{P_{out}} \right)_{\min}^{-1} = 4k_{33}^2 Q_m \frac{\pi + \gamma_0}{\pi^2 \gamma_0^2}$$

$$FOM_{APD} = \left(\frac{P_{out}}{A} \right)_{\max} = \frac{I_{Lmaxo}^2}{4\pi^2 \epsilon f_0}$$

$$\gamma_0 = \sqrt{\pi^2 - 8k_{33}^2} \quad I_{Lmaxo} \propto E_{max}, T_{max}, \delta_{max}$$

(material properties)

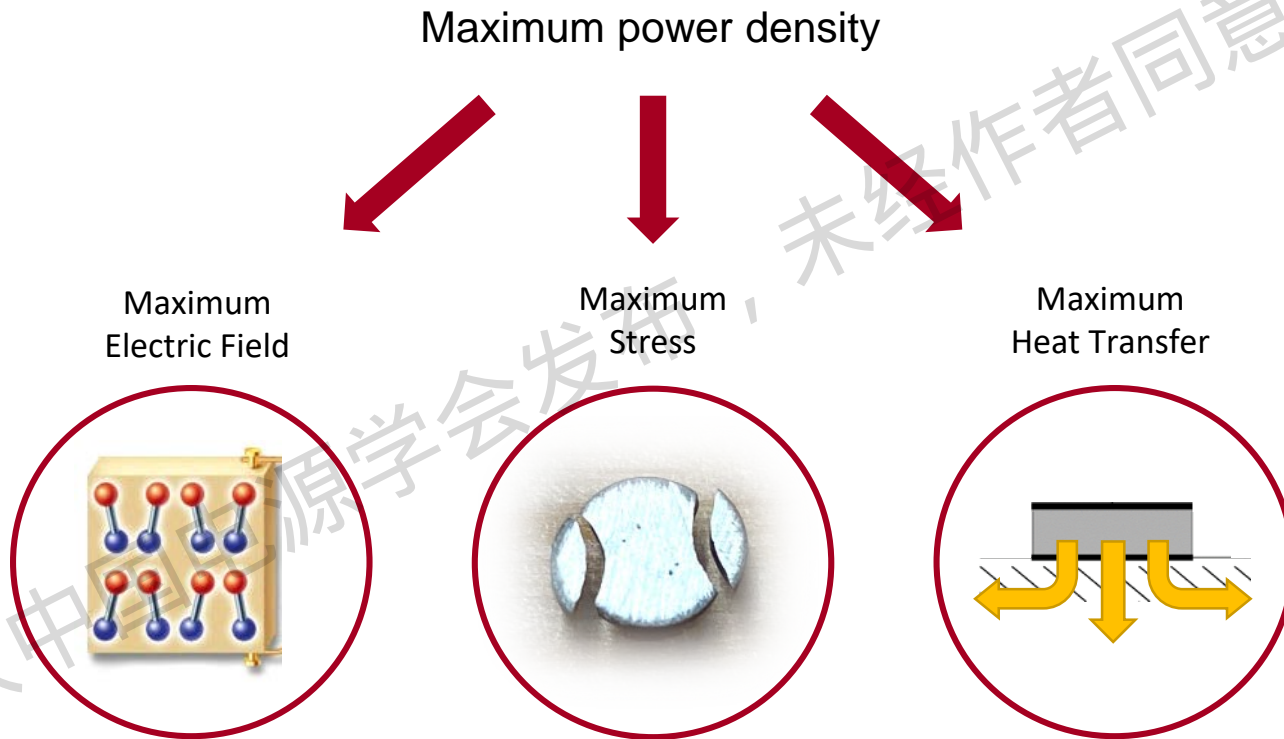
■ Power density is constrained by physical limits



Material Performance Evaluation Example

■ Performance varies widely among materials

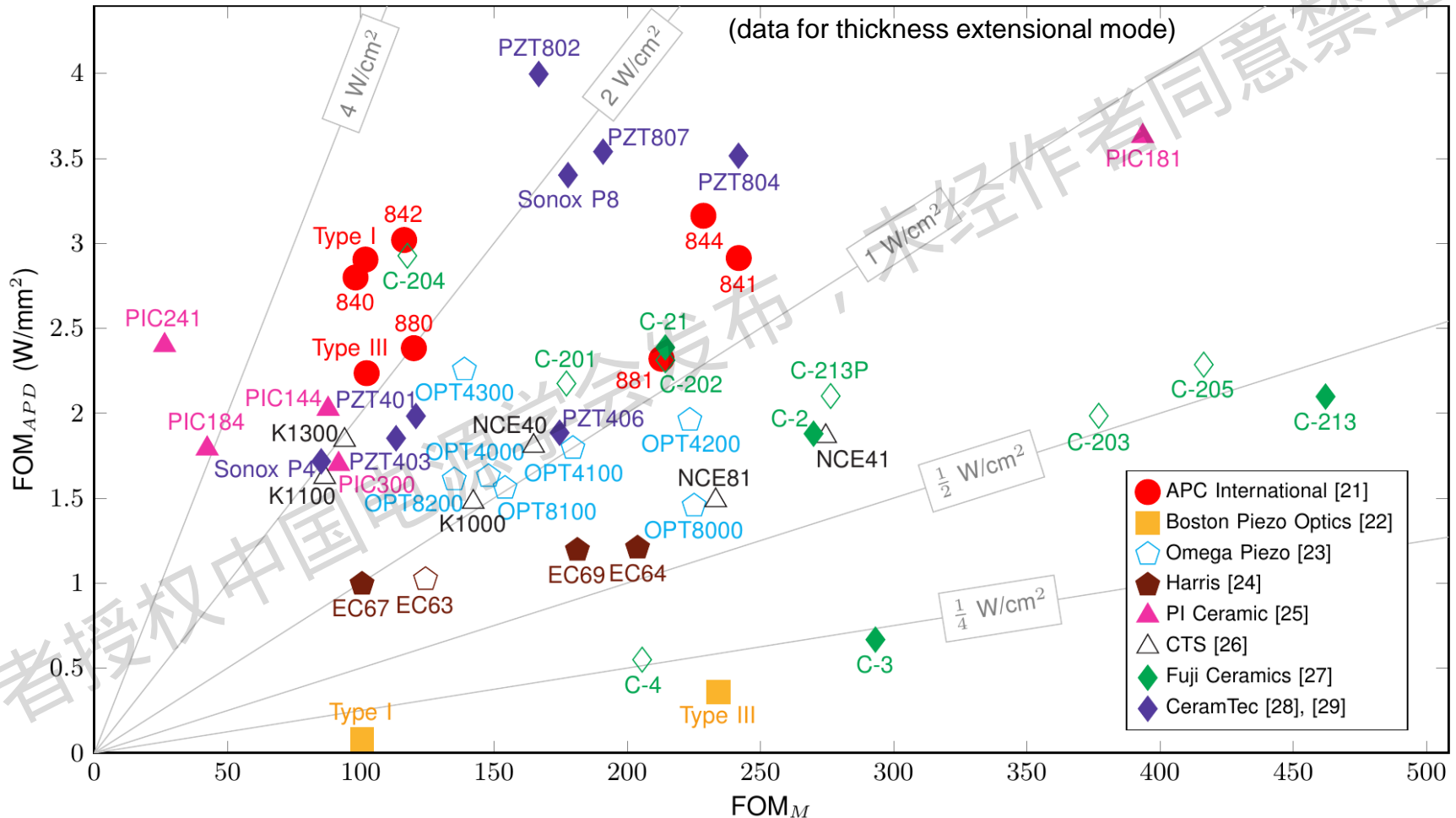
Power density vs. efficiency FOMs for 50 hard PZT materials



Material Performance Evaluation Example


■ Operation under limited heat transfer

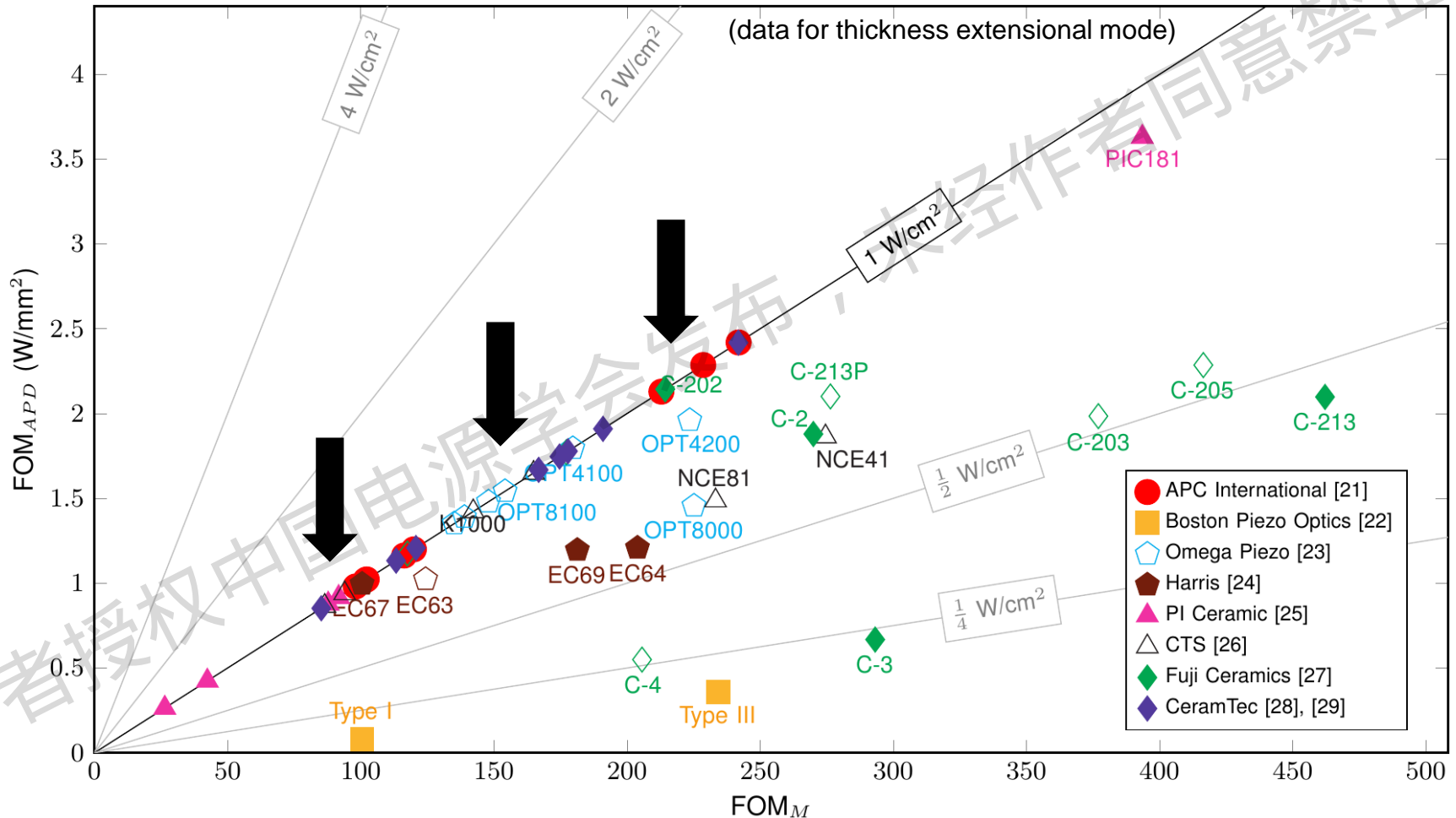Power density vs. efficiency FOMs for 50 hard PZT materials





■ Different vibration modes also vary in terms of FOMs

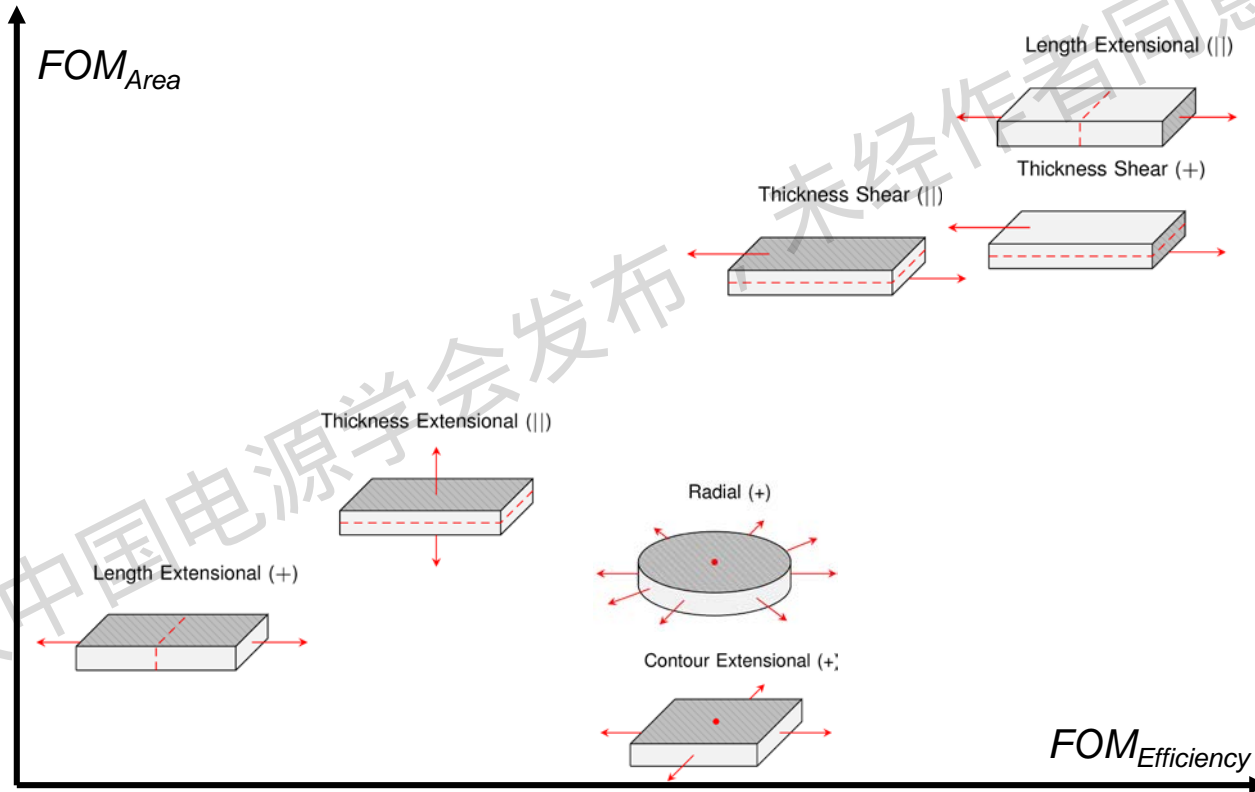Areal power density vs. efficiency FOMs for PZT



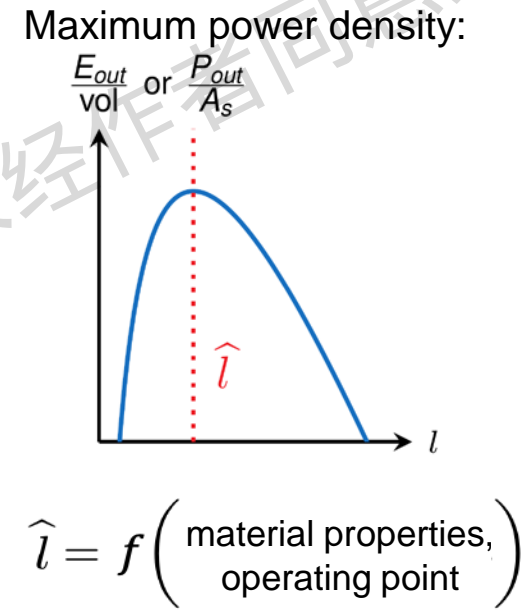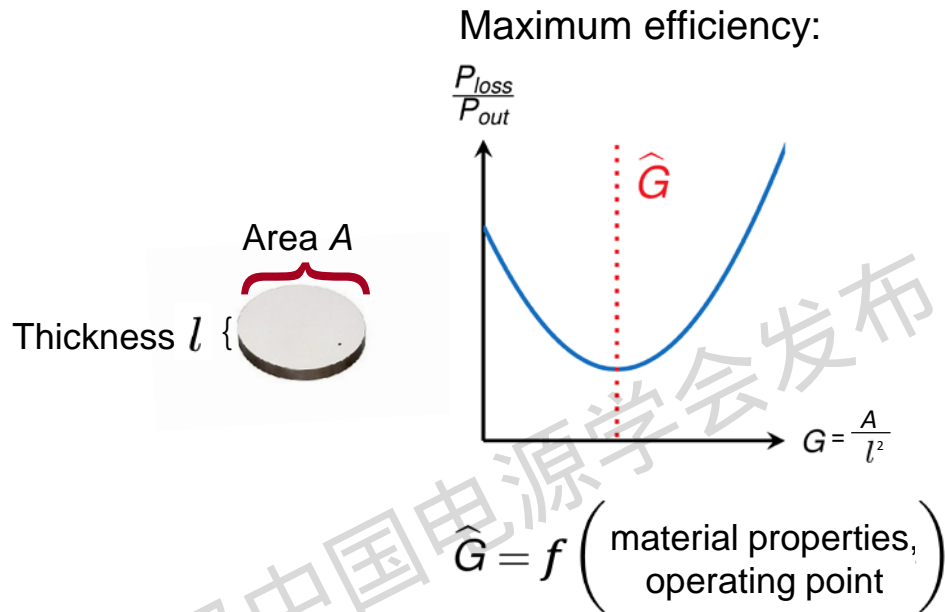- **FOM conditions provide PR geometry design criteria**
 - Can optimize resonator for *both* efficiency and power density!




(e.g., for thickness extensional mode)

$$\hat{G} = \left(\frac{A}{l^2}\right)_{min} = \frac{P_{out}}{V_{in}^2 \epsilon f_0}$$


$$\hat{l} = l_{max} = \frac{2\pi \epsilon f_0 V_{in}}{I_{Lmaxo}}$$

■ Combine emerging design knowledge


Switching Sequence

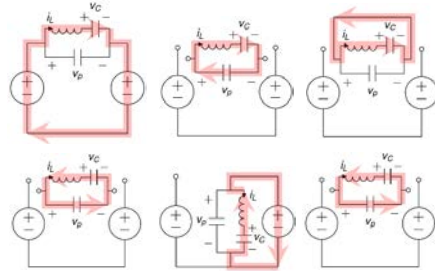


Piezoelectric Material

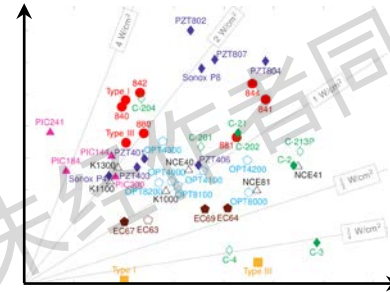

Circuit Topology

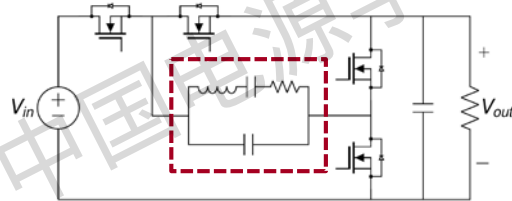

Vibration Mode




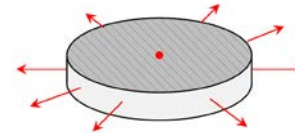


Geometry



- Achieves high performance with high power density
 - Step-down dc/dc converter at ~ 500 kHz
 - PR power handling > 1 kW/cm³ at low ΔT

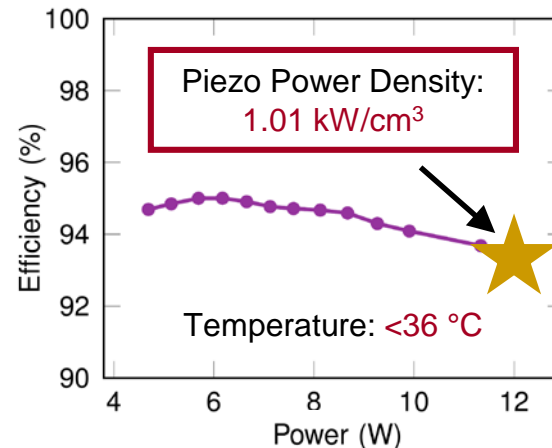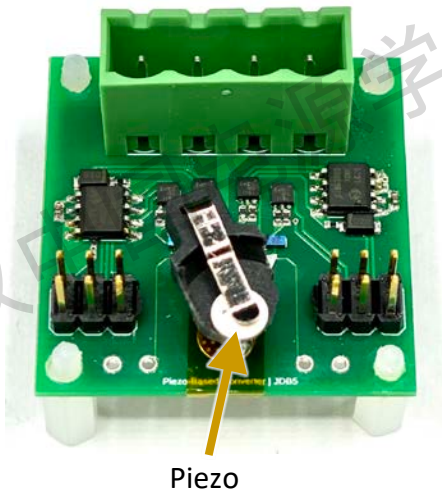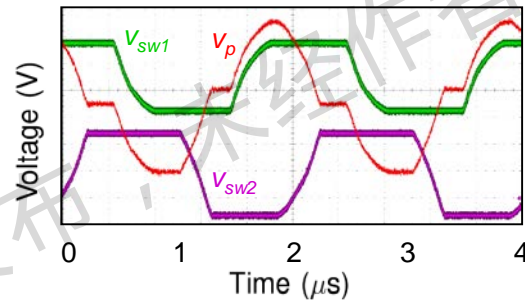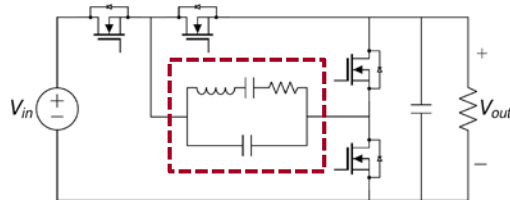
$V_{in} = 275 \text{ V}$, $V_{out} = 150 \text{ V}$, $P_{out} = 12 \text{ W}$, 493 kHz



■ Dramatic reduction in passive component volume compared to a magnetics-based design

□ Still much greater improvements possible

ZVS Resonant transition buck converter

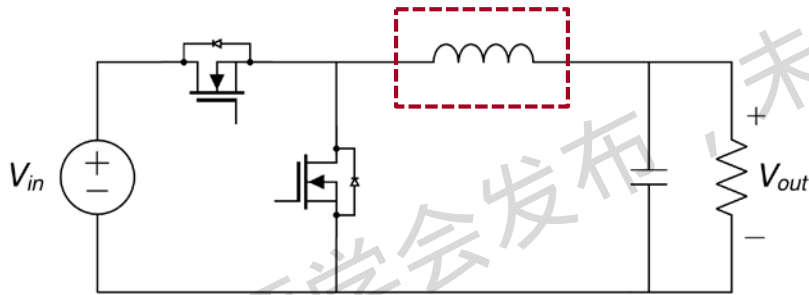


For the same...

- Operating point
- Frequency
- Design efficiency

Piezo design:
12 mm³



Inductor design:
171 mm³


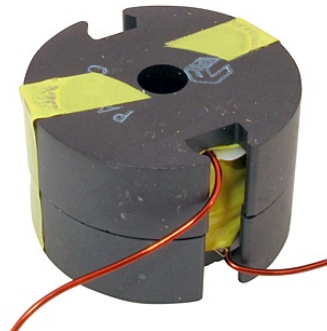


- **Recent results show great promise for piezoelectric-based conversion**
 - High efficiency, better scaling to small size, batch fabrication,...
- **But there are MANY unknowns to address:**
 - System design for wide operating ranges?
 - How to best design piezoelectric resonators and transformers for power conversion?
 - How can one *control* converters in closed loop to utilize the proposed operating modes?
 - Best techniques for packaging and integration?
 - ...
- **Many opportunities for major advances**



We're only just beginning to answer these questions

■ e.g., how to best design for large conversion ratios, wide operating ranges

Circuit Design and Control Strategies:

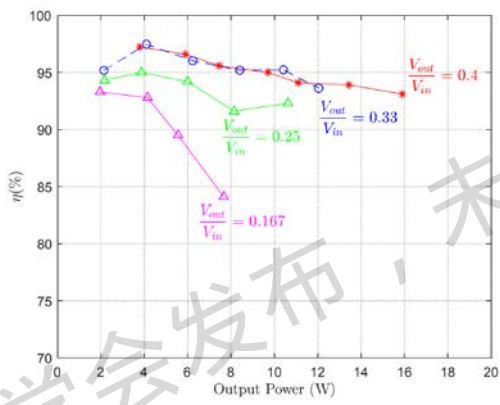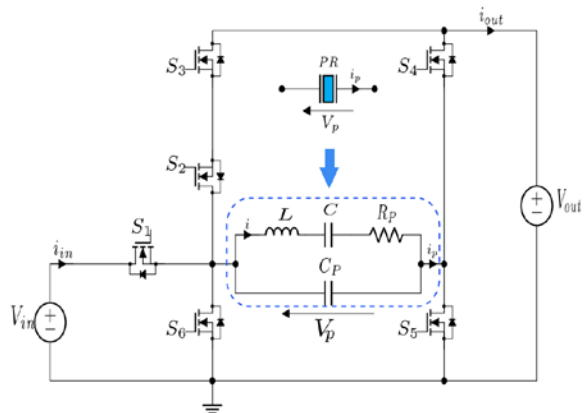

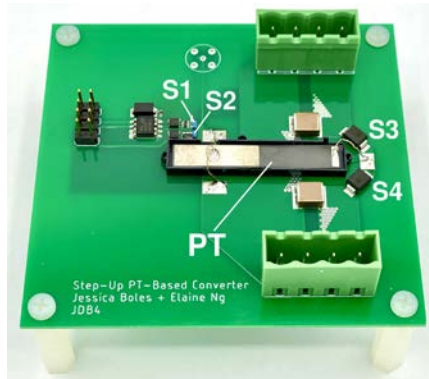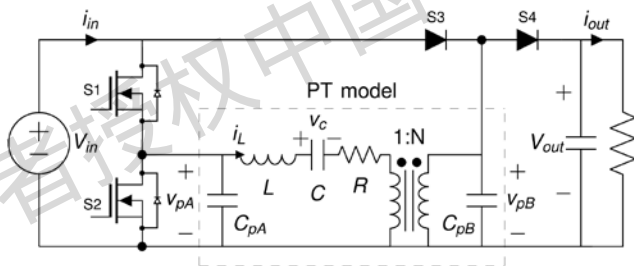M. Touhami et al., "A new topology of dc-dc converter based on piezoelectric resonator," COMPEL, Nov. 2020.




J. D. Boles et al., "Dc-dc converter implementations based on piezoelectric transformers," JESTPE, 2022.


Hybridization with switched capacitor or other techniques:





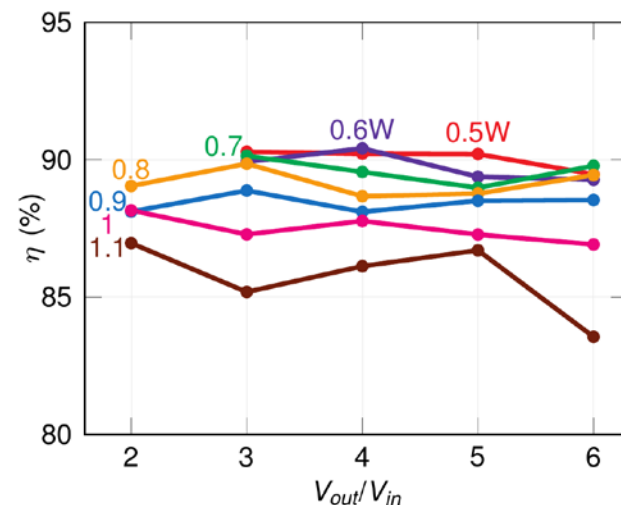
B. Wanyeki, "A Two-Stage Piezoelectric Resonator and Switched-Capacitor DC-DC Converter," MIT M.Eng Thesis, May 2022



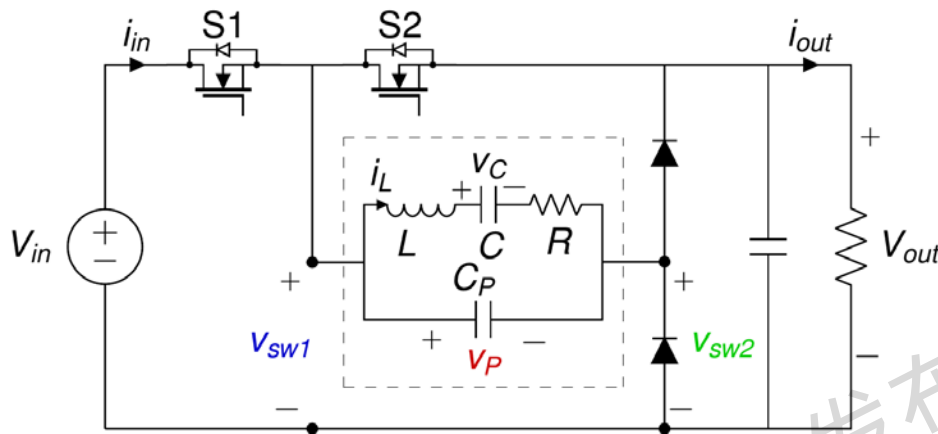Strategies are needed for implementing closed-loop control




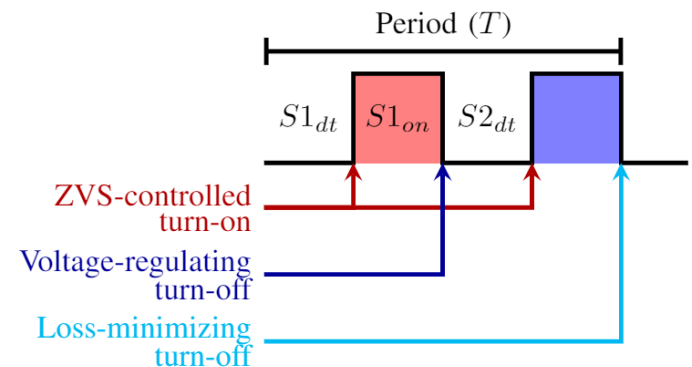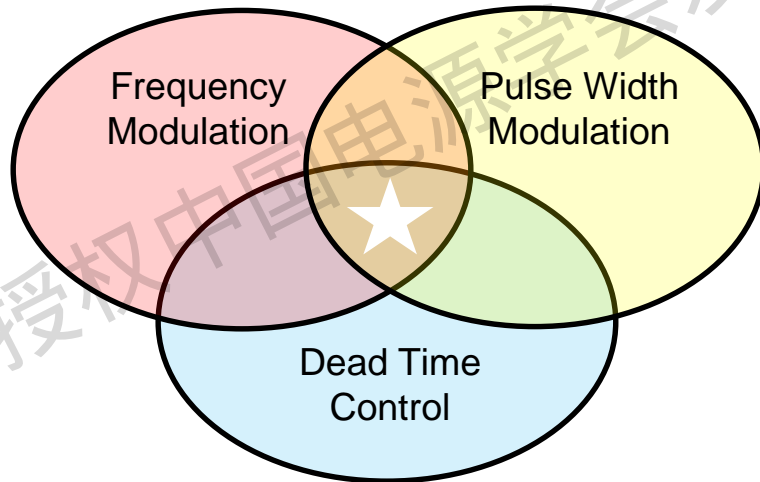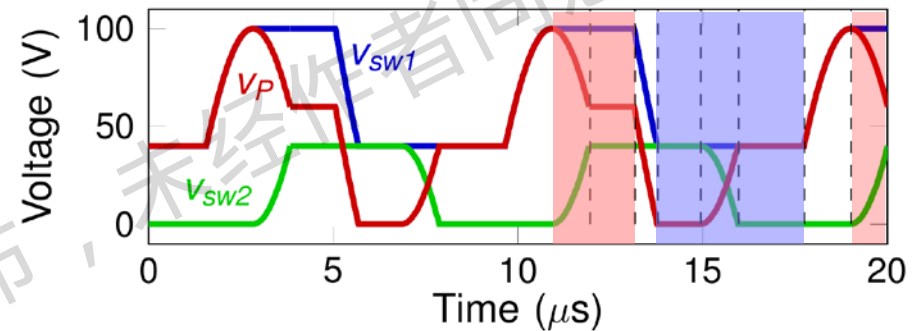Sequence: V_{in} - V_{out} , Zero, V_{out}
 Simulation for $V_{in} = 100$ V, $V_{out} = 40$ V, $P_{out} = 6$ W




S1 and S2 transitions play three different roles

■ e.g., Design to avoid spurious modes

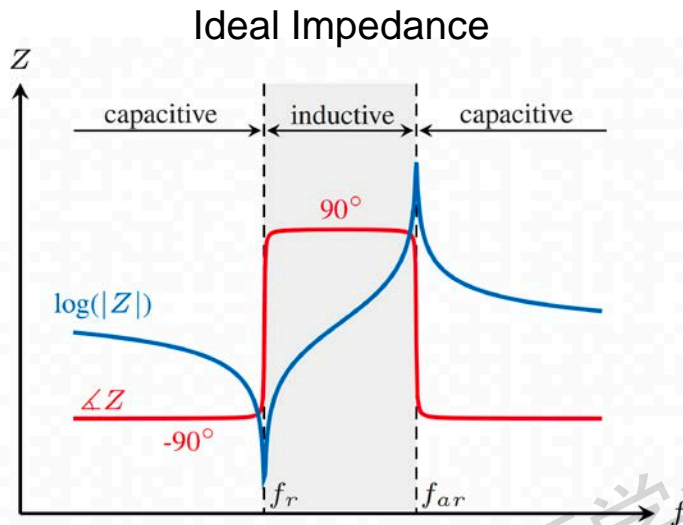


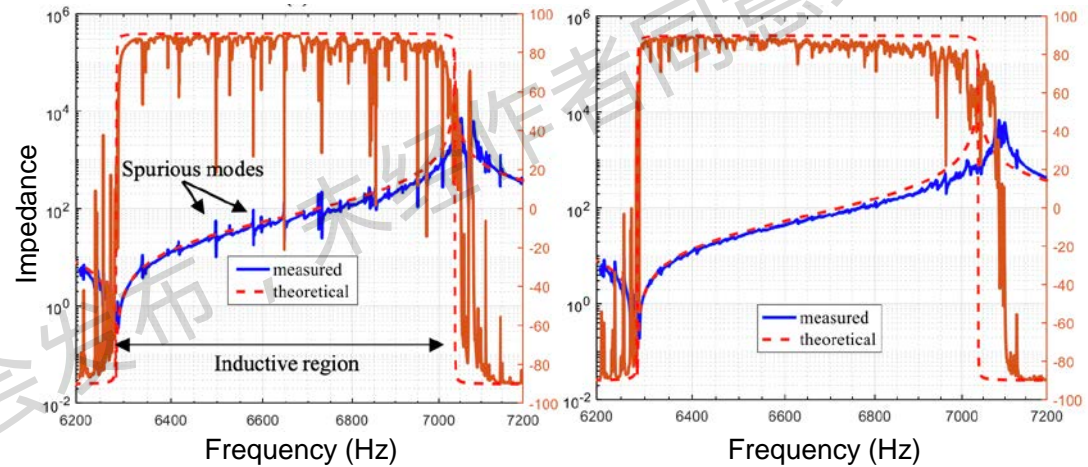Resonator shapes that reduce spurious modes:




M. Touhami et al., "Piezoelectric materials for the dc-dc converters based on piezoelectric resonators," COMPEL, Nov. 2021.

Modeling spurious modes:

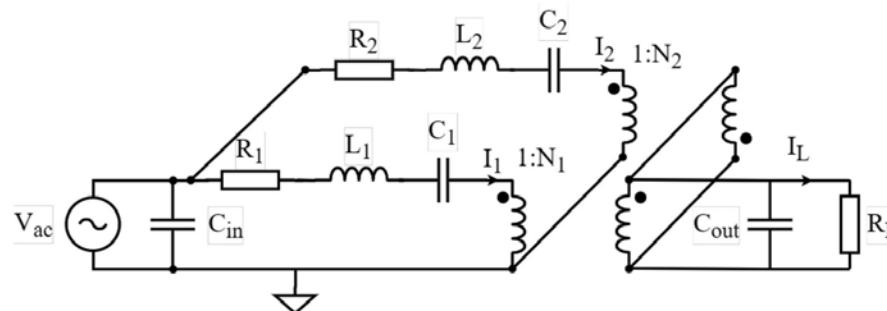


J. Forrester et al., "Influence of spurious modes on the efficiency of piezoelectric transformers: A sensitivity analysis," TPEL, 2020.

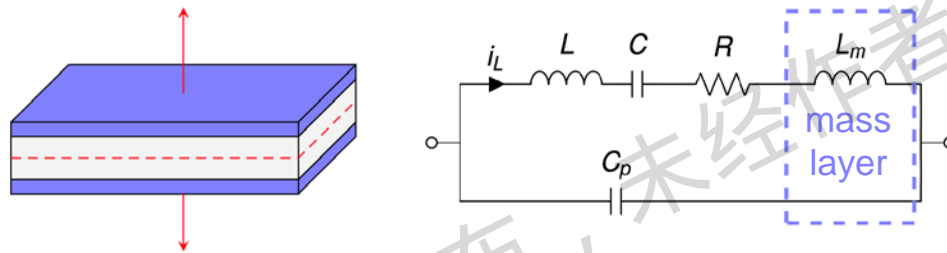- **Mass Augmentation for higher efficiency, density**
 - Introducing high-density mass layers offer improved energy storage performance




Bare vs. Augmented Piezo Impedance

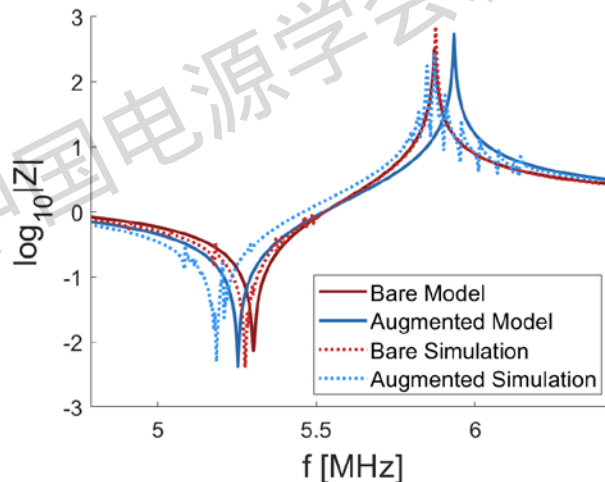

Augmented piezo design:
- **44%** loss ratio
+ **130%** power density

■ How to best mount, package and integrate PRs and PTs

Soldering:

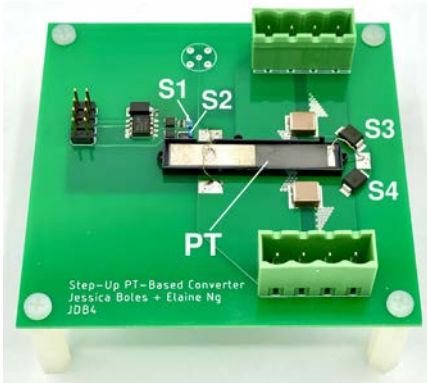

Ng, JESTPE 2022.

Desired Characteristics:

Minimal damping

Maximum thermal conductivity


Minimal added volume

Spring Mount:




Boles, MIT 2022.

Inactive Area:

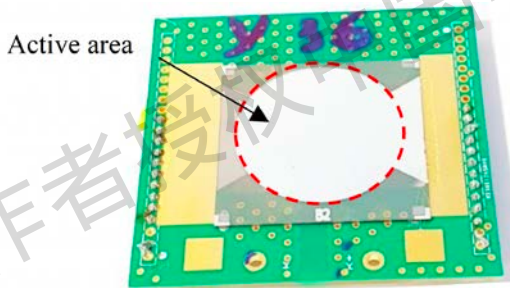


Tohumi, COMPEL 2021.

Wire Bonding:

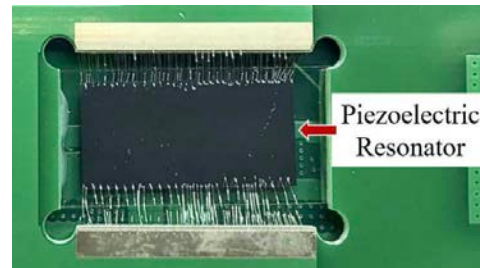


Stolt, OJPE, 2021.

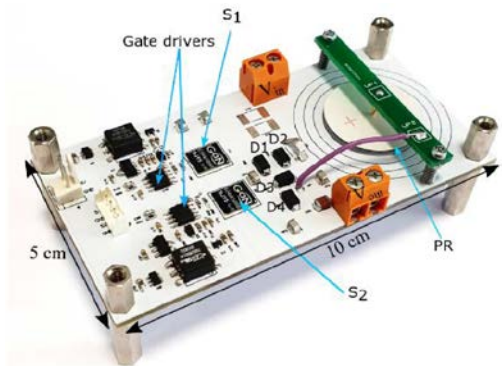



Tohumi, TPEL June, 2022.

■ Applications of piezoelectric energy storage


EMI Filter:

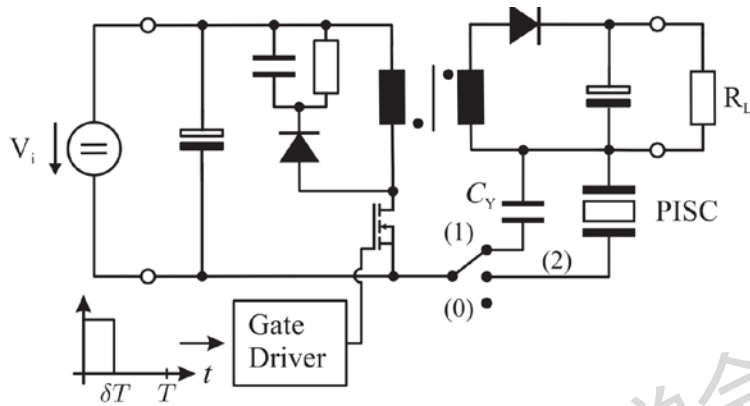

Class ϕ_2 Inverter:

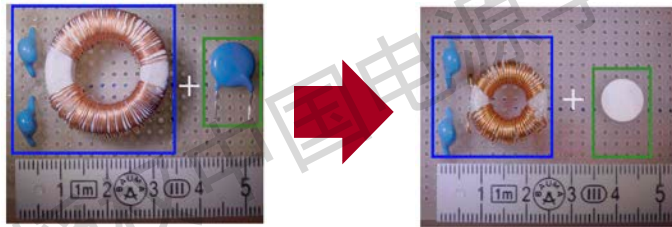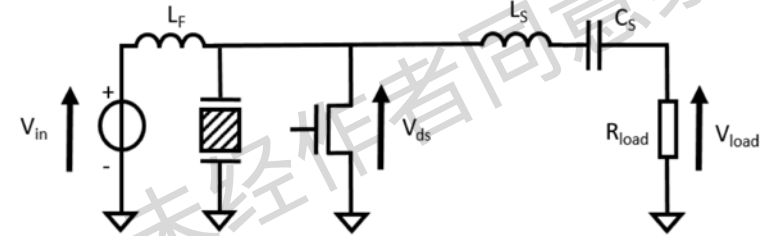

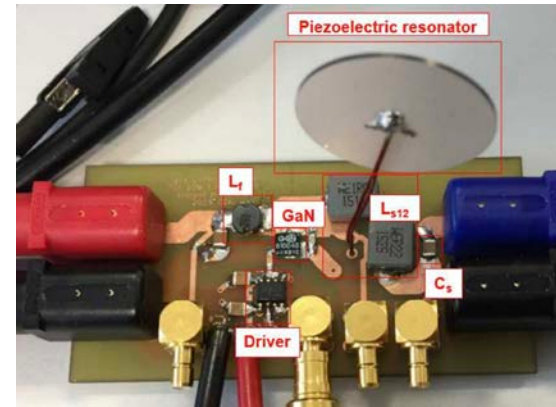F. Hubert et al., "Piezoelectric EMI filter for switched-mode power supplies." TPEL, 2021.



M. Vincent et al., "A new topology of resonant inverter including a piezoelectric component." ECCE Europe, Sept. 2021

Opportunities and Challenges

- **Piezoelectric-based power conversion offers tremendous potential advantages**
 - Substantial miniaturization, better scaling, batch fabrication,...
- **Recent work has shown the tremendous promise of this approach**
 - $> 1 \text{ kW/cm}^3$ component power density at high efficiency
 - *Much* higher performance is possible
- **Many opportunities for advances**
 - Circuit design and control
 - Materials & component design
 - Fabrication, packaging and integration
 - Systems and applications




The opportunities are large, and we're only at the beginning!

Acknowledgments



Joshua Piel

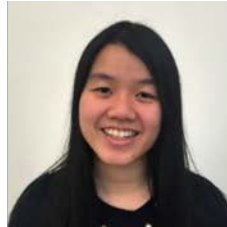

Elaine Ng



Babuabel Wanyeki



Pedro Acosta




Joseph Bonavia



Jessica Boles



Jeffrey Lang

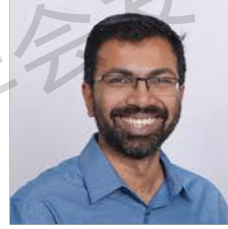


Dr. Yogesh Ramadass




- Zero-crossing detection of current for control
 - Challenging at high frequencies


Voltage differentiator:

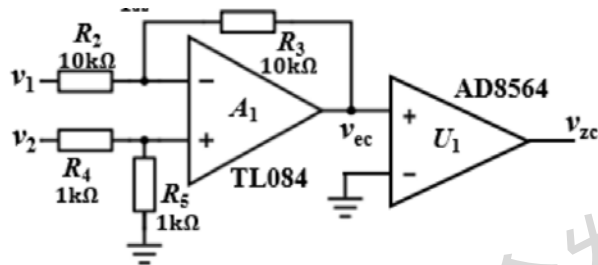

Anti-parallel diode voltage:

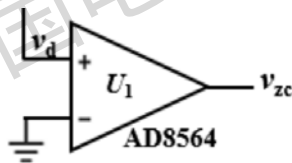

Geometric:

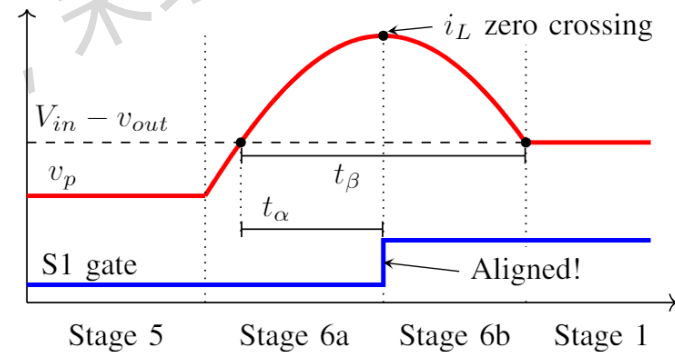


Z. Yang et al., "Resonant current estimation and phase-locked loop feedback design for piezoelectric transformer-based power supplies," TPEL, 2020.

J. J. Piel et al., "Feedback control for a piezoelectric-resonator-based dc-dc power converter," COMPEL, Nov. 2021.

Strategies to avoid spurious modes

Ideal Impedance

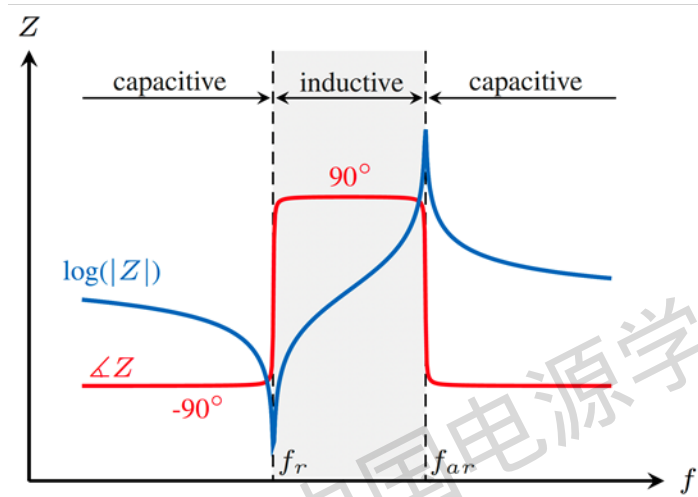

Operating modes that avoid spurious modes:

